

GCE

Electronics

Advanced GCE A2 7826

Advanced Subsidiary GCE AS 3826

Mark Schemes for the Units

June 2008

3826/7826/MS/R/08

OCR (Oxford, Cambridge and RSA Examinations) is a unitary awarding body, established by the University of Cambridge Local Examinations Syndicate and the RSA Examinations Board in January 1998. OCR provides a full range of GCSE, A level, GNVQ, Key Skills and other qualifications for schools and colleges in the United Kingdom, including those previously provided by MEG and OCEAC. It is also responsible for developing new syllabuses to meet national requirements and the needs of students and teachers.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by Examiners. It does not indicate the details of the discussions which took place at an Examiners' meeting before marking commenced.

All Examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the Report on the Examination.

OCR will not enter into any discussion or correspondence in connection with this mark scheme.

© OCR 2008

Any enquiries about publications should be addressed to:

OCR Publications
PO Box 5050
Annesley
NOTTINGHAM
NG15 0DL

Telephone: 0870 770 6622
Facsimile: 01223 552610
E-mail: publications@ocr.org.uk

CONTENTS

Advanced GCE Electronics (7826)

Advanced Subsidiary GCE Electronics (3826)

MARK SCHEMES FOR THE UNITS

Unit/Content	Page
General advice to Assistant Examiners on the procedures to be used	4
ADVICE TO EXAMINERS ON THE ANNOTATION OF SCRIPTS	6
2526 Foundations of Electronics	1
2527 Signal Processing Circuits	11
2529 Communications Circuits	27
2530 Control Circuits	34
Grade Thresholds	42

General advice to Assistant Examiners on the procedures to be used

YOU WILL BE REQUIRED TO UNDERTAKE PRACTICE AND STANDARDISATION SCRIPTS BEFORE STARTING TO MARK LIVE SCRIPTS, YOU WILL BE ADVISED OF THE AMOUNT OF SCRIPTS PRIOR TO THE MARKING PERIOD.

- 1 The schedule of dates for the marking of this paper is very important. It is vital that you meet these requirements. If you experience problems then you must contact your Team Leader (Supervisor) without delay.
- 2 An element of professional judgement is required in the marking of any written paper. Candidates often do not use the exact words which appear in the detailed sheets which follow. If you are in doubt about the validity of any answer then consult your Team Leader (Supervisor) by phone, the messaging system within SCORIS or e-mail.
- 3 Some questions may have a 'Level of Response' mark scheme. Any details about these will be in the rationale.
- 4 If an answer has been crossed out and no alternative answer has been written then mark the answer crossed out.
- 5 In addition to the award of 0 marks, there is a NR (No Response) option on SCORIS.

Award 0 marks

- if there is any attempt that earns no credit (including copying out the question or some crossed out working)

Award NR (No Response)

- if there is nothing written at all in the answer space
OR
 - if there is any comment which does not in any way relate to the question being asked (eg 'can't do', 'don't know')
OR
 - if there is any sort of mark which is not an attempt at the question (eg a dash, a question mark)
- 6 Abbreviations, annotations and conventions used in the detailed Mark Scheme. These vary from paper to paper, you will be advised in advance of the correct abbreviations, annotations and conventions to be used.

Highlighting is also available to highlight any particular points on the script.

7 The Comments box

The comments box will be used by your PE to explain their marking of the practice scripts for your information. Please refer to these comments when checking your practice scripts. You should only type in the comments box yourself when you have an additional object of the type described in Appendix B of the Handbook for Assistant Examiners and Subject Markers.

Please do not use the comments box for any other reason.

Any questions or comments you have for your team leader should be communicated by phone, SCORIS messaging system or e-mail.

8 Abbreviations, annotations and conventions that are used in this Mark Scheme vary from paper to paper. The following annotations are available for this paper.

(SO to add any others)

✓ and ✕

BOD - Benefit of doubt

NBOD – No benefit of doubt

TV - Too Vague

Highlighting is also available to highlight any particular points on the script.

ADVICE TO EXAMINERS ON THE ANNOTATION OF SCRIPTS

- 1 Please ensure that you use the **final** version of the Mark Scheme.
You are advised to destroy all draft versions.
- 2 Please mark all post-standardisation scripts in red ink. A tick (✓) should be used for each answer judged worthy of a mark. Ticks should be placed as close as possible to the point in the answer where the mark has been awarded. Ticks should **not** be placed in the right-hand margin. The number of ticks should be the same as the number of marks awarded. If two (or more) responses are required for one mark, use only one tick. Half marks ($\frac{1}{2}$) should never be used.
- 3 The following annotations may be used when marking. No comments should be written on scripts unless they relate directly to the mark scheme. Remember that scripts may be returned to Centres.


×	= incorrect response (errors may also be underlined)
^	= omission of mark
bod	= benefit of the doubt (where professional judgement has been used)
ecf	= error carried forward (in consequential marking)
con	= contradiction (where candidates contradict themselves in the <u>same</u> response)
sf	= error in the number of significant figures
up	= omission of units with answer
- 4 The marks awarded for each part question should be indicated in the right-hand margin. The mark total for each question should be ringed at the bottom right-hand side. These totals should be added up to give the final total on the front of the paper.
- 5 In cases where candidates are required to give a specific number of answers, mark the first answers up to the total required. Strike through the remainder.
- 6 The mark awarded for Quality of Written Communication in the margin should equal the number of ticks under the phrase.
- 7 Correct answers to calculations should obtain full credit even if no working is shown, unless indicated otherwise in the mark scheme.
- 8 Strike through all blank spaces and pages to give a clear indication that the whole of the script has been considered.


The following abbreviations and conventions are used in the mark scheme:


wttee	= words to that effect
/	= alternative correct answers
;	= separates marking points
NOT	= answers which are not worthy of credit
()	= words which are not essential to gain credit
<u> </u>	= (underlining) key words which must be used to gain credit
ecf	= error carried forward
ora	= or reverse argument
eor	= evidence of rule

2526 Foundations of Electronics

question	grade	expected answer	mark																																			
1a	DE	all four combinations of BA (any order)	1																																			
	DE	Q = 1 for BA = 01 or 10	1																																			
	DE	Q = 0 for BA = 11 or 00	1																																			
1b		C = NOT A	1																																			
		D = NOT B	1																																			
		ecf: E = A AND D	1																																			
		ecf: F = B AND C	1																																			
		ecf: Q = E OR F (ignore Q completely)	0																																			
<table><tr><td>A</td><td>B</td><td>C</td><td>D</td><td>E</td><td>F</td><td>Q</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>				A	B	C	D	E	F	Q	0	0	1	1	0	0	0	1	0	0	1	1	0	1	1	1	0	0	0	0	0	0	1	1	0	0	1	1
A	B	C	D	E	F	Q																																
0	0	1	1	0	0	0																																
1	0	0	1	1	0	1																																
1	1	0	0	0	0	0																																
0	1	1	0	0	1	1																																

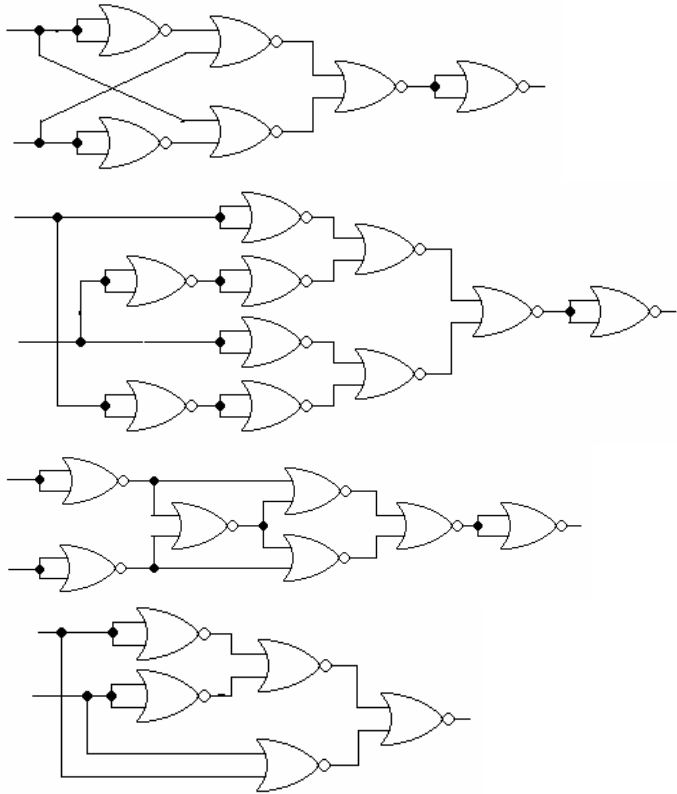question	grade	expected answer	mark
1c	DE	output generated by a NOR gate	1
	DE	correct use of blobs or bridges	1
	DE	use of NOR gates as inverters at inputs (joined inputs or one input low)	1
	BCD	correct symmetry between inputs	1
	BCD	any of the circuits shown below	1
			

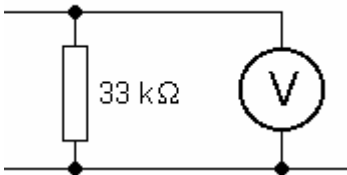question	grade	expected answer	mark
2a	DE	EITHER switch connects resistor to top supply rail (owtte)	1
	BCD	capacitor charges up <u>rapidly</u> (owtte) OR switch has very low resistance <u>short time constant</u> for charging circuit	1
2b	DE	correct symbol	1
	DE	in parallel with resistor 	1
2ci	DE	$\tau = RC$ (eor)	1
	BCD	units conversion: $R = 33 \times 10^3 \Omega$, $C = 2700 \times 10^{-6} \text{ F}$	1
	DE	ecf incorrect powers of ten: $RC = 33 \times 10^3 \times 2700 \times 10^{-6} = 89 \text{ s}$	1
2cii	DE	capacitor discharges	1
	DE	through resistor	1
	BCD	big time constant / small discharge current	1
2ciii	AB	EITHER $t = \tau \ln(V_0/V)$ or $V = V_0 e^{-t/RC}$ (eor)	1
	AB	ecf incorrect τ : $t = 89 \times \ln(15/2) = 179/180 \text{ s}$ OR drops by 0.37 in RC (eor) $0.37 \times 0.37 \times 15 = 2.0$, so $t = 2 \times 89 = 178 \text{ s}$ (ACCEPT 180 s) OR voltage halves in $0.7RC$ (eor) $15/8 = 1.9$, so $t = 3 \times 0.7 \times 89 = 187 \text{ s}$ (accept 190 s)	1

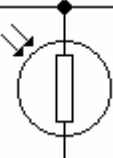
question	grade	expected answer	mark
3ai	DE	 any indication of this component	1
3aai	DE	resistance	1
	BC	increases for decreasing	1
	BC	light intensity	1
3aiii	BC	makes a voltage divider	1
	AB	(allows change of resistance) to become a <u>change of voltage</u> (owtte)	1
3bi	DE	$27 + 43 = 70 \text{ k}\Omega$	1
3bii	DE	$I = V/R$ (eor)	1
	DE	ecf incorrect R : $(15/70 \times 10^3) = 2.14 \times 10^{-4} \text{ A}$	1
	BCD	ecf incorrect I : units conversion: $214 \text{ }\mu\text{A}$ (ACCEPT $210 \text{ }\mu\text{A}$)	1
3biii	DE	$V = IR$ (eor)	1
	BCD	ecf incorrect I : $V = 2.14 \times 10^{-4} \times 43 \times 10^3 = \underline{9.2} \text{ V}$ ACCEPT resistor ratio or voltage divider formula evidence of rule for [1] correct answer for [1] $210 \text{ }\mu\text{A}$ gives $9.0(3) \text{ V}$	1
3c	DE	non-inverting input M below inverting input L (owtte)	1
	DE	output N (saturates) low (ACCEPT 0 V)	1
	BCD	at -13 V	1
	BCD	LED is forward biased / voltage across LED	1
	AB	therefore current in LED (so it glows)	1

question	grade	expected answer	mark														
4a	DE	first row correct	1														
	DE	last three rows correct <table border="1"><tr><td>W</td><td>U</td><td>Q</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	W	U	Q	0	0	1	0	1	0	1	0	0	1	1	0
W	U	Q															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
4b	DE	U goes high / becomes 1 / goes to 5 V	1														
	BCD	so Q goes low / becomes 0 V	1														
	BCD	no voltage drop / no forward bias across LED IGNORE references to current in LED	1														
4c	DE	EITHER (T low)															
	BCD	LED stays off	1														
	BCD	both inputs Q, T of left-hand gate low	1														
	AB	so output W high	1														
		so Q (stays) low / 0V	1														
		OR (T high because other switch closed)															
		LED comes on															
		one input of left-hand gate high															
		so output W low															
		so Q goes high / +5V															
4di	DE	SHOW: $P = VI$ - must be formula or correct equivalent, not a triangle	1														
	DE	$I = P/V$ (eor)	1														
	DE	$5 \times 10^{-3} / 1.8 = \underline{2.8} \times 10^{-3} \text{ A}$ ACCEPT $2.7 \times 10^{-3} \text{ A}$	1														
4dii	DE	$R = V/I$ (eor)	1														
	BCD	$V = 5 - 1.8 = 3.2 \text{ V}$	1														
	DE	ecf incorrect V: $R = 3.2 / 2.8 \times 10^{-3} = 1.1 \times 10^3 \Omega$ 600 Ω for [2] 1700 Ω for [2]	1														

question	grade	expected answer	mark
4diii	DE	LED destroyed by too much power / heat (NOT current or voltage)	1
	AB	current rises rapidly with increasing voltage	1
	BCD	resistor limits current / voltage to safe value	1

question	grade	expected answer	mark
5a	DE	[1] per correct box	4
	DE		
	DE		
	BCD		
5bi	DE	each cycle of mains lasts for 1/50 s	1
	DE	or 20 ms	1
	BCD	rectifier / diode bridge	1
	AB	charges capacitor at both positive and negative peaks of voltage / gives two peaks for each cycle / makes the negative voltage positive ACCEPT appropriate sketches of input and output waveforms	1
5bii	DE	one terminal to upper plate (any recognisable symbol)	1
	AB	other terminal to 0 V 	1
5biii	BCD	correct shape across whole screen	1
	BCD	correct timescale (pattern repeats every 10 ms)	1
	AB	correct peak voltage	1
	AB	correct ripple (ACCEPT half a division) 	1
5ci	DE		1

question	grade	expected answer	mark
5cii	DE	correct shape in forward bias (zero then sudden rise)	1
	BCD	correct shape in reverse bias (zero then sudden fall)	1
	AB	correct voltages for sudden increase of current (by eye)	1


 


question	grade	expected answer	mark
6ai	DE	output <u>only</u> low / 0 V / 0	1
	BCD	when both inputs high / 5 V / 1 IGNORE truth table any correct but incomplete description for [1]	1
6aia	DE	no ecf from (a)(i): C low when A and B high	1
	DE	C high otherwise	1
	DE	ecf incorrect C: D opposite of C	1
	DE	ecf incorrect D: Q low when D and E high	1
	DE	Q high otherwise	1

E	B	A	C	D	Q
0	0	0	1	0	1
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	0	1	0

question	grade	expected answer	mark
6bi	DE	resistance of thermistor decreases	1
	BCD	current increases / voltage across thermistor decreases	1
	AB	voltage across fixed resistor increases	1
6bii	DE	thermistor = $2.5 \text{ k}\Omega \pm 0.1 \text{ k}\Omega$	1
	DE	$I = V/R$ (eor)	1
	BCD	ecf incorrect thermistor resistance: $I = 5 - 2 / 2.5 \times 10^3 = 1.2 \times 10^{-3} \text{ A}$	1
	AB	$R = V/I = 2 / 1.2 \times 10^{-3} = 1.7 \text{ k}\Omega$ ACCEPT alternative method for full marks (resistor ratios or voltage divider formula) i.e. rule [1], substitution [1], correct answer for stated thermistor resistance [1]	1
6c	DE	E goes low / 0 / 0V	1
	DE	Q goes high / 1 / 5V	1
	DE	ecf incorrect Q: alarm sounds	1
	AB	ecf incorrect Q : LED goes out / off	1

question	grade	expected answer	mark
7ai	DE	0 V	1
	BCD	<u>negative</u> feedback (or equivalent explanation) NOT just "virtual earth" / "inputs at same voltage"	1
7aii	DE	$I = \frac{V_{in} - 0}{R_{in}}$	1
7aiii	BCD	$I = \frac{0 - V_{out}}{R_f}$ or $I = -\frac{V_{out}}{R_f}$	2
	AB	[1] for $I = \frac{V_{out}}{R_f}$ or $I = \frac{V_{out} - 0}{R_f}$ [2] for $I = \frac{V_{in} - V_{out}}{R_{in} + R_f}$	
7aiv	AB	$G = V_{out}/V_{in}$	1
	AB	linking expressions to answer e.g. $\frac{V_{in}}{R_{in}} = -\frac{V_{out}}{R_f}$ etc.	1

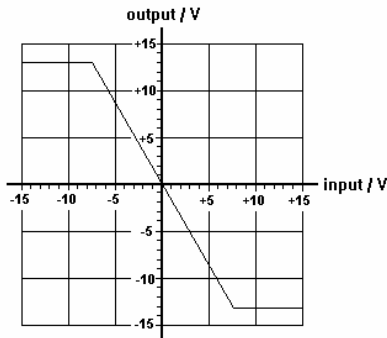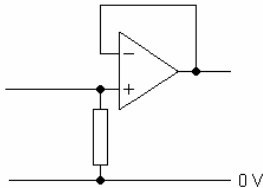7b	DE	straight line through origin (by eye)	1
	BCD	negative slope	1
	BCD	saturates at ± 13 V (NOT at ± 12.5 V)	1
	AB	gain of $(-1.74$ (13 V out for 7.5 V in)	1
			
7ci	DE	inverting input only connected to output (via resistor)	1
	BCD	(100 k Ω) resistor from non-inverting input to 0 V	1
	AB	input directly to non-inverting input	1
			
7cii	BCD	current at output larger than current at input	1
	AB	power amplifier increases VI (owtte)	1

question	grade	expected answer	mark
8a	DE	both A and B are high	1
8b	DE	G before A	1
	DE	A before E	1
	DE	E before D	1
	BCD	D before F	1
	BCD	F before C	1
		got any extra diodes for Christmas?	

Quality of Written Communication

- 3 The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.
- 2 The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.
- 1 The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.
- 0 The language has no rewardable features.

2527 Signal Processing Circuits

Question 1

(a) (i) NAND gate (1)

(ii)

A	B	Q
0	0	1
1	0	1
0	1	1
1	1	0

(1) (1) (1)

(iii) $Q = \overline{A \cdot B}$ (1)

(b) (i) $E = \overline{C}$ (1)

(ii) $F = \overline{D}$ (1)

(iii) $G = \overline{\overline{C \cdot D}}$ (1)

(iv) De Morgan's Theorem (1)

(v) OR gate (1)

(c) (i) $P = \overline{\overline{(K \cdot \overline{L})} \cdot \overline{(\overline{K} \cdot L)}}$ (1) (1)

or $= \overline{K \cdot L} + \overline{\overline{K} \cdot L}$

(ii) Exclusive OR (1)

(iii) Correct symbol for EOR gate (1)

Question 1

Additional guidance for markers

- a. i. gate correct (1)
- ii. correct A, B and Q columns (3)
 correct A and B columns (2)
 correct Q wrt incorrect answer to a. i. (1)
 allow A B columns either way around
- iii. correct $Q = \overline{A \cdot B}$ (1)
 ecf from a. ii. (1)
 Allow equivalent Boolean expressions

$$\text{Allow } Q = \overline{A} \cdot \overline{B} + A \cdot \overline{B} + A \cdot \overline{B}$$

$$\text{Allow } Q = \overline{A} + \overline{B}$$
- b. i. correct $E = \overline{C}$ (nothing else allowed) (1)
 ecf from a. ii. not allowed as different configuration
- ii. correct $F = \overline{D}$ (nothing else allowed) (1)
 ecf not allowed as for b. i.
- iii. $G = \overline{C \cdot D}$ or Boolean simplification (1)
 ecf from incorrect response to b. i. / ii. but correct interpretation of AND gate (1)
- iv. De – Morgan’s Theorem (1)
 Allow correct explanation of the Theorem for 1 mark
- v. correct - OR gate (1)
- c. i. Allow 1 mark for each term and 1 mark for operators (2)
 Remove one mark for each error made
 Allow $P = K \text{ “EOR” } L$ (where EOR is replaced by correct symbol)
- ii. Correct - EOR / XOR (1)
- iii. Correct symbol for EOR / XOR gate (1)
 Allow ecf for incorrect gate response to c. ii. (1)

Question 2

(a)

J	K	H
0	0	1
0	1	0
1	0	1
1	1	1

(1)

(b)

$$\overline{T} = R + S \quad (1)$$

(c)

X	Y	Z
0	0	0
0	1	0
1	0	1
1	1	0

1 for correct Z = (1)

1 for correct Z = (1)

Question 2

Additional guidance for markers

- a. Correct order (1 / 0 / 1 / 1) (1)
- b. Correct response (1)
- c. Correct order (0 / 0 / 1 / 0) (2)
 - For correct $Z = 0$ response (1)
 - For correct $Z = 1$ response (1)

Question 3

(a) (i) $I = P / V$ (1)

$$= 24 / 8$$

$$= 3 \text{ A} \quad (1)$$

(ii) pd lost across internal resistance $= I r$ (1)

$$= 3 \times 4$$

$$= 12 \text{ V} \quad (1)$$

power amplifier produces $= 12 + 8$ (1)

$$= 20 \text{ V}$$

(iii) Voltage gain of power amplifier $= 20 / 0.4$ (1)

$$= 50 \quad (1)$$

(b) (i) Current input to power amplifier $= 0.4 / 1.6 \text{ k}$ (1)

$$= 0.25 \text{ mA} \quad (1)$$

(ii) pd lost across internal resistance of cell $= 1.9 - 0.4$ (1)

$$= 1.5 \text{ V}$$

Internal resistance of solar cell $= 1.5 / 0.25$ (1)

$$= 6 \text{ k } \Omega \quad (1)$$

Question 3

Additional guidance for markers


- | | | |
|-------|---|-----|
| a. i. | Use of correct Power formula (may be implied) | (1) |
| | Correct response - 3A | (1) |
| ii. | Expected answer - | |
| | Formula for pd lost across internal resistance | (1) |
| | Correct response to pd | (1) |
| | Correct addition of pd's | (1) |
| | Alternative answer – | |
| | Resistance of motor – 2.7 ohms | (1) |
| | Total resistance - 6.7 ohms | (1) |
| | Correct use of resistance ratio | (1) |
| | Note: Allow incorrect current from a (i) for 2 marks | |
| iii. | Correct selection of ratio for voltage gain | (1) |
| | Correct calculation – 50 | (1) |
| | Allow 1 mark for use of Gain formula even if 8/0.4 | |
| | Not worried about units for Gain | |
| b. i. | Correct selection of values for I calculation | (1) |
| | Correct answer - 0.25 mA or other suitable form | (1) |
| ii. | Correct pd loss across ir of call | (1) |
| | Correct use of ohms law with 1.5V | (1) |
| | Correct answer – 6 kohms | (1) |
| | Allow ecf of incorrect I from b. i. but correct use of 1.5V for 3 marks | |
| | Correct use of equation with incorrect 1.9 V value for 1 mark | |

Question 4

(a)

two resistors used correctly (1)
 non-inverting input to 0V (1)
 capacitor in series with input (1)

 
input resistor 2.7 k Ω (1)
 voltage gain quoted as R_f / R_i (1)
 $R_f = 320 \times 2.7 = 864 \text{ k } \Omega$ (1)



C

Break frequency quoted as $1 / 2\pi RC$ (1)
 $= 1 / 2\pi \times 2700 \times 320$ (1)
 $= 1.84 \times 10^{-7} \text{ F}$
 $= 184 \text{ nF}$ (1)

(b)

 

any bass cut shape (1)
 break frequency at 320 Hz (1)
 flat frequency response beyond 320 Hz (1)
 power of 10 roll off below 320 Hz (1)

(c)

no change in frequency response within gain-bandwidth product of 10^6 (1)
 flat frequency response ends at about 3.2 kHz (1)
 thereafter the gain rolls off to 1 at 1 MHz (1)

Question 4

Additional guidance for markers

- a. As per expected mark scheme (9)
Correct calculation of Capacitor value allowed irrespective of positioning of capacitor in diagram
Allow input resistor values greater than 2.7k
- b. As per expected mark scheme (4)
- c. As per expected mark scheme (3)
Allow 1 mark for a repeat of a correct 4 b graph line

Question 5

- (a) Integrator or Ramp generator (1)
- (b) (i) $V_{\text{out}} / \text{time} = -V_{\text{in}} / RC$ (1)
 $= -5 / 220 \times 10^3 \times 22 \times 10^{-6}$ (1)
 $= -1.03 \text{ volt sec}^{-1}$ (1)
- (ii) The motor starts from rest and accelerates (backwards?) (1)
 It continues getting faster and faster (linearly?) for 13 seconds (1)
 At which point the output saturates (1)
 So the motor continues running at top speed for a further 7 seconds (1)
- (c) When input to circuit becomes zero the integrator freezes on its present output (1)
 So the motor will continue to run at top speed (1)
- (d) When S_1 is pushed the capacitor discharges more or less instantly (1)
 (So the output rises from -13V to 0V and the motor stops)
 Because S_2 is set to 0V no further integration takes place so the motor stays off (1)
- (e) Maximum voltage across motor will be in the order of $\pm 13\text{V}$ (1)
 So maximum current drawn from op-amp $\approx 130 \text{ mW} / 13\text{V} \approx 10 \text{ mA}$
 (Exam Board 081 type) op-amp cannot deliver much more than 10 mA (1)
- (f) Potential divider of two resistors drawn between +15V line and 0V
 with junction connected to the +5V line (1)
 Resistor values generate +5V as asked (1)
 Resistor values at least 10 times lower than 220 k Ω (to avoid loading effect) (1)
 Explanation of loading effect :
 e.g. current drained by 220 k Ω input resistor should be significantly smaller than current
 in potential divider otherwise the input will drop below +5V. (1)

Question 5

Additional guidance for markers

- a. Correctly identifies integrator / ramp generator (1)
- b. i. Correct selection of formula (1)
Correct use of R and C values (1)
Minus sign required
- ii. As per expected mark scheme (4)
Allow reference to saturation at 13V
- c. As S2 goes to zero, then no further charging (1)
so V(out) remains at -13v and motor remains at that speed (1)
- d. S1 discharges capacitor so V(out) rises by 13V to 0V (1)
Motor stops as input at S2 is zero so no integration (1)
- e. Calculation to indicate max I for motor is approx 10mA (1)
Reference to max current for TL081 being 10mA (1)
- f. i. Correct positioning of potential divider (1)
- ii. As per mark scheme (3)
R values <<220 kohms to avoid large current to op amp and
Reduction of pd below 5V

Question 6

- (a) *Saturation* When the output voltage tries to exceed op-amp power supplies or when output has (approx) reached supply line and can go no further (1)

Virtual earth When not saturated the two op-amp input voltages are almost identical
 Because of the huge open loop gain (or due to negative feedback)
 And as + input is wired to 0V the - input must be approx 0V also
 P is virtual because it is not a current source or sink (any) (1) (1)

- (b) (i) pd across top 10k resistor is 0.5V (0.5 at one end and 0V at other end)
 Similarly, pd across lower 10k is 0.2V (1)

$$\begin{aligned} \text{Current from } V_1 \text{ in } 10\text{k resistor} &= 0.5 / 10\text{k} = 50 \mu\text{A} \\ \text{Current from } V_2 \text{ in } 10\text{k resistor} &= 0.2 / 10\text{k} = 20 \mu\text{A} \end{aligned} \quad (1)$$

These currents add and as no current enters op-amp input it must all enter

□
 feedback resistor.

- (ii) Output voltage $V_{\text{out}} = I R = 70 \mu\text{A} \times 100 \text{ k} = 7\text{V}$ (1)
 and is -ve because the op-amp output is sinking this current (or wtte) (1)

- (c) In general, the current in the feedback resistor is the vector sum of the currents in the two input resistors

$$(V_1 - 0) / 10\text{k} + (V_2 - 0) / 10\text{k} = I_{\text{feedback}} = (0 - V_{\text{out}}) / 100\text{k} \quad (1)$$

$$\begin{aligned} V_{\text{out}} &= -100\text{k} (V_1 / 10\text{k} + V_2 / 10\text{k}) \\ &= -10 (V_1 + V_2) \end{aligned} \quad (1)$$

- (d) Voltmeter connected directly across either battery can only measure terminal pd to nearest volt so it cannot detect small differences

Batteries are connected with a common 0V line to make V_1 -ve and V_2 +ve

(1)

Circuit now operates according to $V_{\text{out}} = 10 (V_1 - V_2)$

(1)

So any difference in terminal pd is magnified tenfold and should allow the voltmeter to be read

(1)

Question 6

Additional guidance for markers

- a. Saturation – As per mark scheme (1)
Do not allow reference to “+13V” without explanation
- Virtual Earth - As per mark scheme (2)
Allow reference to high resistance of op amp input
Explanation required not just a statement
- b. i. As per mark scheme (4)
Alternative –
Allow use of voltage summer formula (1)
Correct values selected and used (1)
Correct answer (1)
Comment relating to no current entering op amp (1)
- ii. As per mark scheme (2)
- c. As per mark scheme (3)
“Show” requires use of formula plus V and R values
Providing voltage summer formula with no explanation (1)
- d. As per mark scheme (3)

Question 7

- Referee push button + resistor across power lines (1)
- Referee junction correctly connected to both Resets of D-types (1)
- X push button + resistor across power lines (1)
- Y push button + resistor across power lines
- X junction correctly connected to clock input of D-type (1)
- Y junction correctly connected to clock input of D-type
- NOT Q from X's D-type correctly connected to D input of Y's D-type (1)
- NOT Q from Y's D-type correctly connected to D input of X's D-type (1)
- Q outputs connected to LEDs + resistors to 0V (or NOT Q to +5V) □
- LEDs correctly labelled from corresponding contestant push buttons (1)

Question 7

Additional guidance for markers

As per mark scheme


(8)



Allow resets of D-types being "active low" and therefore "referee" switch and potential divider resistor positions could be reversed.

Allow 1 mark for X and Y push buttons and pull down resistors


Allow 1 mark for correct connections of both X and Y to clocks




Examples of alternative solutions

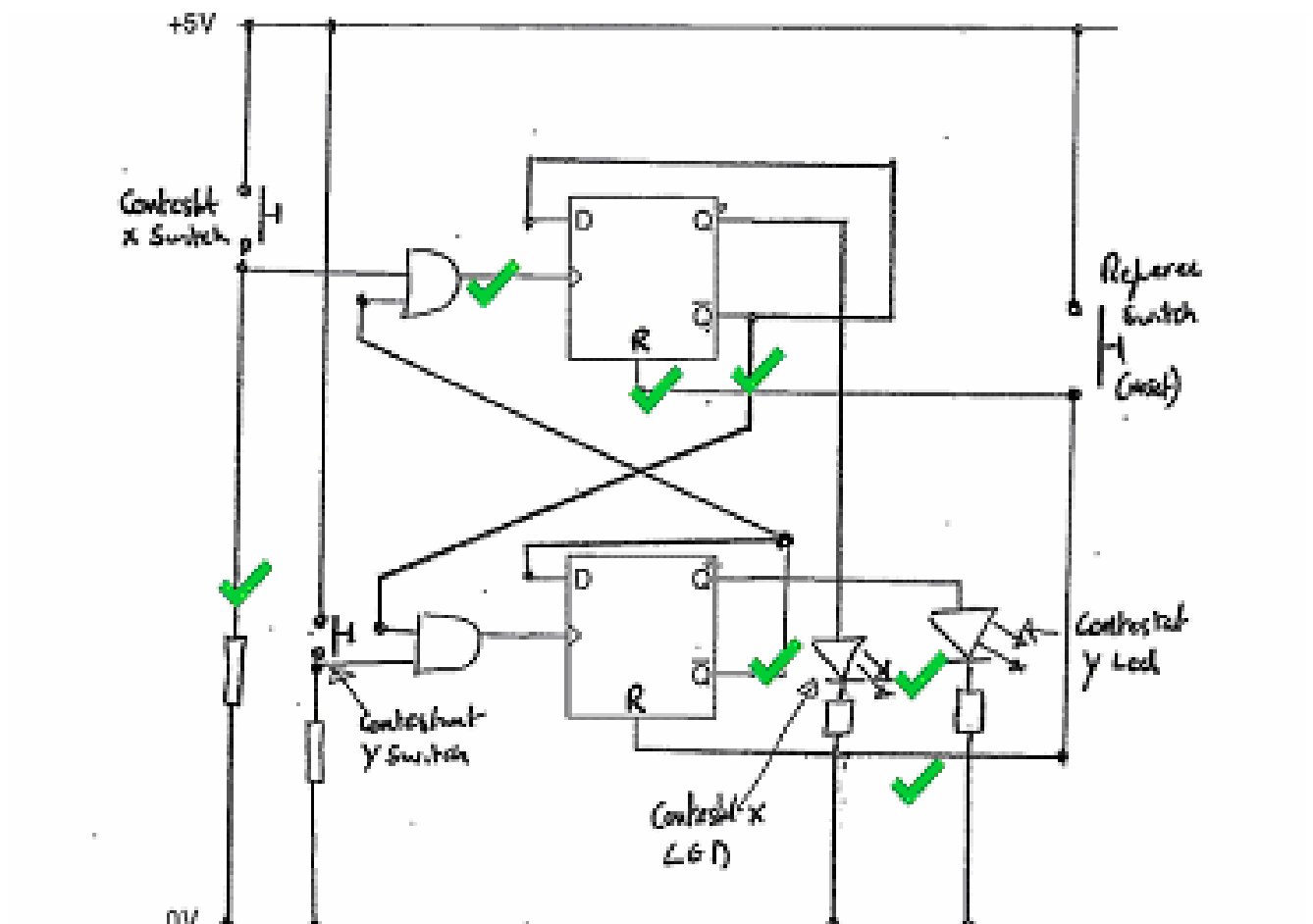

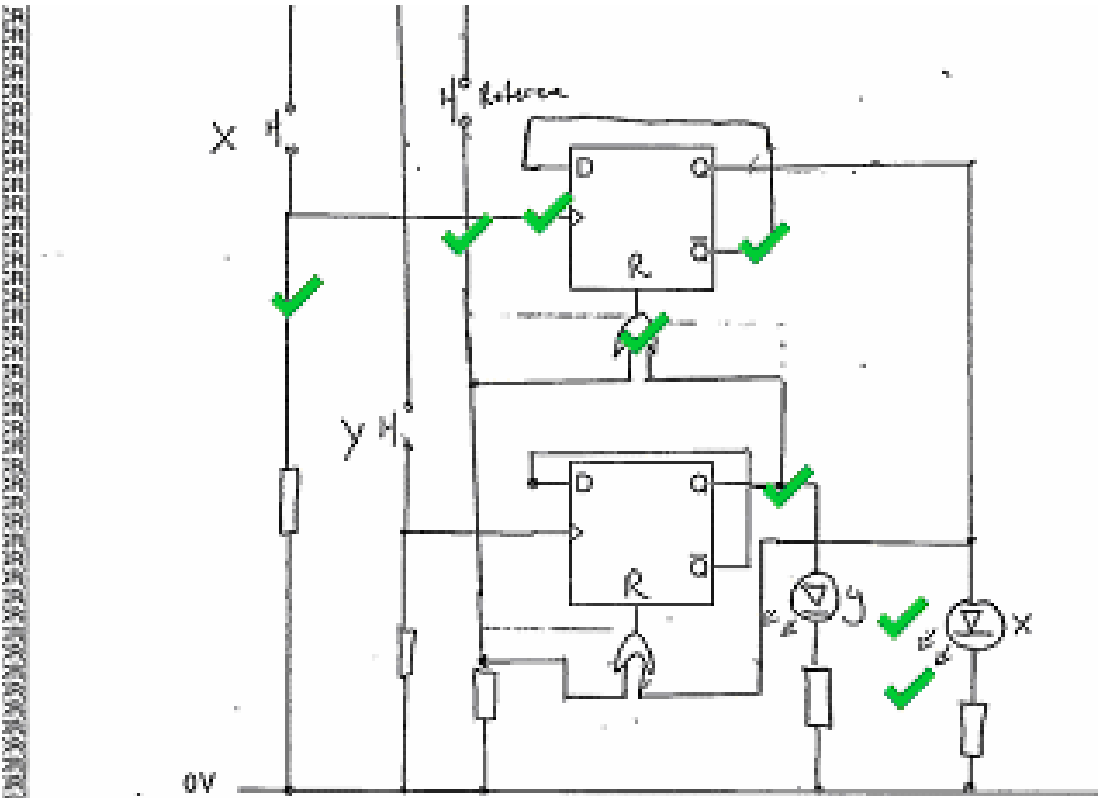
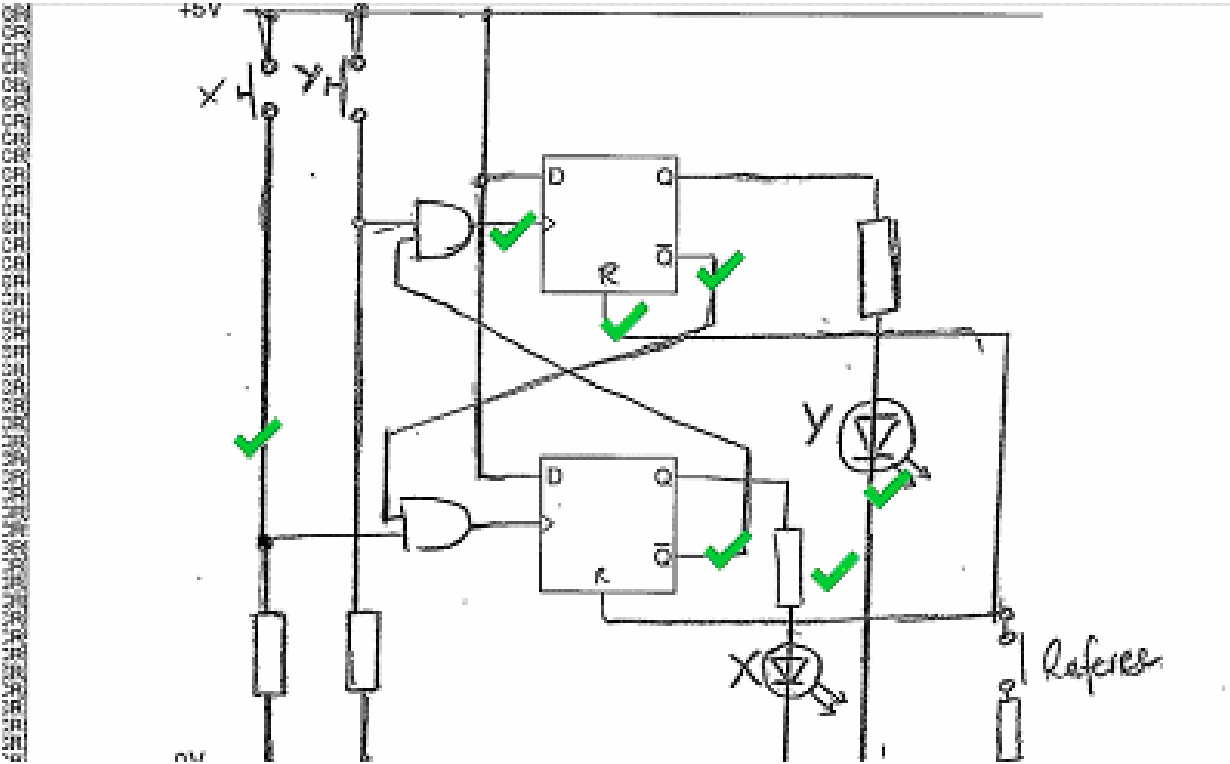





2529 Communications Circuits

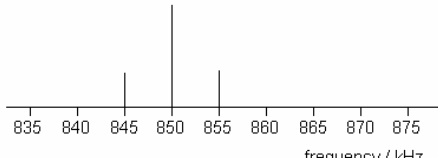
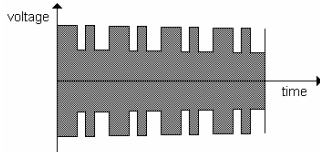
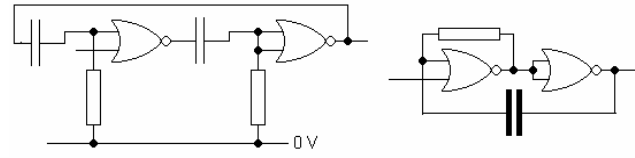
question	grade	expected answer	mark
1ai	BCD	$f_0 = \frac{1}{2\pi\sqrt{LC}}$ (eor)	1
	DE	correct units conversion: $L = 470 \times 10^{-6}$ H, $C = 91 \times 10^{-12}$ F	1
	AB	no ecf: $f_0 = 1 / 2\pi (470 \times 10^{-6} \times 91 \times 10^{-12})^{1/2} = \underline{7.7} \times 10^5$ Hz (NOT 7.6)	1
1aii	DE	tuned circuit has large impedance/reactance/resistance	1
	DE	at frequencies close to 800 kHz / resonant frequency	1
	BCD	only (alternating) current in the aerial at those frequencies	1
	AB	sets up an (alternating) voltage at G	1
1aiii	DE	any pattern with correct symmetry, peaking at 850	1
	DE	pattern extends from 845 to 855 only	1
	BCD	pattern is three spikes separated by 5 kHz	1
			
1b	DE	higher input resistance (impedance) / draws less current (power)	1
	BCD	any two of the following, [1] each:	2
	AB	<ul style="list-style-type: none"> raising Q of tuned circuit increasing sensitivity / increasing signal increasing selectivity / smaller bandwidth 	
1ci	DE	SHOW: $I = V/R$	1
	DE	$V = -3 - (-15) = 12$ V	1
	BCD	ecf incorrect V: $I = 12/2.2 \times 10^3$	1
	BCD	$I = \underline{5.5} \times 10^{-3}$ A (ACCEPT 5.5 / 5.4 mA)	1
1cii	DE	$V = IR$ (eor)	1
	DE	voltage drop = $5.5 \times 10^{-3} \times 2.2 \times 10^3 = 12.1$ V	1
	AB	so voltage at D = $15 - 12.1 = 2.9$ V	1
		5.4 mA gives 3.1 V 6 mA gives 1.8 V ACCEPT 3 V	
1d	DE	increasing voltage at gate increases source / drain current	1
	BCD	so more voltage drop across drain resistor	1
	AB	(top of drain resistor fixed) so drain goes down in voltage. ACCEPT reverse argument	1

question	grade	expected answer	mark
2ai	DE BCD	any two of the following, [1] each <ul style="list-style-type: none"> • higher quality transmission of signals / better SNR • because noise can be removed • by a Schmitt trigger • can be encoded / compressed • to speed up transmission / give smaller file 	2
2aii	DE BCD	any two of the following, [1] each <ul style="list-style-type: none"> • less bandwidth required • more channels available • less distortion • simpler circuitry • cheaper 	2
2bi	DE	amplitude modulated carrier	1
	DE	square wave modulation (ACCEPT 100% modulation)	1
	DE	higher frequency carrier (ACCEPT shading)	1
			
2bii	DE	each word needs start and stop bits	1
	DE	ecf: $\text{bit rate} = 10 \times 10 \times 10^3 = 100 \text{ kbits per second}$ (8 bits = 80 kbps)	1
	BCD	signal for widest spread of sidebands is 101010101	1
	AB	maximum modulation frequency therefore 50 kHz	1
	AB	sidebands at $\pm 50 \text{ kHz}$	1
2c	DE	correct circuit	3
	DE	[-1] per error or omission, minimum [0]	
	AB	R at least $10 \text{ k}\Omega$	1
	BCD	RC between $2 \times 10^{-4} \text{ s}$ and $5 \times 10^{-5} \text{ s}$	1
			
2d	DE BCD DCB		
		shift register in any box	1
		shift register anywhere before DAC	1
		DAC anywhere before filter	1

question	grade	expected answer	mark
3a	DE	correct output capacitor	1
	DE	correct input capacitor	1
	DE	input and output labelled	1
3b	DE	SHOW: $I = V/R$	1
	DE	$R = 130 \text{ k}\Omega$	1
	DE	ecf R : $I = 15/130 \times 10^3 = 1.15 \times 10^{-4} \text{ A}$ (ACCEPT $120 \text{ }\mu\text{A}$ or 0.12 mA)	1
	BCD	ecf I : $V = IR = 1.15 \times 10^{-4} \times 10 \times 10^3 = 1.2 \text{ V}$ NOT alternative method	1
3c	DE	SHOW: $I = V/R$	1
	BCD	$V = 1.2 - 0.7 = 0.5 \text{ V}$	1
	DE	ecf incorrect V : $I = 0.5 / 380 = 1.3 \text{ mA}$ 1.15 V gives 1.2 mA	1
		1.0 V gives 0.3 V 1.0 V gives 0.79 mA	
3di	DE	halfway between supply rails	1
	BCD	allows large amplitude output signal (owtte)	1
3dii	DE	$R = V/I$ (eor)	1
	DE	ecf incorrect I : $R = 7.5 / 1.3 \times 10^{-3}$	1
	DE	$R = 5700 \text{ }\Omega$	1
		1.2 mA gives $6.25 \text{ k}\Omega$ 0.79 mA gives $9.5 \text{ k}\Omega$	
		1.15 mA gives $6.5 \text{ k}\Omega$ 1 mA gives $7.5 \text{ k}\Omega$	
3diii	BCD	$G = -R_C/R_E$ (eor)	1
	BCD	ecf incorrect R_C : $G = -5700/380 = (-)15$	1
	AB	negative sign	1

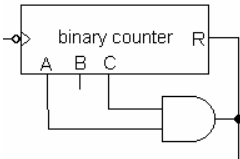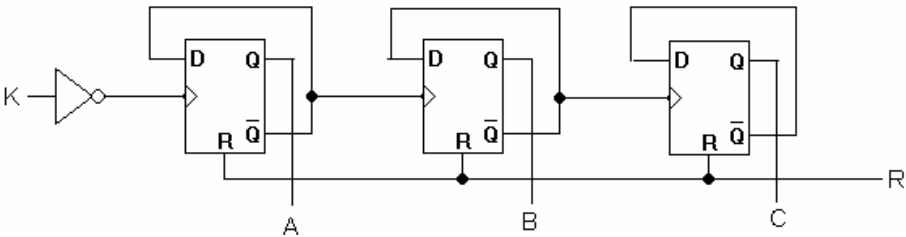question	grade	expected answer	mark
4a	DE	correct symbol for AND gate	1
	DE	inputs to A, C	1
	DE	output to R	1
			
4b	DE	D to Q-bar three times	1
	BCD	Q-bar to next clock twice	1
	DE	outputs A, B, C labelled correctly	1
	DE	reset and clock inputs labelled appropriately	1
	AB	NOT gate before first clock	1
	AB	all blobs or bridges as required	1
			
4c	DE	A before D	1
	BCD	D before F	1
	BCD	F before E	1
	AB	E before B	1
		all diodes feel extremely bad	
4d	DE	0 shows that word transmission has started	1
	AB	1 resets line so that subsequent start bit can be recognised (owtte)	1
		ACCEPT allows receiver to detect start of the word for [1] NOT just start and stop bits	
	DE	$6 \times 6.8 \times 10^6 = 4.1 \times 10^7$ (Hz) [1]	2
	BCD	$6 \times 512 \times 10^3 = 3.1 \times 10^6$ (Hz) [2]	

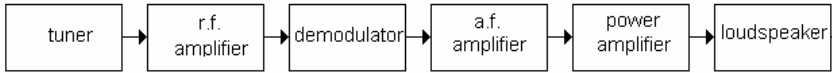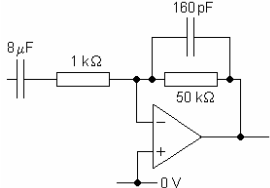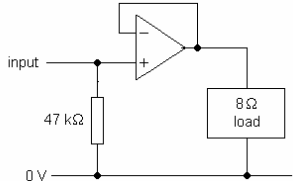question	grade	expected answer	mark
5a	DE	r.f. amplifier before a.f. amplifier	1
	DE	a.f. amplifier before power amplifier	1
	BCD	power amplifier before loudspeaker	1
			
5b	DE	$f_0 = 1/2\pi RC$ (eor)	1
	DE	$RC = 8 \times 10^{-3}$ s for bass cut filter	1
	DE	$RC = 8 \times 10^{-6}$ s for treble cut filter	1
	BCD	all R between 1 k Ω and 10 M Ω	1
	DE	overall midband gain 50	1
	AB	bass cut filter circuit	1
	AB	treble cut filter circuit	1
			
5ci	AB	ACCEPT two stage circuit	1
	BCD	negative feedback to give voltage gain of 1	1
	DE	input to non-inverting terminal (ignore 47 k Ω in series) ecf: input resistance of 47 k Ω	1
			
5cii	DE	$V_0 = \sqrt{2} \times V_{rms}$ (eor)	1
	DE	$V_0 = 1.414 \times 9 = \underline{12.7}$ V	1
5ciii	DE	SHOW: $I = V/R$	1
	BCD	ecf $V: I = 12.7 / (4 + 8) = 1.06$ A	1
	AB	$V = IR = 1.06 \times 8 = \underline{8.5}$ V	1
		13 V gives 8.7 V ACCEPT use of voltage divider formula / idea stated rule [1], substitution [1], answer [1]	
5civ	DE	$P = VI$ (eor) or V^2/R (eor)	1
	DE	ecf $I, V: P = 8.5 \times 1.06 = 9.0$ W	1

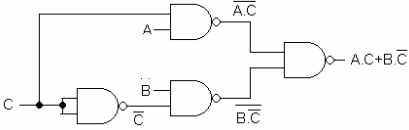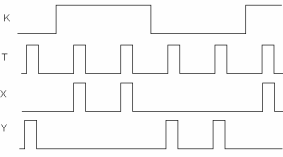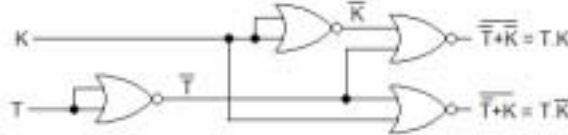
question	grade	expected answer	mark																				
6a	DE	more than one signal / channel	1																				
	DE	sent down a single link	1																				
	BCD	by allowing each signal / channel access to the link for short times	1																				
6bi	DE	De Morgan's Theorem:	1																				
	BCD	correct use e.g. $T = \overline{\overline{A.C}} + \overline{\overline{B.C}} + \overline{\overline{A.B}}$	1																				
	AB	Race Hazard Theorem: $T = (A.C) + (B.C) + (A.B) = (A.C) + (B.C)$	1																				
6bii	DE	NAND gate to generate NOT C	1																				
	BCD	NAND gates to generate inverse of each term	1																				
	BCD	NAND gate to generate output	1																				
	AB	correct algebra at output of each gate, e.g.	1																				
																							
6ci	DE	full marks for any NAND gate circuit which works and is justified																					
	DE	ignore blobs or bridges																					
	DE	all four combinations of TK	1																				
	DE	X correct	1																				
	DE	Y correct	1																				
		<table border="1"> <thead> <tr> <th>T</th><th>K</th><th>X</th><th>Y</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	T	K	X	Y	0	0	0	0	0	1	0	0	1	0	0	1	1	1	1	0	
T	K	X	Y																				
0	0	0	0																				
0	1	0	0																				
1	0	0	1																				
1	1	1	0																				
6cii	DE	X correct (by eye)	1																				
	DE	Y correct (by eye)	1																				
																							
6cii	DE	NOR to generate NOT K (and NOT T) - including one input low	1																				
	BCD	correct NOR gate circuit for X	1																				
	BCD	correct NOR gate circuit for Y	1																				
	AB	truth table or algebra showing outputs of all gates e.g.	1																				
																							
		IGNORE number of gates used.																					


Quality of Written Communication

- 3 The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.
- 2 The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.
- 1 The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.
- 0 The language has no rewardable features.

2530 Control Circuits

Question	Expected answer		Mark
1	(a)	Program counter	Register inside the microprocessor
			Holds address of next memory location to be accessed
			Is normally incremented by one to move through memory
			Can be loaded with new memory location for Jumps
	(any two) (1)(1)		[2]
	(b)	Accumulator	Register inside the microprocessor
			Holding data which can be processed/controlled
	(c)	Look-up table	Area of memory
			Where only data is stored
	(d)	Arithmetic Logic Unit	Circuitry inside microprocessor
			Carries out any logic functions or arithmetic processing

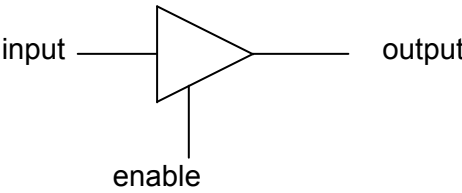Question	Expected answer	Mark
2 (a) (i)	E = logic 1	[1]
	Because OR / NOR gates are frozen with a logic 1 input	[1]
	or because this produces a logic 0 output from both NOR gates	[1]
	(ii) The output <u>floats</u>	[1]
	because it is not connected to any power line/no defining voltage	[1]
(b)	To energise a relay there must be a logic 1 at the NOR output	
	Logic 1 output is only produced by both inputs being logic 0	[1]
	The inverter from D means there can never be a double logic 0 at inputs	[1]
(c)	To energise relay 1 there must be two logic 0s at the NOR inputs	[1]
	Thus E = 0 and D = 1	[1]
(d) (i)	Tristate,	[1]
	(ii)	
		
	allow ECF from d(i) (ignore any inversion circles) (1) (1)	[2]
(iii)	It allows multiplexing where multiple users can share the same data line for economy of tracking/wiring (1) (1)	[1]

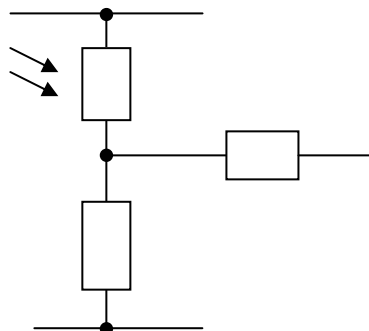Question	Expected answer	Mark	
3	(a)	Maximum resistance R_1 = 24V / 30mA	[1]
		= 800 Ω	[1]
	(b)	Motor current = 100W / 24V	[1]
		= 4.2 A	[1]
		Current rating for T_2 \geq 5A	[1]
	(c) (i)	Maximum R_2 = 24V / 4mA	[1]
		= 6 k Ω	
		Maximum R_3 = 24V / 50mA	[1]
		= 480 Ω	
	(d)	Pressing S_1 allows a current in excess of minimum 30mA in gate to fire T_2	[1]
		Once fired, the gate ceases to have any effect so the switch S_1 can be released	[1]
	(e)	Before pressing S_2 when T_1 is still conducting, plate A = +24V plate B \approx 0V	[1]
		Pressing S_2 allows a current in excess of minimum 4mA in gate to fire T_2 . Thus plate A falls rapidly to \approx 0V Thus plate B also falls rapidly to \approx - 24V	[1]
		Triac T_1 is thus momentarily deprived of its main current so it switches off	[1]
(f)		Any potential divider with LDR	[1]
		LDR in correct position	[1]
		Junction connected to R_2	[1]
(g)	Once fired by the gate, the triac cannot be turned off by the same initiation or once fired the triac latches (or wtte)		
	Hence very limited use eg burglar alarms		
	In ac circuits the supply is constantly returning to zero hence triac is constantly turned off every half cycle		
		(any two) (1) (1)	

Question	Expected answer	Mark
4 (a)	<i>Isolation</i> This means there is no electrical connection between the two circuits or the power supply for A has no reference whatsoever to that of B (or wtte)	[1]
(b) (i)	Transformer	[1]
(b) (ii)	Changing current or voltage from A in primary coil creates variations Variation induce /create varying current or voltage in B Changing magnetic flux generates induced emf in secondary coil to B	[1]
	(allow 1 mark for a simple explanation of an ac input generating an ac output)	[1]
(c) (i)	Optoisolator or Optocoupler or optotransistor	[1]
(c) (ii)	Current from A generates light emission from LED	[1]
	Light falls on phototransistor and generates current in circuit B	[1]
(d)	The transformer in Fig 4.1 can only transmit wobbly/ac signals and generally within a fairly limited bandwidth The optoisolator in Fig 4.2 can transmit dc signals or ac signals and generally over a fairly broad bandwidth Include signal size;include voltage range	[1]
	Difference between -1 mark Explanation of difference -1mark	[1]

Question	Expected answer	Mark
5	(a)	[1]
	Total number of address locations = $2^{\text{number of address pins}}$	
	8192 = 2^n	[1]
	$n \log 2 = \log 8192$	[1]
	$n = 13$	
	(b)	
	Total number of memory cells = total addresses x number of data pins	
	number of data pins = $131072 / 8192$	
	= 16	[1]
	Allow ECF from (a)	
	(c)	[1]
	Address information on bus can only flow one way into chip from μP	
	(d)	[1]
	Data can flow into or out of the chip so flows both ways on data bus	
	(e)	[1]
	Address bus must be set up with the location of memory store in RAM	
	The R / \overline{W} = logic 0 and the chip is in WRITE mode	[1]
	the data to be stored is placed on the data bus by μP or peripheral	
	The Enable pin is pulsed low and the data word is swallowed and stored	[1]
	The R / \overline{W} = logic 1 and the chip is in READ mode	[1]
	The Enable pin is made logic 0	
	the data stored at the active address is placed on the data bus in order to exit RAM and travel to μP or peripheral for use.	[1]
	Alternative	
	Correct Sequence 1mark	
	\overline{R} = 1 read (1) \overline{E} =0 enable (1)	
	\overline{W} =0 write (1) Address first (1)	

Question	Expected answer			Mark		
6	(a)	Address	Contents	Explanation	[1]	
		00	3E 00	Accumulator = 00		
		02	32 AA	Move 00 to memory location AA		
		04	32 BB	Move 00 to memory location BB	[1]	
		06	3E 03	Accumulator = 03		
		08	32 FF	Output 03	[1]	
		Summary	Clear contents of memory locations AA and BB Then unfreeze D-types And display zero on both 7-segment displays Keeps LED off (any 2 for 2marks)	[1]		
				[1]		
		(b)	Address	Contents	Explanation	
			0A	3A EF	Swallow input port	[1]
	0C		E6 80	Mask for test switch only	[1]	
	0E		CA 0A	If zero, go back and input again	[1]	
	10		3E 00	Accumulator = 00		
	12		6F	X register = 00	[1]	
	13		C9	increment X register		
	14		7D	Move X contents to Accumulator		
	15		C2 13	(all for 1 mark)	[1]	
	17		C3 30	If not yet zero, return to increment X further jump to address 30 (not load Pc with 30)	[1]	
	Summary		Wait until the test switch has been pushed	[1]		
			Then execute a short time delay	[1]		
	(c)		Address	Contents	Explanation	
			30	3E 40	Accumulator = 40	[1]
			32	32 FF	Output 40	
			34	3A EF	Swallow input	
			36	E6 11	Mask for A or B inputs only*	
		38	CA 34	if still zero go back and input again (all for 1 mark)	[1]	
		3A	E6 10	Mask for A alone		
3C		C2 50	if A's button is pressed go to address 50	[1]		
3E		C3 60	if not A then must be B so go to 60 (all for 1 mark) *key point for the mark			
Summary		This section lights up the LED Unfreezes the D-types Blanks out both 7-segment displays Then it waits for either A or B to press their switch If A has won then got to address 50 otherwise go to address 60 for B win	[1]			
		[1]				
		[1]				
		[1]				

Question	Expected answer			Mark	
(d)	Address	Contents	Explanation	[1]	
	50	3A AA	Accumulator = A's current score		
	52	C6 04	Increment A's score by one		
	54	32 AA	and save new score back in memory		
			AA		
	56	C3 70	go to address 70		
			(all for 1 mark)		
	60	3A BB	Accumulator = B's current score		
	62	C6 04	Increment B's score by one		
	64	32 BB	and save new score back in memory		
		BB	[1] [1]		
66	C3 70	go to address 70			
Summary	This section either increments A's score by one point Or it increments B's score by one point After which it jumps to address 70				
(e)	Address	Contents		Explanation	[1]
	70	3E 80		Accumulator = 80	
	72	32 FF		Output	
	74	3A AA		Accumulator = A's current score	
	76	C6 02		Add 02	
	78	32 FF		Output	
	7A	3A BB	Accumulator = B's current score		
	7C	C6 01	Add 01		
7E	32 FF	Output	[1] [1]		
80	3A EF	Swallow input port			
82	E6 80	Mask for test switch only			
84	CA 74	If test zero go back to output score of A then B			
86	C3 10	If test positive, go back to time delay sequence			
Summary	This section resets all three D-types Then it takes A's current score and adds 02 (ie logic 1 to activate A's display) Then it lights up A's display while that of B is blanked. (and at the same time unfreezes the D-types) Then it takes B's current score and adds 01 (ie logic 1 to activate B's display) Then it lights up B's display while that of A is blanked. (and still unfreezes D-types) Then it swallows the input to see if the referee has pressed the test switch. If not then it returns to the loop of flashing A's score and then flashing B's score after each check on the test switch.				

Question	Expected answer	Mark
	Once the referee has pressed the test switch the program jumps back to address 10	[1]
	Alternative applies to bold type	
	Adds 02 to A and explains why and display or wtte(1)	[1]
	Adds 01 to B and explains why display or wtte	
	A and B displayed alternately (1)	

Grade Thresholds

Advanced GCE Electronics 3826 7826
June 2008 Examination Series

Unit Threshold Marks

Unit		Maximum Mark	A	B	C	D	E	U
2526	Raw	120	86	77	69	61	53	0
	UMS	120	96	84	72	60	48	0
2527	Raw	90	59	52	45	39	33	0
	UMS	90	72	63	54	45	36	0
2528	Raw	78	61	54	47	40	33	0
	UMS	90	72	63	54	45	36	0
2529	Raw	120	87	78	69	61	53	0
	UMS	120	96	84	72	60	48	0
2530	Raw	90	65	59	53	47	41	0
	UMS	90	72	63	54	45	36	0
2531	Raw	90	71	64	58	52	46	0
	UMS	90	72	63	54	45	36	0

Specification Aggregation Results

Overall threshold marks in UMS (ie after conversion of raw marks to uniform marks)

	Maximum Mark	A	B	C	D	E	U
3826	3826	300	240	210	180	150	120
7826	7826	600	480	420	360	300	240

The cumulative percentage of candidates awarded each grade was as follows:

	A	B	C	D	E	U	Total Number of Candidates
3826	22.8	36.7	55.3	69.7	83.1	100	699
7826	32.1	52.5	72.8	86.5	96.1	100	421

1120 candidates aggregated this series

For a description of how UMS marks are calculated see:

http://www.ocr.org.uk/learners/ums_results.html

Statistics are correct at the time of publication.

OCR (Oxford Cambridge and RSA Examinations)
1 Hills Road
Cambridge
CB1 2EU

OCR Customer Contact Centre

(General Qualifications)

Telephone: 01223 553998

Facsimile: 01223 552627

Email: helpdesk@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; 1 Hills Road, Cambridge, CB1 2EU
Registered Company Number: 3484466
OCR is an exempt Charity



OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553