

ADVANCED GCE
ELECTRONICS
Control Circuits

2530

Candidates answer on the Question Paper

OCR Supplied Materials:

- Microprocessor Instruction Set (inserted)

Other Materials Required:

- A calculator may be used

Tuesday 8 June 2010
Morning

Duration: 1 hour 15 minutes



Candidate Forename		Candidate Surname	
--------------------	--	-------------------	--

Centre Number						Candidate Number				
---------------	--	--	--	--	--	------------------	--	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name clearly in capital letters, your Centre Number and Candidate Number in the boxes above.
- Use black ink. Pencil may be used for graphs and diagrams only.
- Read each question carefully and make sure that you know what you have to do before starting your answer.
- Answer **all** the questions.
- Do **not** write in the bar codes.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your Candidate Number, Centre Number and question number(s).

INFORMATION FOR CANDIDATES

- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **90**.
- You may assume, unless otherwise stated, that:
 - (i) the p.d. across a forward-biased silicon diode is 0.70 V,
 - (ii) the base-emitter p.d. for a conducting silicon transistor is 0.70 V,
 - (iii) the power supplies for operational amplifiers are +15 V and –15 V,
 - (iv) the saturation levels for operational amplifiers are +13 V and –13 V,
 - (v) logic 1 = 5 V and logic 0 = 0 V.
- The quality of written communication will be assessed in your answers to all the questions.
- **QUESTION 7 REQUIRES THE MICROPROCESSOR INSTRUCTION SET INCLUDED.**
- This document consists of **16** pages. Any blank pages are indicated.



**A calculator may
be used for this
paper**

1 Explain the following as they apply to microprocessor systems.

(a) General Purpose Register.

.....

.....

.....

..... [2]

(b) Fetch – execute cycle.

.....

.....

..... [2]

(c) Subroutine.

.....

.....

..... [2]

(d) Handshaking.

.....

.....

..... [2]

2 A tristate can be used as part of a microprocessor memory system.

(a) Draw the symbol for a tristate.

Label the input, output and enable.

[2]

(b) Complete the truth table below for a tristate.

Enable	Input	Output

[2]

(c) Explain why tristates are used in microprocessor systems.

.....

.....

.....

..... [2]

- 3 (a) Fig. 3.1 shows a circuit symbol for a triac.

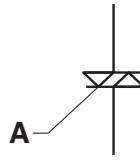


Fig. 3.1

- (i) State the name of terminal **A**.

A [1]

- (ii) Describe how a triac can control alternating current in a load.

.....

 [3]

- (iii) Explain why it is easier to control the operation of a triac with alternating current rather than direct current.

.....

 [2]

(b) Fig. 3.2 shows a triac being used as part of a protection circuit for a motor.

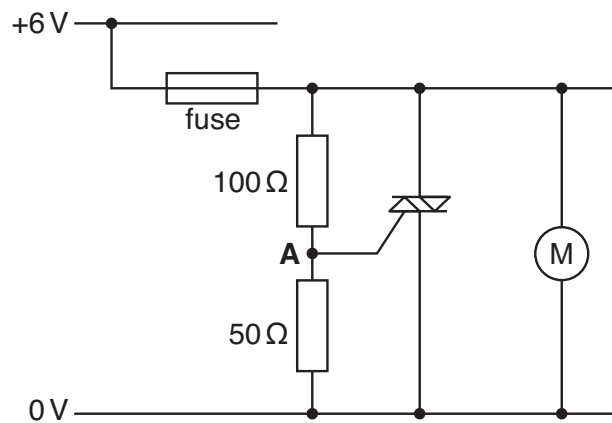


Fig. 3.2

(i) The power supply is operating normally.

Calculate the voltage at point **A** in Fig. 3.2 if the triac is not conducting.

voltage = V [3]

(ii) The power supply develops a fault and its output voltage rises.

The triac begins to conduct when point **A** reaches 2.5V.

Calculate the voltage of the power supply when this occurs.

voltage = V [2]

(iii) Explain how the triac and fuse protect the motor as the power supply voltage rises.

.....

 [3]

4 Fig. 4.1 shows a circuit for heating an animal house.

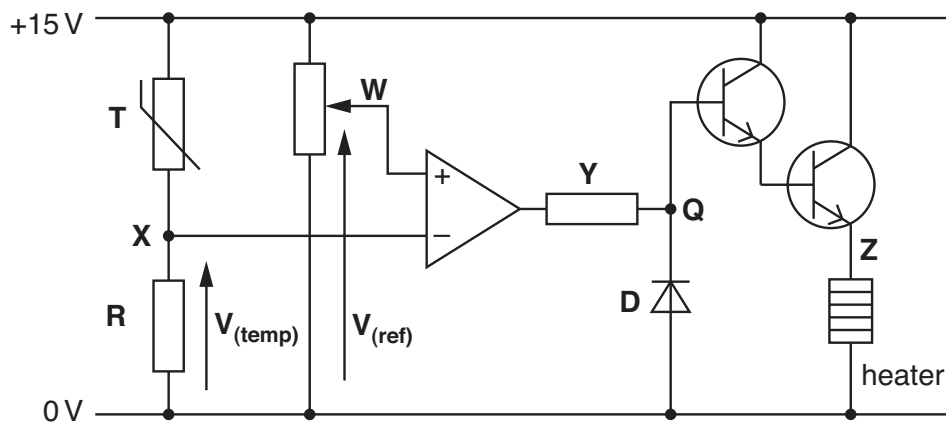


Fig. 4.1

(a) (i) State the name of component **T**.

T [1]

(ii) Explain why the voltage at point **X** rises as the temperature increases.

.....

 [3]

(iii) The component **T** in Fig. 4.1 is placed near the heater.

Describe and explain the changes within the circuit following a sudden increase in the voltage $V_{(ref)}$.

.....

 [5]

(iv) State and explain the voltage at point **Q** when the op amp saturates negatively.

.....

 [2]

- (b) An improved version of the temperature control circuit is shown in block diagram form in Fig. 4.2.

The output of the Difference Amplifier is $(X-W)$ when its inputs are W and X as shown.

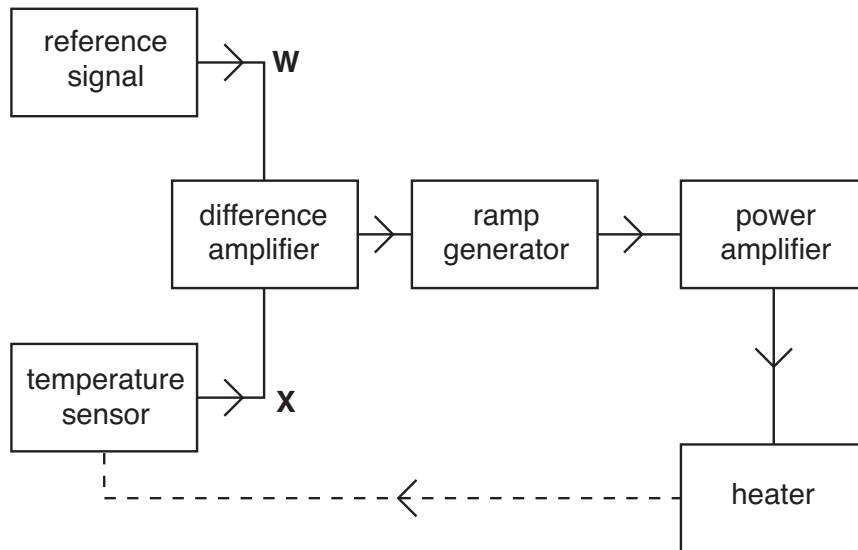


Fig. 4.2

- (i) Draw a circuit diagram of a ramp generator.

Component values are not required.

[3]

- (ii) Explain why the presence of a ramp generator in the temperature control circuit will lead to an improvement in the way that the circuit functions compared with that in Fig. 4.1.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

[4]

5 (a) State the function of the following in the operation of a microprocessor.

(i) Clock.

.....
..... [1]

(ii) Address Bus.

.....
..... [1]

(iii) Data Bus.

.....
..... [1]

(b) Binary and hexadecimal are commonly used to represent data and instructions.

Convert the following:

(i) 1010 1111 from binary to hexadecimal.

..... [1]

(ii) D 4 from hexadecimal to binary.

..... [1]

- (c) A register can be used to store a single word.

D-type flip-flops can be arranged to create a register.

Complete the circuit diagram of Fig. 5.1 for a 4-bit register.

Label the inputs and outputs.

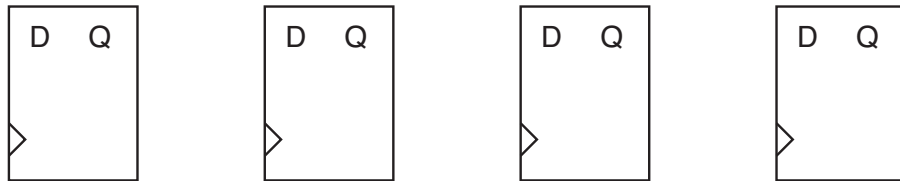


Fig. 5.1

[3]

- 6 (a) A small read only memory was created from components shown in Fig. 6.1.

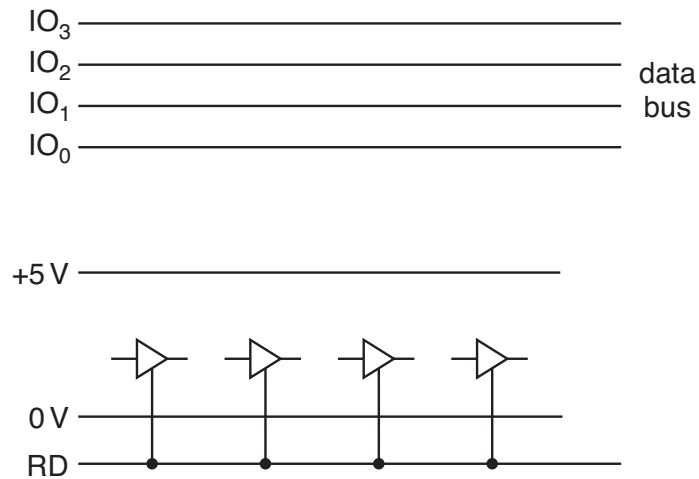


Fig. 6.1

- (i) Complete Fig. 6.1 to show how the memory would **permanently** store the binary value 0110. [2]

- (ii) State how this binary value would be placed on the data bus.

..... [1]

- (b) A random access memory was created from components shown in Fig. 6.2.

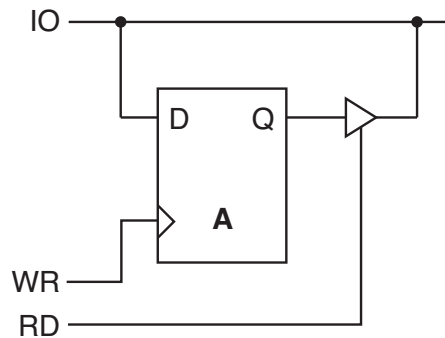


Fig. 6.2

- (i) State the name of component A.

A [1]

- (ii) The line marked IO shown in Fig. 6.2 is said to be *bi-directional*.

State what is meant by *bi-directional*.

..... [1]

(c) A 4-bit RAM is shown in Fig. 6.3.

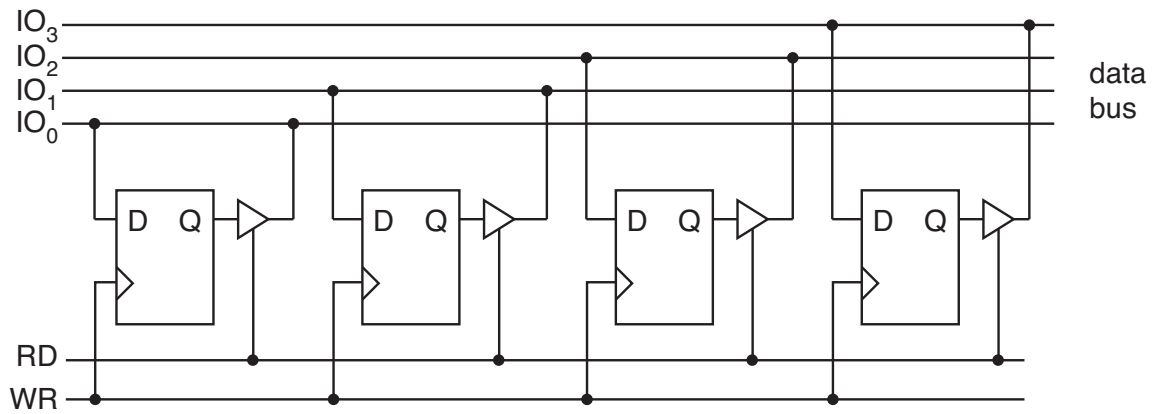


Fig. 6.3

Explain

(i) how a 4-bit word would be saved from the data bus.

.....

 [2]

(ii) how a 4-bit word stored in the RAM would be placed on the data bus.

.....

 [2]

7 Fig. 7.1 shows a microprocessor system designed to operate as a word game.

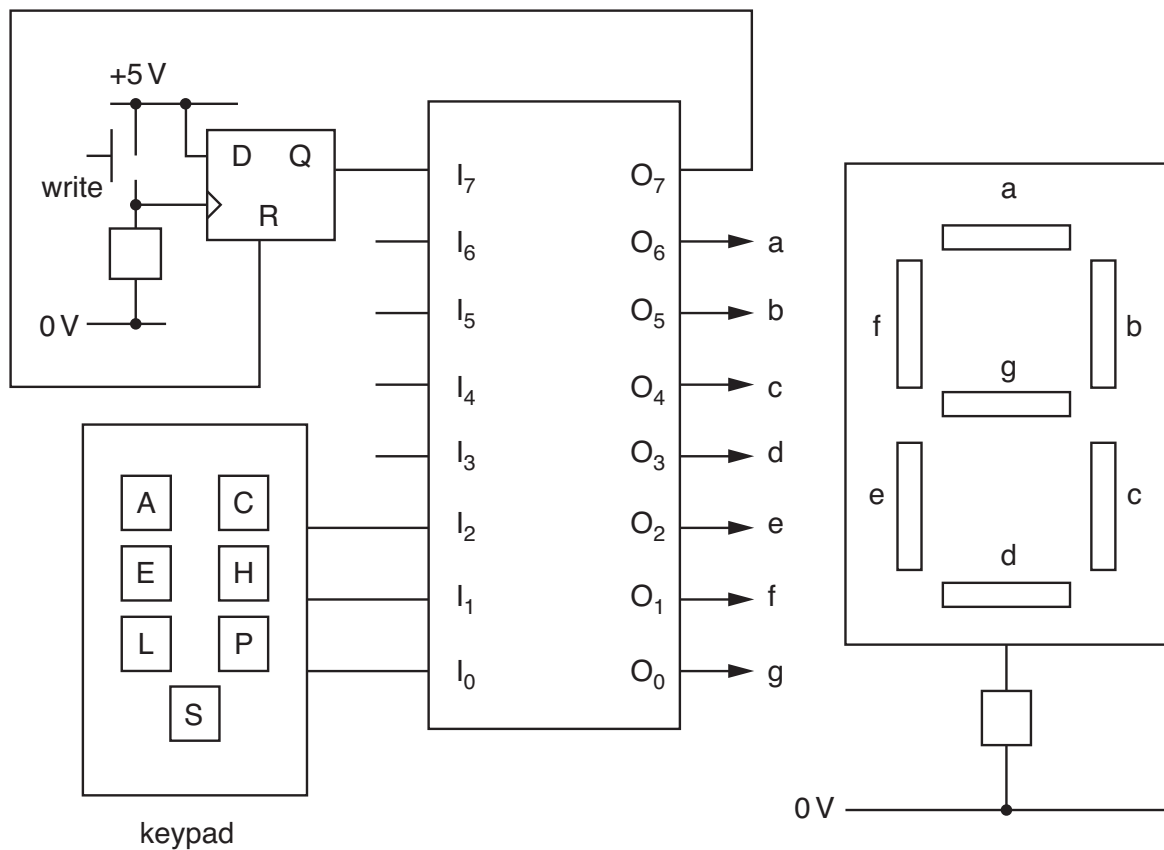


Fig. 7.1

The player of the game has a keypad with seven keys. Each key represents a capital letter which can be displayed on the 7-segment display. The object of the game is to compose as many words as possible using only the seven letters on the keypad.

To play the game, the player selects the first letter of the new word and pushes the appropriate key for a few moments before releasing it. They then press the next letter of their word and again release the key. This continues for all the letters in their word. They then press the "write" button, after which the microprocessor will display the word on the 7-segment display in the letter order the player originally set. At the end of the sequential letter display, the microprocessor will return to its starting state for the player to compose another word.

- (a) The 7-segment codes of the seven letters are stored in a look-up table at addresses A1 to A7. These addresses contain codes which will both reset the D-type and illuminate a particular letter on the display. Complete the table below to show the contents of this look-up table.

Address	Reset + Letter	Contents
A1	1 + A	F7
A2	1 + C	CE
A3	1 + E	CF
A4	1 + H	
A5	1 + L	
A6	1 + P	
A7	1 + S	

[4]

- (b) When no key is being pushed, the keypad output is 000. When any one of the keys is pressed, the keypad outputs a 3-bit word which is not 000.

The programme segment starting at address 00 has to perform the following function:

Blank the 7 segment display
 Store 00 into address DD
 Test to see if any key on the keypad has been pressed
 If this has occurred go to address 14

In the space below write the appropriate coding for this programme segment using the instruction set provided.

Address	Contents
00
.....
.....
.....
.....
.....

[7]

(c) The program uses the following addresses.

Address DD is used to store the **number** of letters in the player's word.

Address EE is used as a temporary store for the 7-segment code of the letter.

Each time a key is pressed on the key pad, the following code is executed.

Using the instruction set provided explain the function of each programme line and summarise the effect of this section.

Address	Contents	Explanation
14	C6 A0
16	6F
17	7E
18	32 EE
1A	3A DD
1C	C6 B0
1E	6F
1F	3A EE
21	77
22	3A DD
24	C6 01
26	32 DD
28	3A EF
2A	E6 07
2C	C2 28
2E	C3 06

Summary

.....

.....

[10]

- (d) The final part of the programme includes a segment starting at address 46 to provide a time delay.

In the space below write the appropriate addresses and coding for this segment using the instruction set provided.

Address	Contents
46	

[3]

Quality of Written Communication [3]

END OF QUESTION PAPER

PLEASE DO NOT WRITE ON THIS PAGE



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations, is given to all schools that receive assessment material and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.