

## ELECTRIC FIELD & CAPACITOR MODEL SOLUTION

JAN 2003

$$\begin{aligned} 1. \text{ Charge, } Q_1 &= CV \\ &= 2.0\mu \times 50 \\ &= \underline{1.0 \times 10^{-4} \text{ C}} \end{aligned}$$

$$\begin{aligned} \text{Charge, } Q_2 &= CV \\ &= 3.0\mu \times 100 \\ &= \underline{3.0 \times 10^{-4} \text{ C}} \end{aligned}$$

$$\begin{aligned} \text{Energy, } W_1 &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} \times 2.0\mu \times 50^2 \\ &= \underline{2.5 \times 10^{-3} \text{ J}} \end{aligned}$$

$$\begin{aligned} \text{Energy, } W_2 &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} \times 3.0\mu \times 100^2 \\ &= \underline{1.5 \times 10^{-2} \text{ J}} \end{aligned}$$

$$\begin{aligned} C_{\text{total}} &= C_1 + C_2 \\ &= [2.0 + 3.0] \mu\text{F} \\ &= \underline{5.0 \mu\text{F}} \end{aligned}$$

$$\begin{aligned} \text{Total charge} \\ &= 1.0 \times 10^{-4} + 3.0 \times 10^{-4} \\ &= \underline{4.0 \times 10^{-4} \text{ C}} \end{aligned}$$

$$\begin{aligned} E_{\text{total}} &= \frac{1}{2} [Q^2 / C] \\ &= \frac{1}{2} \{ [4.0 \times 10^{-4}]^2 / [5.0 \times 10^{-6}] \} \\ &= \underline{0.016 \text{ J}} \end{aligned}$$

There's loss of stored energy when the capacitors are connected due to gain in internal energy during electrical work

**OR**

There's loss of stored energy when the capacitors are connected because of the heating in the wires resulting in the dissipation of thermal heat.

**OR**

There's loss of stored energy when the capacitors are connected due to work done in charges

**OR**

There's loss of stored energy when the capacitors are connected because energy is needed to overcome resistance in wires.

**PREPARED BY MR.DERYK NG**  
**UCSI UNIVERSITY**  
**A LEVEL ACADEMY**