

- 1 (a) Complete the truth table for a NOR gate.

B	A	Q
0	0	
0	1	
1	0	
1	1	

[1]

- (b) The circuit of Fig. 1.1 contains AND and NOR gates.

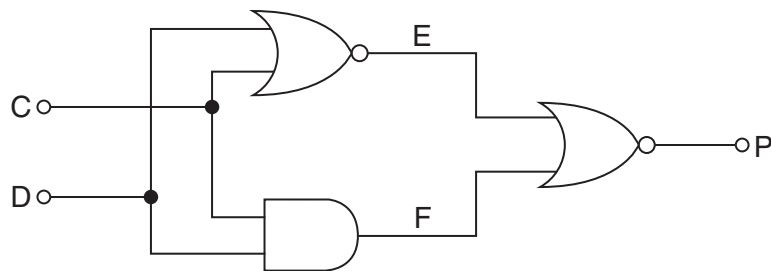


Fig. 1.1

- (i) Complete the truth table for the circuit.

C	D	E	F	P
0	0			
0	1			
1	1			

[4]

- (ii) The circuit of Fig. 1.1 can be replaced by a single logic gate.
State the name of the logic gate.

.....[1]

- (c) (i) On Fig. 1.2, draw a circuit to show how the AND gate of Fig. 1.1 can be made from three NOR gates.

C ○ —————

————— ○ F

D ○ —————

[3]

Fig. 1.2

- (ii) Use a truth table, with columns for the outputs of each NOR gate, to show that your circuit behaves like an AND gate.

[4]

- 2 Fig. 2.1 is a block diagram for a low voltage power supply.



Fig. 2.1

- (a) Describe the **function** of these blocks.

transformer

.....

rectifier

.....

smoother

.....[6]

- (b) In the space below, draw a circuit diagram for a power supply made from a transformer, a single diode and a capacitor.
Label the output terminals, indicating their polarity.

[5]

- (c) The power supply operates from the 230V, 50Hz mains electricity supply and delivers a current of 250 mA into a load of $27\ \Omega$.


- (i) Show that the voltage across the load is about 7V.

[3]

- (ii) Do a calculation to show that the capacitor is charged up at intervals of 20 ms.

[2]

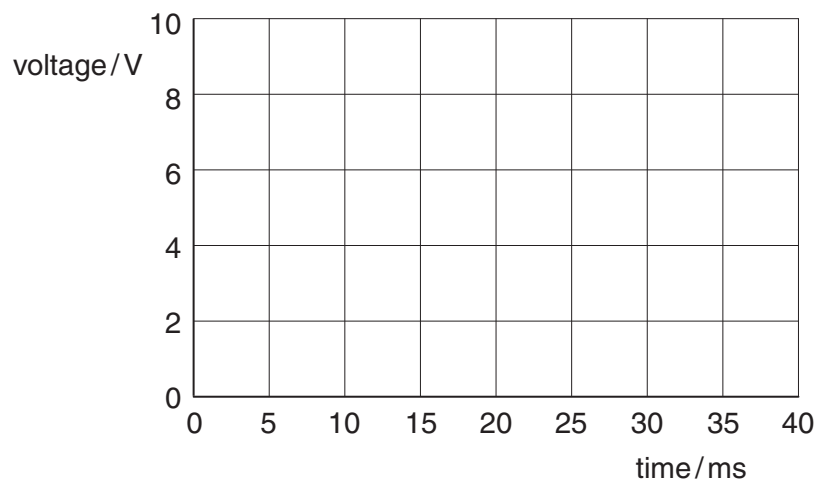- (iii) A 27Ω load gives a ripple voltage of 0.5V. On the axes of Fig. 2.2, sketch a graph to show how the voltage across the 27Ω load changes with time.



[4]

Fig. 2.2

- (iv) Calculate a value for the capacitor which will give a ripple of 0.5V at a current of 250mA.

capacitor = μF [3]

- 3 Fig. 3.1 shows how a zener diode can generate a steady 5V from a 12V car battery.

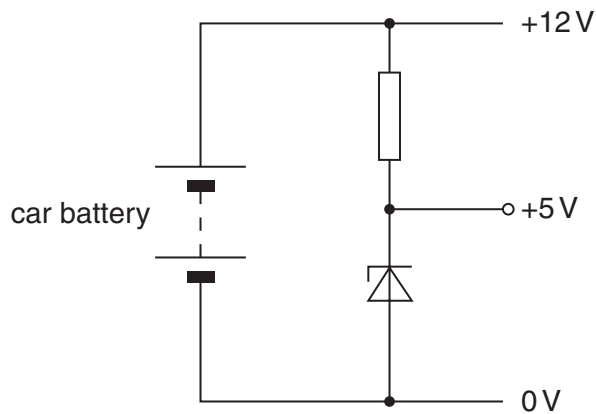


Fig. 3.1

- (a) The zener diode has been connected in reverse bias.

- (i) Draw an arrow on Fig. 3.1 to show the direction of the current in the zener diode. [1]
- (ii) Describe how the current in the reverse biased zener diode depends on the voltage across it.

.....

.....

.....

.....[3]

- (b) The zener diode is rated at 5V, 1.2W.

- (i) Show that the maximum safe current in the diode is about 250 mA.

[3]

- (ii) How does exceeding this current damage the zener diode?

.....

.....[1]

(c) The resistor in Fig. 3.1 is chosen to limit the current in the diode to a safe value of 150 mA.

- (i) Draw on Fig. 3.1 to show how a voltmeter should be connected to measure the voltage drop across the resistor.

[2]

- (ii) State the voltage drop across the resistor.


voltage drop = V [1]

- (iii) Calculate a value for the resistor which limits the diode current to 150 mA.

resistance = Ω [3]

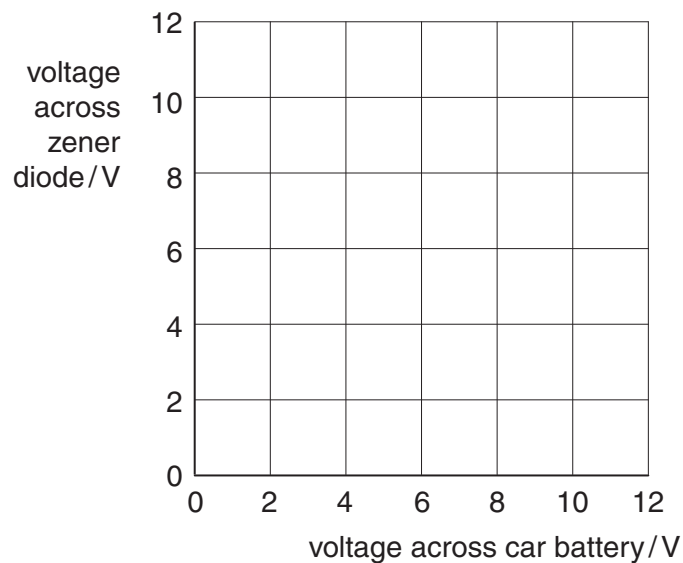- (d) The voltage across the car battery can vary from 0V to +12V, depending on its state of charge.

Draw on Fig. 3.2 to show how the voltage across the zener diode depends on the voltage across the car battery.



[2]

Fig. 3.2

4 Fig. 4.1 shows a bistable made from a pair of NAND gates.

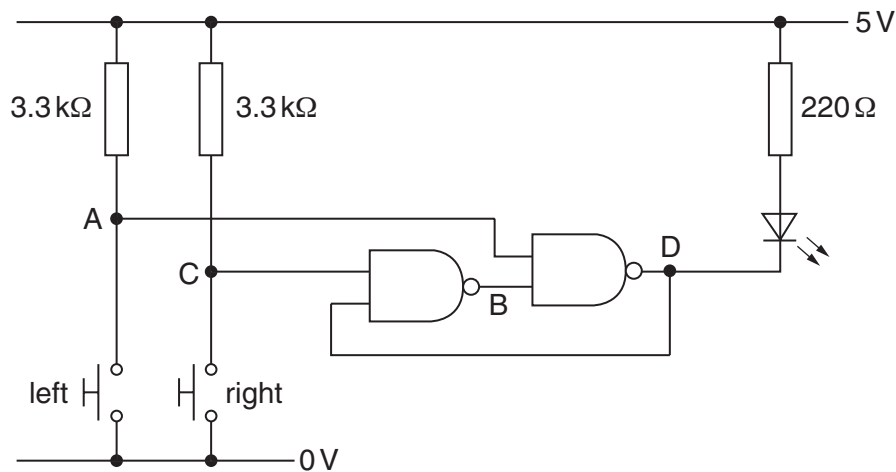


Fig. 4.1

(a) The state of the output D is shown with a green LED.

(i) Draw a ring around the LED. [1]

(ii) State the voltage drop across the LED when it is glowing.

voltage drop = V [1]

(iii) Calculate the current in the LED when it glows.

current = mA [3]

(b) The point labelled A in Fig. 4.1 is high when the left-hand switch is open and low when the left-hand switch is closed. Explain why.

.....

 [2]

(c) (i) Complete the truth table for a NAND gate.

A	B	D


[2]

(ii) Explain why pressing the left-hand switch stops the LED from glowing.

.....

[3]

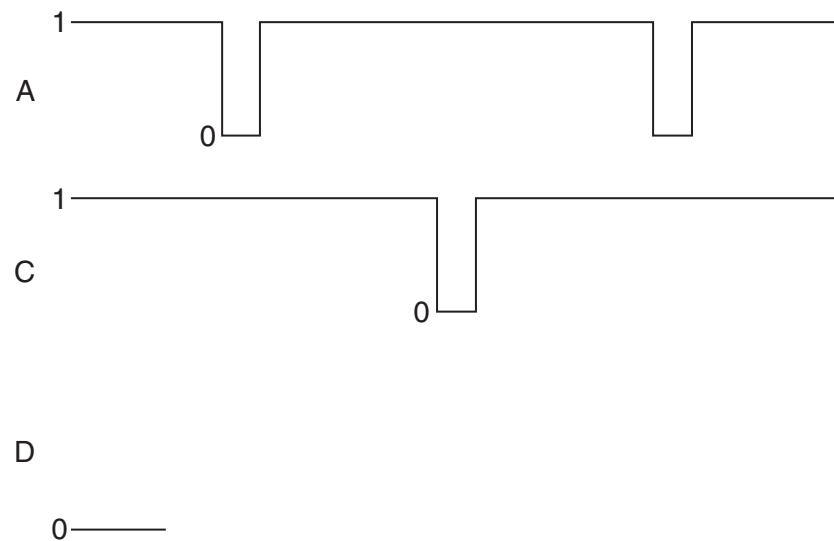(d) Complete the timing diagram of Fig. 4.2 for the bistable shown in Fig. 4.1.



[3]

Fig. 4.2

- 5 The circuit of Fig. 5.1 switches on the motor when the thermistor gets too hot.

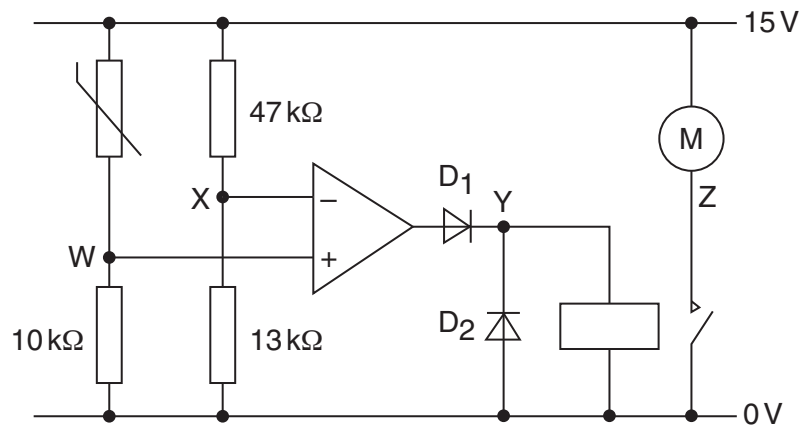


Fig. 5.1

- (a) Show that point X is at a constant voltage of about +3V.

[3]

- (b) (i) Draw a ring around the thermistor.

[1]

- (ii) Explain why the voltage at point W rises as the temperature of the thermistor rises.

.....

.....

.....

.....

.....[3]

- (iii) Explain why the motor turns on when the thermistor gets too hot.

.....

.....

.....

.....

.....

.....[5]

- (c) Suggest why the circuit contains a relay.

.....

.....[1]

- (d) The circuit of Fig. 5.1 contains two silicon diodes.

- (i) Describe the electrical properties of a silicon diode.

.....

.....

.....

.....[3]

- (ii) Explain why the diodes have been included in the circuit.

D_1

.....

.....

D_2

.....

.....[4]

6 The circuit of Fig. 6.1 includes some logic gates and a D-type flip-flop.

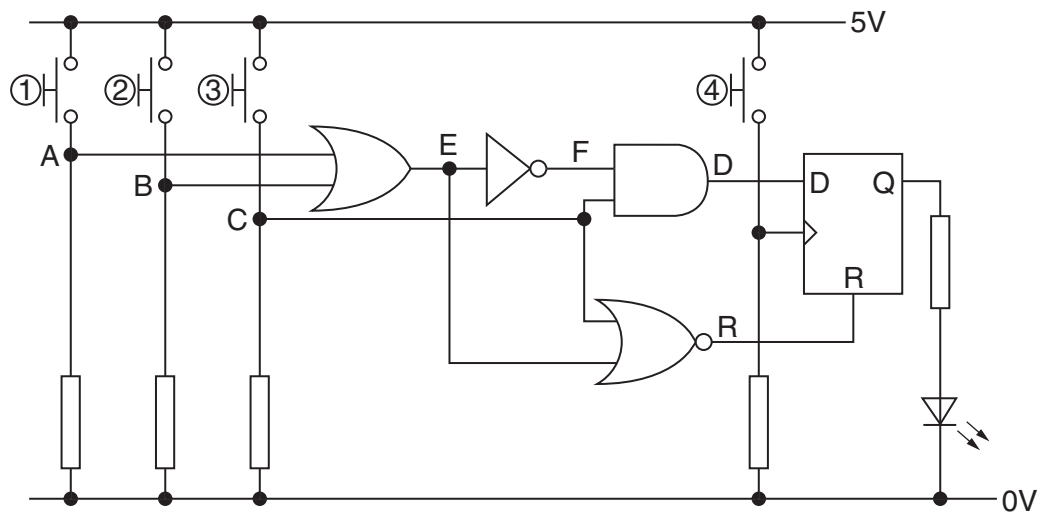


Fig. 6.1

(a) Complete the truth table.

A	B	C	E	F	D	R
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

[7]

(b) Explain why the LED does **not** glow when all four switches are open.

.....

.....

.....

.....[3]

(c) State and explain how the switches must be pressed to make the LED glow.

.....

.....

.....

.....

.....

.....[4]

- 7 The circuit of Fig. 7.1 contains an op-amp arranged as an amplifier.

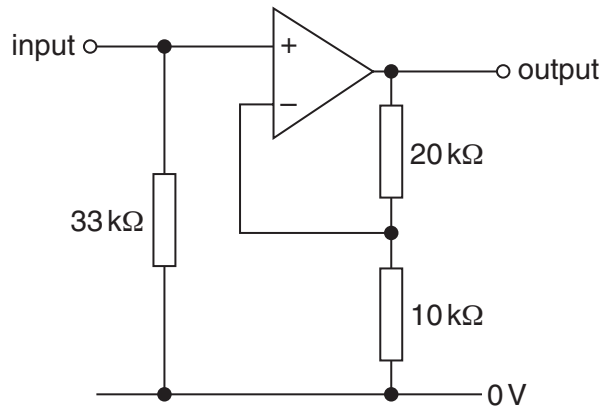


Fig. 7.1

- (a) Three types of amplifier are shown below.

inverting

non-inverting

voltage follower


Draw a ring around the type of amplifier shown in Fig. 7.1.

[1]

- (b) Calculate the voltage gain of the amplifier.

voltage gain = [3]

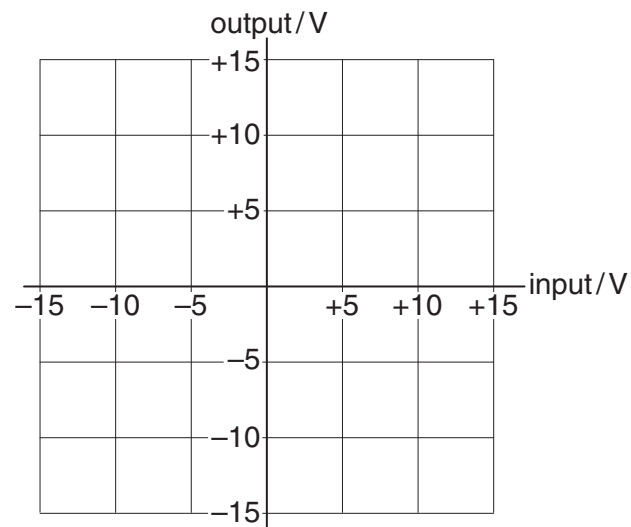- (c) On Fig. 7.2, show how the voltage at the output changes as the voltage at the input is swept from -15V to $+15\text{V}$.



[3]

Fig. 7.2

- 8 The circuit of Fig. 8.1 includes a buzzer which makes a noise.

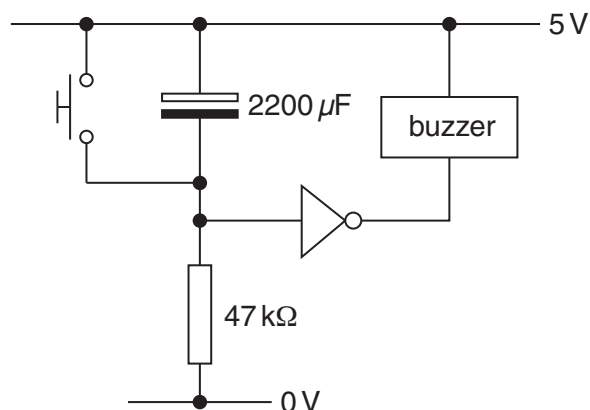


Fig. 8.1

- (a) Calculate the time constant of the RC network.

time constant = s [3]

- (b) The sentences (A to I) describe what happens when the switch is pressed and then released. They are in the wrong order.

- A The buzzer makes a noise.
- B The buzzer stops making a noise.
- C The input of the NOT gate goes low.
- D The input of the NOT gate goes high.
- E The output of the NOT gate goes low.
- F The output of the NOT gate goes high.
- G The capacitor discharges quickly through the pressed switch.
- H The capacitor charges up slowly through the resistor.
- I The switch is released.

Complete the boxes to show the correct order.

G → → → → **I** → → → → [6]

Quality of Written Communication [3]