

Surname						Other Names					
Centre Number						Candidate Number					
Candidate Signature											

For Examiner's Use

General Certificate of Secondary Education
June 2008

**DESIGN AND TECHNOLOGY
(ELECTRONIC PRODUCTS) (SHORT COURSE)
Written Paper
Foundation Tier**

3551/F

F



Monday 9 June 2008 1.30 pm to 3.00 pm

<p>For this paper you must have:</p> <ul style="list-style-type: none"> a pen, a pencil, a ruler, an eraser and a pencil sharpener. <p>You may use a calculator.</p>
--

Time allowed: 1 hour 30 minutes

Instructions

- Use black ink or black ball-point pen. Use pencil only for drawing.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Answers written in margins or on blank pages will not be marked.
- Do all rough work in this book. Cross through any work you do not want to be marked.
- Show the working of your calculations.

Information

- The maximum mark for this paper is 100.
- The marks for questions are shown in brackets.
- A list of formulae and other information, which you may wish to use in your answers, is provided on pages 2 and 3.
- You are reminded of the need for good English and clear presentation in your answers.

For Examiner's Use			
Question	Mark	Question	Mark
1		5	
2		6	
3		7	
4		8	
Total (Column 1) →			
Total (Column 2) →			
TOTAL			
Examiner's Initials			


You may need to use one or more of the following formulae when answering questions which include calculations.

Potential Difference Potential Difference = Current \times Resistance ($V = I \times R$)

Series Resistors $R_{\text{total}} = R_1 + R_2 + R_3 \text{ etc}$

Electrical Power Electrical Power = Current \times Potential Difference ($P = I \times V$)

Potential Divider

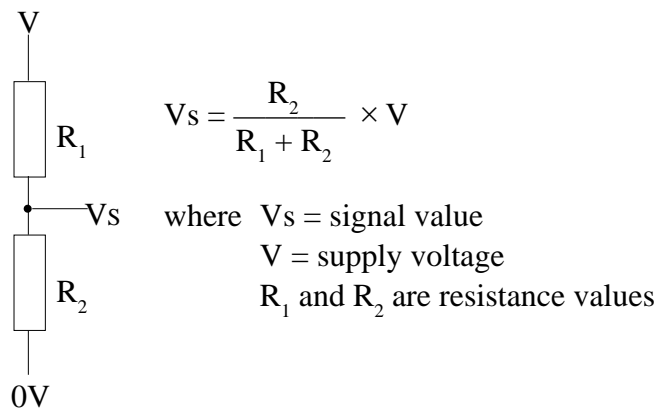

Time Constant Time Constant \approx Resistance \times Capacitance ($T \approx R \times C$)

Astable
Frequency for 555 $f = \frac{1.44}{(R_1 + 2R_2) \times C}$

Pulse duration $= \frac{1}{\text{frequency}}$

You may need to use the following information when answering some of the questions.

Capacitor series 10, 22, 47

Resistor Colour Code

Colour	Band 1	Band 2	Band 3 (No. of 0s)	Band 4 (Tolerance)
Black	0	0	None	
Brown	1	1	0	
Red	2	2	00	
Orange	3	3	000	
Yellow	4	4	0000	
Green	5	5	00000	
Blue	6	6	000000	
Violet	7	7	–	
Grey	8	8	–	
White	9	9	–	
				Gold = 5%
				Silver = 10%

Turn over for the first question

Turn over ►

Answer **all** questions in the spaces provided.

- 1** This question is about research.



A student is designing a road safety product to be positioned on the ground behind a car to warn other motorists that a car has broken down.

The product must be able to be seen in poor light conditions.

- 1** (a) Identify **two** useful features for the product giving a reason for each one.

An example has been done for you.

e.g. The product needs to be stable so that it will not be blown over.

Feature 1

.....

.....

.....

(2 marks)

Feature 2

.....

.....

.....

(2 marks)

- 1 (b)** Describe **two** different methods of finding out information about existing road safety products.

Method 1.....

.....

.....

.....

(2 marks)

Method 2.....

.....

.....

.....

(2 marks)

Turn over for the next question

8

Turn over ►

2 This question is about designing the case of the product.

2 (a) In the box below sketch a design idea for the road safety product to be positioned on the ground behind a car.

This should show the following aspects:

- the specific materials which would be used.
- how it is made stable whilst standing on the ground.
- how it is suitable for storing in the car.

(6 marks)

2 (b) Using notes and sketches, develop your design for the case of the road safety product, to contain a circuit with six LEDs. Your design must include the following aspects:

- the position of the six LEDs.
- how the LEDs are held securely in place.
- the position of an off/on switch and how it is fitted in the case.
- access to the inside of the case.

(10 marks)

Quality of communication (3 marks)

Turn over ►

3 This question is about components and systems.

As part of their research the student investigates different components.

3 (a) Look at the electronic component symbols below:

A	B	C	D	E	F

Which of the symbols above correspond with the names listed below? Indicate by writing the symbol letter in the box provided. An example has been done for you.

Component Name

e.g. Thermistor

E

(i) Bulb/Lamp

(1 mark)

(ii) Fixed Resistor

(1 mark)

(iii) Buzzer

(1 mark)

(iv) Transistor

(1 mark)

3 (b) Name an electronic component which best fits each of the descriptions given below:

3 (b) (i) emits light when a current flows from the anode to the cathode.

.....
(1 mark)

3 (b) (ii) its resistance decreases as the temperature increases.

.....
(1 mark)


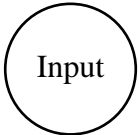


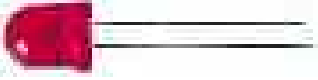

3 (b) (iii) a wire melts when too large a current flows.

.....
(1 mark)

3 (b) (iv) it has three connections called anode, cathode and gate.

.....
(1 mark)

- 3 (c) Identify in which part of the system (input, process or output) the components shown in the table below are usually found. An example is done for you.

	Component	Input	Process	Output
e.g.			Process	Output
(i)		Input	Process	Output
(ii)		Input	Process	Output
(iii)		Input	Process	Output
(iv)		Input	Process	Output

Images reproduced by kind permission of Rapid Electronics Ltd www.rapidonline.com

(4 marks)

12

Turn over for the next question

Turn over ►

4 This question is about components and circuits.

4 (a) A diode is an example of a polarised component.

Explain what is meant by the term 'polarised component'.

.....

.....


.....

.....

(2 marks)

4 (b) Complete **Figure 1** by naming the leads of the diode symbol.

Figure 1

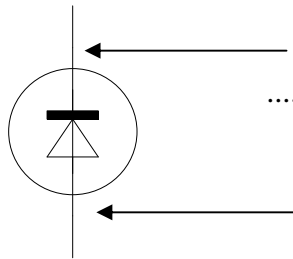


.....

.....

(2 marks)

4 (c) Draw on **Figure 2** the means of indicating the positive and negative leads of the diode.

Figure 2

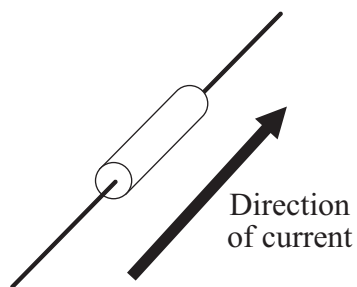


Direction
of current

(1 mark)

- 4 (d) **Figure 3** shows a basic thyristor latching circuit.

Figure 3

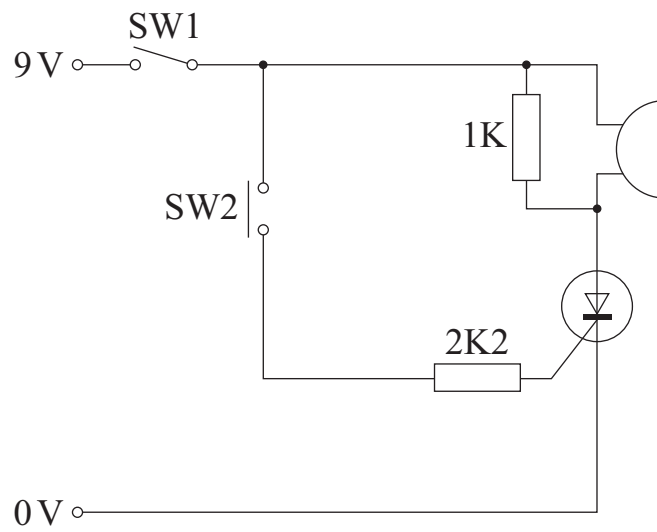

Briefly describe how the circuit works.

.....

.....

.....

.....

.....

.....

.....

.....

(4 marks)

Turn over for the next question


5 This question is about an astable circuit.

During their research a student finds a 555 IC astable and decides to connect six LEDs to the output:

- three are sinking (on when the astable output is low).
- three are sourcing (on when the astable output is high).

An incomplete circuit diagram is shown in **Figure 4**.

Figure 4

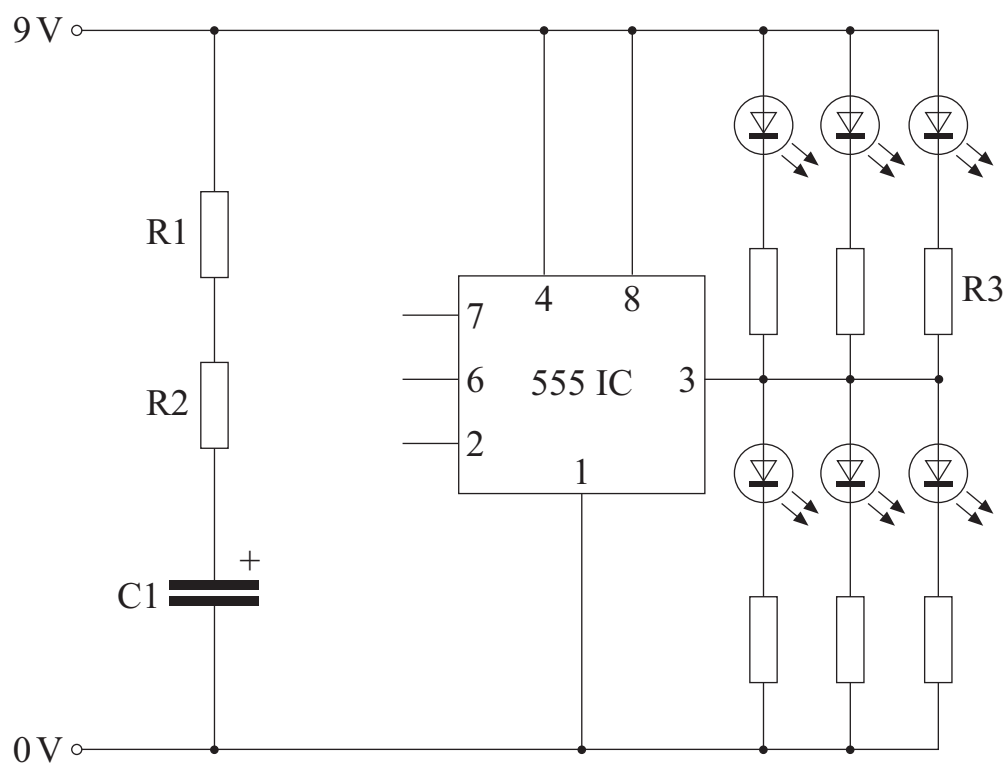

5 (a) Complete the circuit diagram in **Figure 4** by drawing the connections to make it work as an astable.

(3 marks)

- 5 (b) Describe how the circuit could be changed to make the frequency of the output of the astable adjustable after the circuit is complete.

.....

.....

.....

.....

(2 marks)

- 5 (c) Each LED has a current limiting resistor connected in series.

Calculate the value of the resistor R3 in **Figure 4** if the LED requires 2V and 20mA to be at full brightness.

Formula:

Working:

Answer (with units):
(5 marks)

- 5 (d) When the circuit in **Figure 4** was tested the LEDs in the top half were brighter than the LEDs in the bottom half.

Explain why this has happened and suggest a suitable modification to the circuit.

Explanation

.....

.....

.....

(2 marks)

Modification

.....

.....

.....

(2 marks)

Turn over for the next question


6 This question is about testing circuits.

Circuits can be tested using either a breadboard (prototype board) or using a computer simulator.

6 (a) **Figure 5** shows a diagram of a common breadboard.

Show clearly how the different holes are connected together.

Figure 5

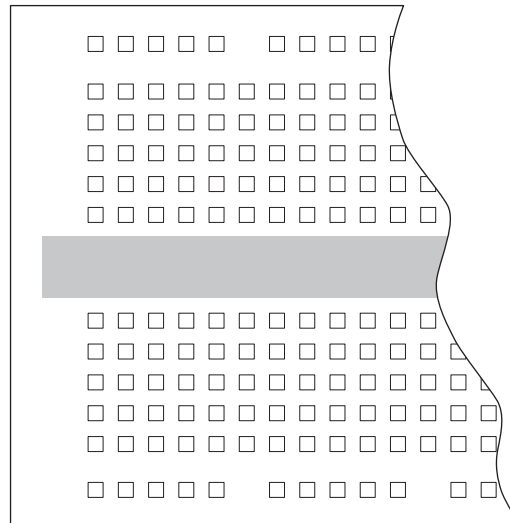

(4 marks)

6 (b) What is the purpose of the shaded area shown in **Figure 5**?

.....

.....

.....

.....

(2 marks)

6 (c) State **two** advantages and **two** disadvantages of using a breadboard to test a circuit idea.

Prototyping using breadboards	
Advantages	Disadvantages
1.	1.
2.	2.

(4 marks)

- 6** (d) Give **three** reasons a designer would use CAD software to design a circuit board layout.

Reason 1

.....

.....

.....

(2 marks)

Reason 2

.....

.....

.....

(2 marks)

Reason 3

.....

.....

.....

(2 marks)

Turn over for the next question

- 7 This question is about the manufacture of the case for a product.
- 7 (a) In the box below use notes and sketches to describe the main steps in producing a mould/former to be used in the vacuum forming process. State the materials you would use and the important details of the mould.

(7 marks)

- 7 (b) If it did not work correctly what change might be required to be made to the mould?

.....

.....

.....

.....

(2 marks)

- 7 (c) Name a suitable plastic which could be shaped using the vacuum forming process.

.....

(1 mark)

Turn over for the next question

10

Turn over ►

8 This question is about Social and Environmental issues.

The rapid expansion of electronics has greatly improved road safety.

8 (a) Describe the impact on road safety of the use of Speed Cameras.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

(6 marks)

- 8 A lorry, as shown in **Figure 6**, uses mirrors to allow the driver to have a clear vision of their position in relation to other road users.

Figure 6

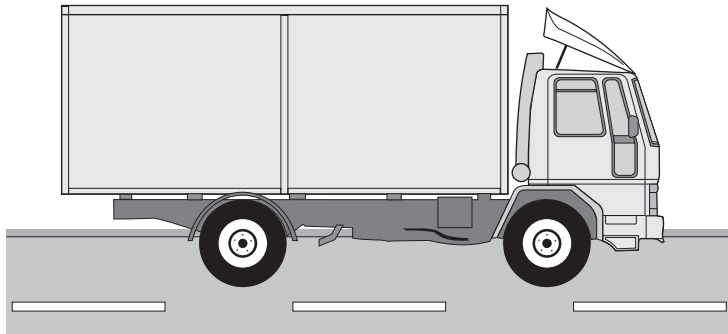

- 8 (b) Describe ways in which electronic products could be used to improve the vision of the driver.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(6 marks)

END OF QUESTIONS

There are no questions printed on this page

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**