

Surname		Other Names	
Centre Number		Candidate Number	
Candidate Signature			

General Certificate of Secondary Education  
Spring 2004



**SCIENCE: DOUBLE AWARD (MODULAR)      346010**  
**PHYSICS (MODULAR)**  
**Electricity (Module 10)**

Wednesday 3 March 2004 Morning Session

**In addition to this paper you will require:**

- a black ball-point pen;
- an answer sheet.

You may use a calculator.

Time allowed: 30 minutes

**Instructions**

- Fill in the boxes at the top of this page.
- Check that your name, candidate number and centre number are printed on the separate answer sheet.
- Check that the separate answer sheet has the title “Electricity” printed on it.
- Attempt **one Tier only**, either the Foundation Tier or the Higher Tier.
- Make sure that you use the correct side of the separate answer sheet; the Foundation Tier is printed on one side and the Higher Tier on the other.
- Answer **all** the questions for the Tier you are attempting.
- Record your answers on the separate answer sheet only. Rough work may be done on the question paper.

**Instructions for recording answers**

- Use a **black ball-point pen**.

- For each answer **completely fill in the circle** as shown:
 

1	2	3	4
<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>

- Do **not** extend beyond the circles.

- If you want to change your answer, **you must** cross out your original answer, as shown:
 

1	2	3	4
<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>	<input checked="" type="radio"/>

- If you change your mind about an answer you have crossed out and now want to choose it, draw a ring around the cross as shown:
 

1	2	3	4
<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>	<input checked="" type="radio"/>

**Information**

- The maximum mark for this paper is 36.

**Advice**

- Do **not** choose more responses than you are asked to. You will lose marks if you do.
- Make sure that you hand in both your answer sheet and this question paper at the end of the test.
- If you start to answer on the wrong side of the answer sheet by mistake, make sure that you cross out **completely** the work that is not to be marked.

---

You must do **one Tier** only, **either** the Foundation Tier **or** the Higher Tier.  
The Higher Tier starts on page 16 of this booklet.

---

**FOUNDATION TIER**

**SECTION A**

Questions **ONE** to **FIVE**.

In these questions match the words in the list with the numbers.

Use **each** answer only **once**.

Mark your choices on the answer sheet.

---

**QUESTION ONE**

The table gives the symbols of some components used in circuit diagrams.



Match words from the list with the numbers **1–4** in the table.

**fuse**

**resistor**

**thermistor**

**variable resistor**

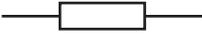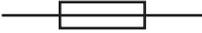Component	Symbol
1	
2	
3	
4	

**QUESTION TWO**

The diagram shows the inside of a 3-pin plug.


Match words from the list with the labels 1–4 on the diagram.

**cable grip**

**earth terminal**

**fuse**

**live terminal**

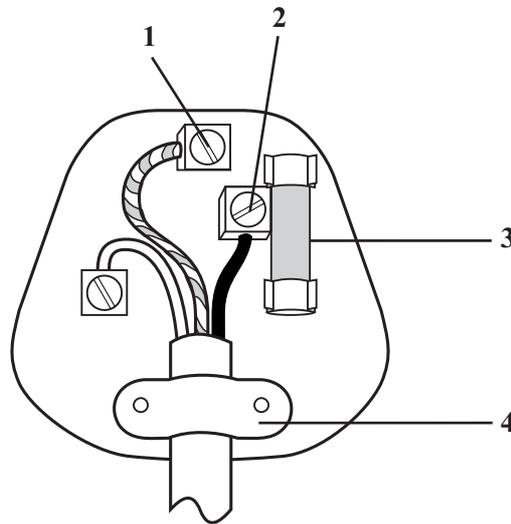

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

**QUESTION THREE**

The table is about the resistance of different components.

Match words from the list with the numbers 1–4 in the table.

**diode**

**filament lamp**


**LDR**

**thermistor**

<b>Component</b>	<b>Resistance</b>
<b>1</b>	its resistance decreases as light intensity increases
<b>2</b>	its resistance decreases as temperature increases
<b>3</b>	its resistance depends on the direction of the current flowing through it
<b>4</b>	its resistance increases as temperature increases

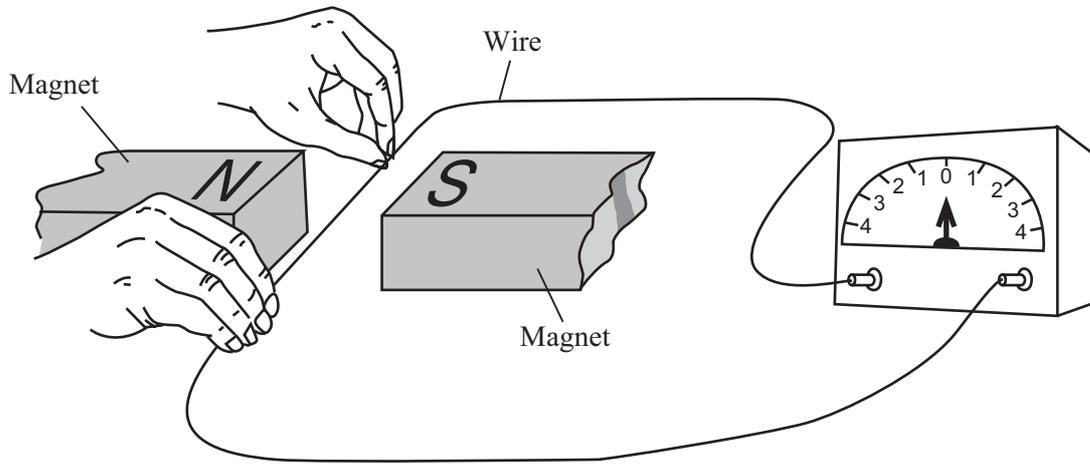**QUESTION FOUR**

The diagram shows a wire between the poles of a magnet.  
The apparatus is often used to show how electricity may be produced.



Match words from the list with the spaces **1–4** in the sentences.

**current**

**magnetic field**

**potential difference (voltage)**

**wire**

The . . . . **1** . . . . is moved downwards.

It passes through the . . . . **2** . . . . .


A . . . . **3** . . . . is induced between its ends.

If the wire is part of a circuit, a . . . . **4** . . . . flows.

**Turn over ►**


**QUESTION FIVE**

The diagram shows a circuit breaker.

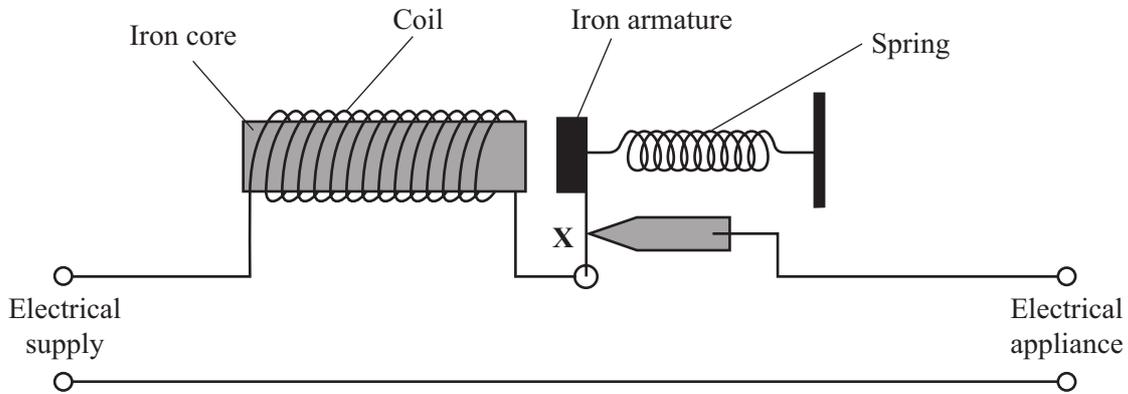

Explain how the circuit breaker works by matching statements, **J**, **K**, **L** or **M**, from the list with the boxes **1–4** in the flow diagram.

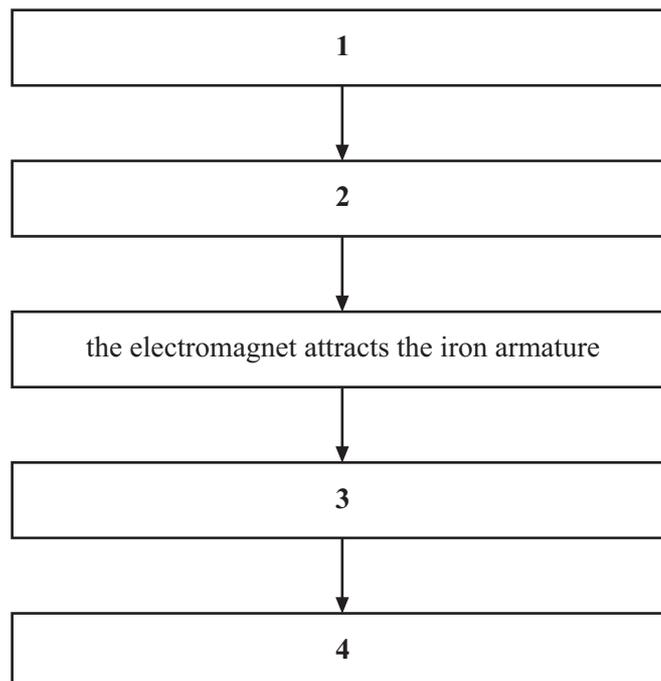- J** the contacts are broken at X
- K** the current in the circuit becomes too large
- L** the current stops flowing
- M** the iron core becomes a strong electromagnet



**NO QUESTIONS APPEAR ON THIS PAGE**

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

---


**SECTION B**Questions **SIX** and **SEVEN**.In these questions choose the best **two** answers.Do **not** choose more than two.Mark your choices on the answer sheet.

---

**QUESTION SIX**

A rod is rubbed with a cloth.

The rod becomes positively charged. It now attracts a small piece of paper.

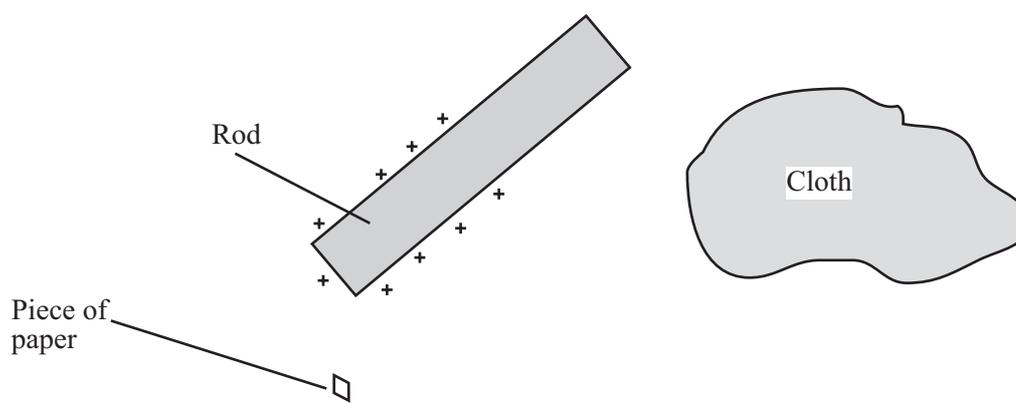Which **two** of the following statements are correct?**electrons were rubbed from the cloth on to the rod****electrons were rubbed from the rod on to the cloth****the cloth gained a negative charge****the cloth gained a positive charge****the piece of paper has a positive charge**

**QUESTION SEVEN**

Fuses are often used with electrical appliances.

Which **two** of the following statements, **P**, **Q**, **R**, **S** and **T** are **not** correct?

- P** if a fault causes too large a current to flow, the fuse causes the circuit to break
- Q** the fuse is connected to the neutral terminal in a plug
- R** the fuse should have a lower value than the current which flows through the appliance when it is working normally
- S** the wire in the fuse melts when it gets too hot
- T** when the wire in the fuse melts, the circuit is broken

**TURN OVER FOR THE NEXT QUESTION**

Turn over ►

**SECTION C**Questions **EIGHT** to **TEN**.

Each of these questions has four parts.





In each part choose only **one** answer.

Mark your choices on the answer sheet.

**QUESTION EIGHT**Four different power supplies, **P**, **Q**, **R** and **S**, are connected in turn to an oscilloscope.

The oscilloscope settings are not changed.

The traces are shown below.

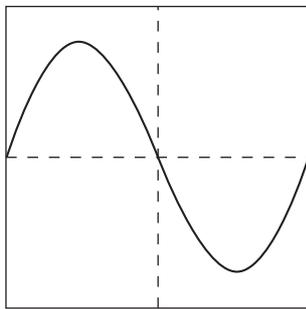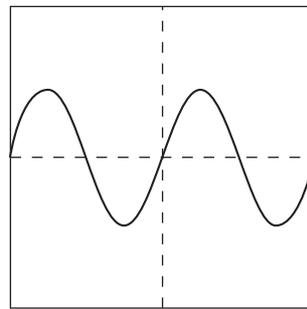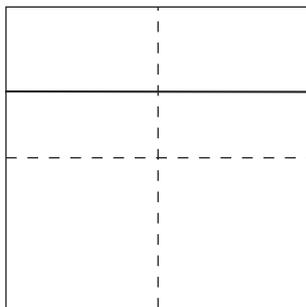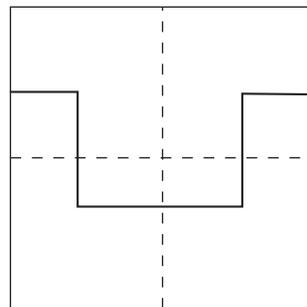
**P****Q****R****S****8.1** Which of the power supplies has the greatest peak voltage?

- A**    **P**
- B**    **Q**
- C**    **R**
- D**    **S**

8.2 Which trace shows a d.c. supply?

- A P
- B Q
- C R
- D S

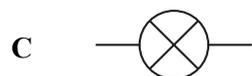8.3 Which component could produce, by itself, one of the traces shown?



8.4 Trace P represents a supply of frequency 60 Hz.

What is the frequency of supply Q?


- A 30 Hz
- B 60 Hz
- C 90 Hz
- D 120 Hz

**TURN OVER FOR THE NEXT QUESTION**

Turn over ►

**QUESTION NINE**

The diagram shows an electric circuit.

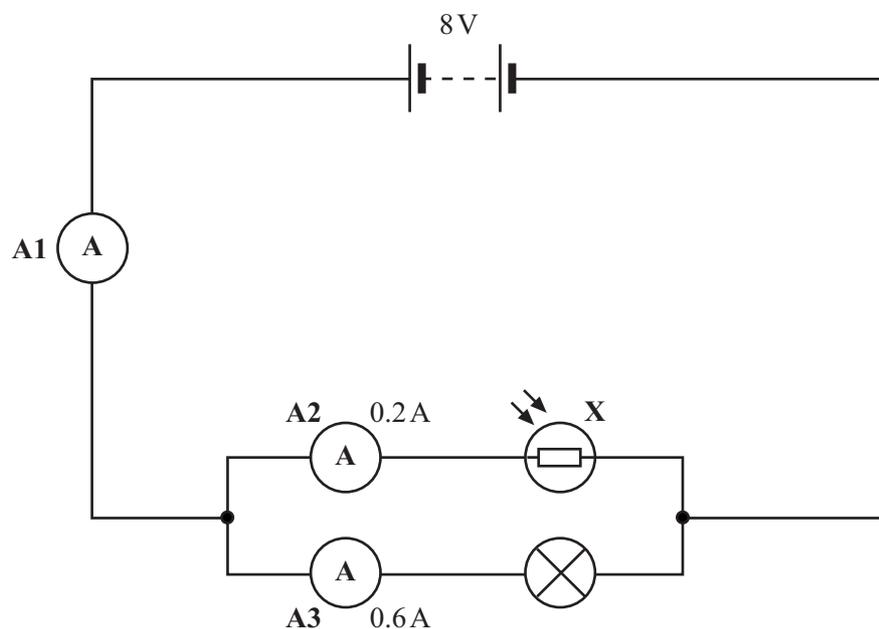

**9.1** What is the current flowing through ammeter A1?

- A 0.2 A
- B 0.4 A
- C 0.6 A
- D 0.8 A

**9.2** What is the potential difference (voltage) across X?

- A 4 V
- B 6 V
- C 8 V
- D 12 V

**9.3** What is the power of the lamp?

- A** 1.6 W
- B** 4.8 W
- C** 13.3 W
- D** 40.0 W

**9.4** What will happen to the reading on ammeter **A2** when the light intensity increases?

- A** It will fall to zero
- B** It will fall but not to zero
- C** It will stay the same
- D** It will increase

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

**QUESTION TEN**

The diagram shows how electricity is transferred from a power station to homes.



**10.1** The generator at the power station . . . . .

- A can have a rotating magnet or a rotating coil to produce a.c.
- B must have a coil rotating in a magnetic field to produce a.c.
- C must have a magnet rotating inside a coil to produce a.c.
- D produces only d.c.

**10.2** The devices labelled **X** and **Y** are . . . . .

- A circuit breakers.
- B motors.
- C transformers.
- D turbines.

**10.3** The device labelled **X** is used to . . . . .

- A change a.c. to d.c.
- B change d.c. to a.c.
- C decrease the voltage.
- D increase the voltage.

**10.4** The device labelled **Y** is used to . . . . .

- A** change a.c. to d.c.
- B** change d.c. to a.c.
- C** decrease the voltage.
- D** increase the voltage.

**END OF TEST**

You must do **one Tier** only, **either** the Foundation Tier **or** the Higher Tier.  
The Foundation Tier is earlier in this booklet.

## HIGHER TIER

### SECTION A

Questions **ONE** and **TWO**.


In these questions match the words in the list with the numbers.

Use **each** answer only **once**.

Mark your choices on the answer sheet.


### QUESTION ONE

The diagram shows a circuit breaker.

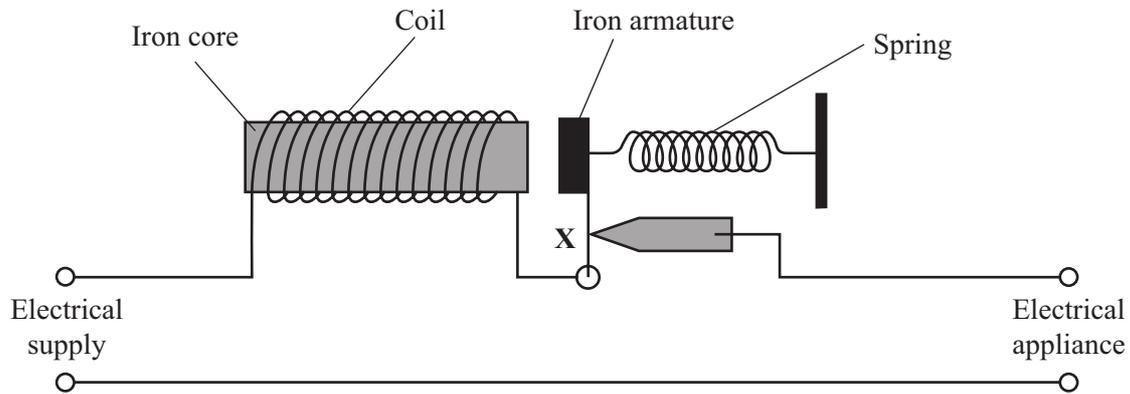

Explain how the circuit breaker works by matching statements, **J**, **K**, **L** or **M**, from the list with the boxes **1–4** in the flow diagram.

- J** the contacts are broken at X
- K** the current in the circuit becomes too large
- L** the current stops flowing
- M** the iron core becomes a strong electromagnet

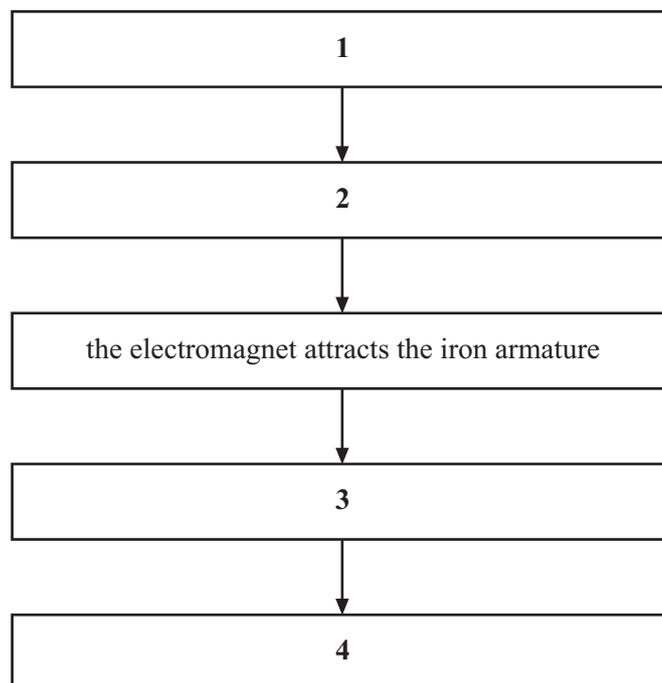**QUESTION TWO**

Match units from the list with the numbers 1–4 in the table.

**ampere**

**ohm**

**volt**

**watt**

<b>Unit</b>	<b>Definition</b>
<b>1</b>	one coulomb per second
<b>2</b>	one joule per coulomb
<b>3</b>	one volt per ampere
<b>4</b>	one volt $\times$ one ampere

**Turn over ►**

**SECTION B**Questions **THREE** and **FOUR**.In these questions choose the best **two** answers.Do **not** choose more than two.Mark your choices on the answer sheet.

---

**QUESTION THREE**


Fuses are often used with electrical appliances.

Which **two** of the following statements, **P**, **Q**, **R**, **S** or **T** are **not** correct?

- P** if a fault causes too large a current to flow, the fuse causes the circuit to break
- Q** the fuse is connected to the neutral terminal in a plug
- R** the wire in the fuse melts when it gets too hot
- S** the fuse should have a lower value than the current which flows through the appliance when it is working normally
- T** when the wire in the fuse melts, the circuit is broken

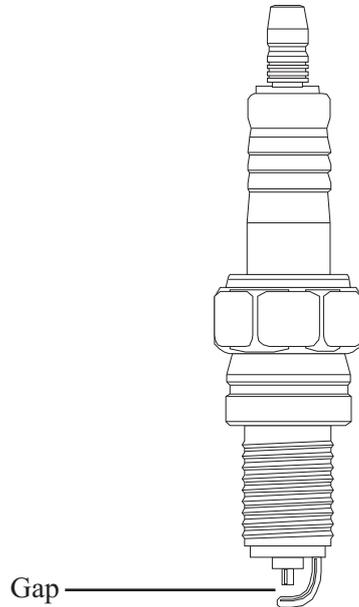**QUESTION FOUR**

The diagram shows a spark plug from a car.  
The plug produces a spark which ignites the fuel.



Which **two** of the following will make it easier for a spark to jump the gap?

- a bigger gap**
- a higher voltage**
- a smaller current**
- a smaller gap**
- a smaller voltage**

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

**SECTION C**Questions **FIVE** to **TEN**.

Each of these questions has four parts.





In each part choose only **one** answer.

Mark your choices on the answer sheet.

**QUESTION FIVE**Four different power supplies, **P**, **Q**, **R** and **S**, are connected in turn to an oscilloscope.

The oscilloscope settings are not changed.

The traces are shown below.

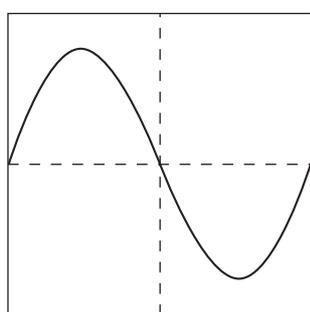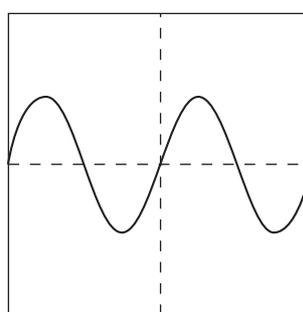
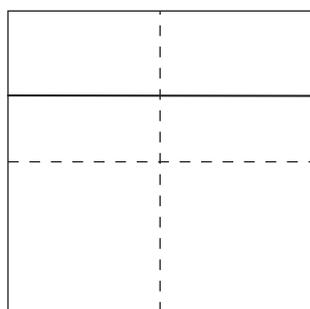
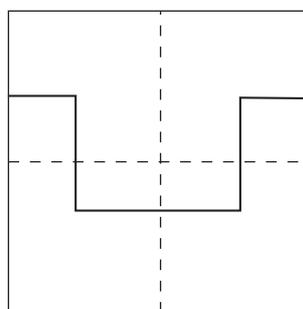
**P****Q****R****S****5.1** Which of the power supplies has the greatest peak voltage?

- A**   **P**
- B**   **Q**
- C**   **R**
- D**   **S**

5.2 Which trace shows a d.c. supply?

- A P
- B Q
- C R
- D S

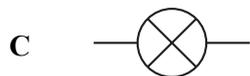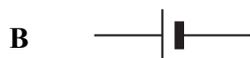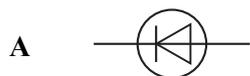5.3 Which component could produce, by itself, one of the traces shown?



5.4 Trace P represents a supply of frequency 60 Hz.

What is the frequency of supply Q?


- A 30 Hz
- B 60 Hz
- C 90 Hz
- D 120 Hz

**TURN OVER FOR THE NEXT QUESTION**

Turn over ►

**QUESTION SIX**

The diagram shows an electric circuit.

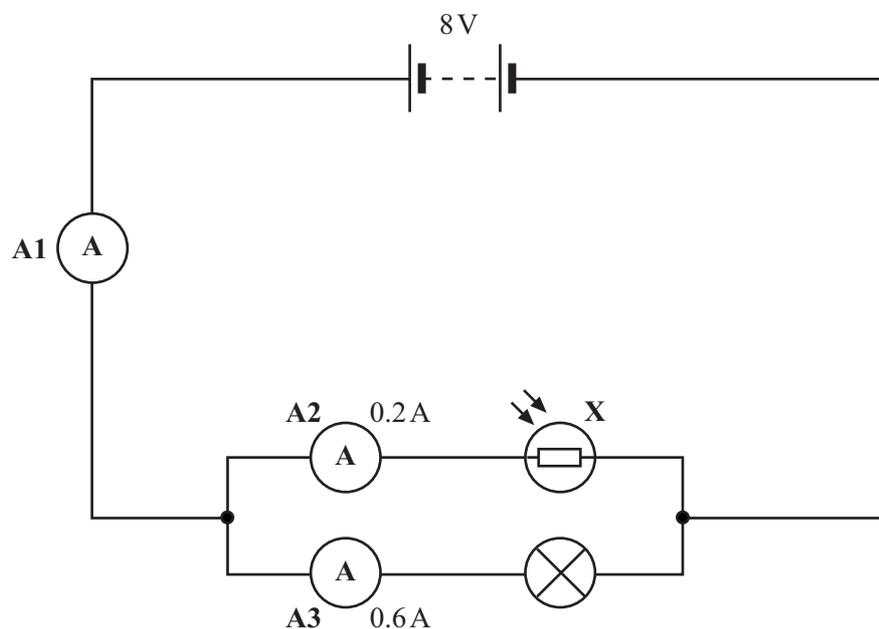

**6.1** What is the current flowing through ammeter A1?

- A 0.2 A
- B 0.4 A
- C 0.6 A
- D 0.8 A

**6.2** What is the potential difference (voltage) across X?

- A 4 V
- B 6 V
- C 8 V
- D 12 V

**6.3** What is the power of the lamp?

- A** 1.6 W
- B** 4.8 W
- C** 13.3 W
- D** 40.0 W

**6.4** What will happen to the reading on ammeter **A2** when the light intensity increases?

- A** It will fall to zero
- B** It will fall but not to zero
- C** It will stay the same
- D** It will increase

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

**QUESTION SEVEN**

The diagram shows how electricity is transferred from a power station to homes.



- 7.1** The generator at the power station . . . . .
- A** can have a rotating magnet or a rotating coil to produce a.c.
  - B** must have a coil rotating in a magnetic field to produce a.c.
  - C** must have a magnet rotating inside a coil to produce a.c.
  - D** produces only d.c.
- 7.2** The devices labelled **X** and **Y** are . . . . .
- A** circuit breakers.
  - B** motors.
  - C** transformers.
  - D** turbines.
- 7.3** The device labelled **X** is used to . . . . .
- A** change a.c. to d.c.
  - B** change d.c. to a.c.
  - C** decrease the voltage.
  - D** increase the voltage.
- 7.4** The device labelled **Y** is used to . . . . .
- A** change a.c. to d.c.
  - B** change d.c. to a.c.
  - C** decrease the voltage.
  - D** increase the voltage.


**NO QUESTIONS APPEAR ON THIS PAGE**

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**
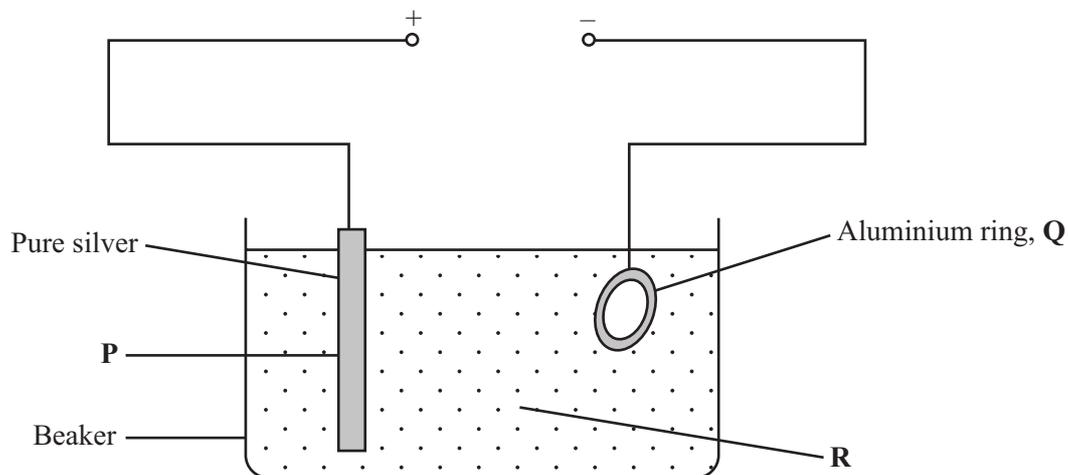
### QUESTION EIGHT

Some types of jewellery can be made by plating aluminium with a layer of silver, by electrolysis. The circuit is shown in the diagram.



Silver is deposited on the aluminium ring **Q**.

**8.1** Which line in the table correctly matches the labels **P**, **Q** and **R** on the diagram?

	<b>P</b>	<b>Q</b>	<b>R</b>
<b>A</b>	negative electrode	positive electrode	silver nitrate solution
<b>B</b>	negative electrode	positive electrode	water
<b>C</b>	positive electrode	negative electrode	silver nitrate solution
<b>D</b>	positive electrode	negative electrode	water

**8.2** Which statement correctly describes what happens in the beaker?

- A** Negative silver ions travel towards **Q**
- B** Positive silver ions travel towards **Q**
- C** Silver atoms travel towards **P**
- D** Silver atoms travel towards **Q**

**8.3** A charge of 900 C will deposit 1g of silver.

How long will it take a current of 2.5 A to deposit 1g of silver?

**A** 6 minutes

**B** 40 minutes

**C** 360 minutes

**D** 2250 minutes

**8.4** If a current of 5 A flows for three times as long as the current in **8.3**, what mass of silver will be deposited?

**A** 1 g

**B** 2 g

**C** 3 g


**D** 6 g

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

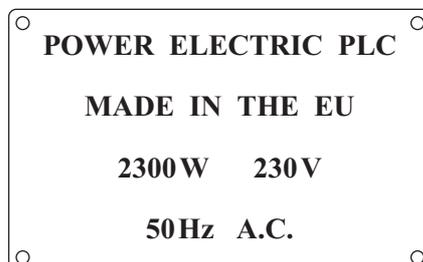**QUESTION NINE**

The diagram shows the base plate from an electric kettle.



**9.1** The kettle is connected to the stated power supply.

What current flows through the heating element?

- A** 4.6 A
- B** 5.0 A
- C** 10.0 A
- D** 46.0 A

**9.2** What charge flows through the element of the kettle when 920 000 J of energy are transferred?

- A** 800 C
- B** 4 000 C
- C** 20 000 C
- D** 48 000 C

**9.3** The kettle is taken to the USA where the supply is 115 V, 50 Hz a.c.

What is the power of the kettle in the USA?

- A** 575 W
- B** 1150 W
- C** 2300 W
- D** 48 000 W

- 9.4** The kettle is used in another country where the voltage of the supply is not known. A current of 8 A and a charge of 6 000 C flows through the element.

For how long has the kettle been switched on?


- A 0.8 seconds
- B 12.5 seconds
- C 0.8 minutes
- D 12.5 minutes

**TURN OVER FOR THE NEXT QUESTION**

**Turn over ►**

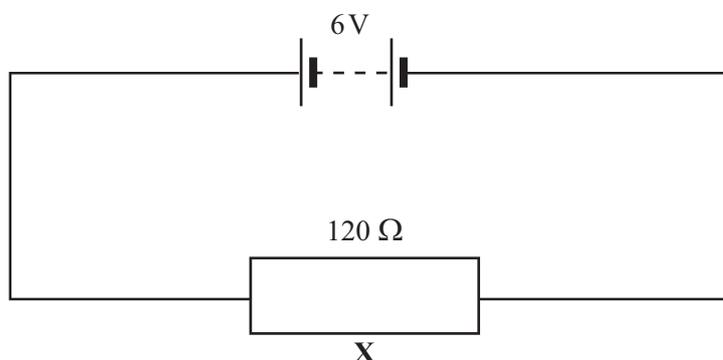**QUESTION TEN**

A 120 ohm resistor, **X**, is connected to a 6 volt battery as shown in the diagram.



**10.1** The battery consists of 1.5 V cells connected in series. The number of cells needed is . . . . .

- A 2
- B 3
- C 4
- D 9

**10.2** What current flows through **X**?

- A 0.05 A
- B 20 A
- C 114 A
- D 720 A

**10.3** Another 120 ohm resistor is connected in series with **X**.

The current now flowing through **X** is . . . . .

- A less than half the current flowing when only **X** was connected.
- B half the current flowing when only **X** was connected.
- C the same as the current flowing when only **X** was connected.
- D twice the current flowing when only **X** was connected.

**10.4** The second resistor is now connected in parallel with **X**, instead of in series.

The current flowing through **X** is now . . . . .

- A** less than half the current flowing when only **X** was connected.
- B** half the current flowing when only **X** was connected.
- C** the same as the current flowing when only **X** was connected.
- D** twice the current flowing when only **X** was connected.

**END OF TEST**

**THERE ARE NO QUESTIONS PRINTED ON THIS PAGE**