

Subject: ELECTRONIC DEVICES AND CIRCUITS

Time: 3 Hours

Max. Marks: 100

JUNE 2011

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The reverse recovery time t_{rr} in a PN junction diode is equal to_____.


- (A) Storage time t_s (B) Transition time t_t
(C) $t_s + t_t$ (D) $t_s - t_t$

b. In a full wave bridge rectifier the minimum reverse breakdown voltage that each diode should have, when the input is $V_m \sin \omega t$, is _____.

- (A) $2 V_m$ (B) V_m
(C) $V_m / 2$ (D) $4 V_m$


c. In the Zener diode regulator circuit shown in Fig.1, the power dissipation in the Zener diode is_____.

- (A) 630mW (B) 270mW
(C) 900mW (D) 1.7W

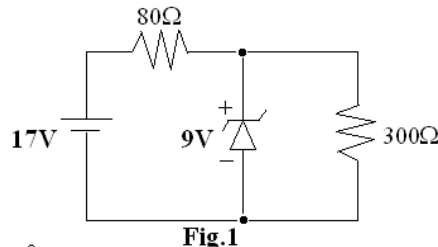

d. In the circuit of Fig.2, the base terminal of the transistor is kept open. If the transistor has $\alpha = 0.98$ and $I_{CO} = 40\text{nA}$, then V_{CE} of the transistor = _____.

- (A) 2.6V
(B) 2.8V
(C) 3V
(D) 0.7V

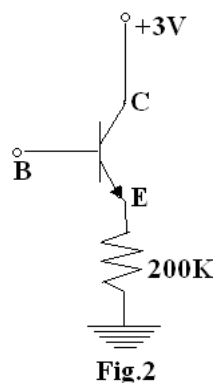

e. An amplifier has an open loop gain of 40dB and a bandwidth of 100kHz. Bandwidth needs to be increased to 0.6MHz by providing suitable negative feedback. The amount of negative feedback should be_____.


- (A) 0.5% (B) 0.05%
(C) 50% (D) 5%

f. Three amplifiers are cascaded to provide an overall gain of 10,000. The two stages have a gain of 40dB and 26dB respectively. The gain of the third stage is equal to ____ dB.

- (A) 5 (B) 14
(C) 54 (D) 66

g. In the circuit of Fig.3, if $g_m = 3\text{mA/V}$, the voltage gain v_o/v_i is equal to ____.

- (A) +24
(B) -24
(C) +6
(D) -6

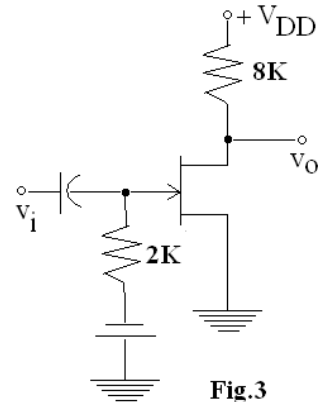

h. An amplifier has an open loop gain of 60dB and a gain stability of 20% due to temperature variations. If 1.9% negative feedback is given, the gain stability of the amplifier with feedback is equal to ____.

- (A) 10% (B) 1%
(C) 0.1% (D) 0.01%

i. If the intrinsic stand-off ratio, η , of a UJT is 0.55, and its R_{B2} is equal to $20\text{K}\Omega$, its R_{B1} is equal to ____.



- (A) 10K (B) 24.4k
(C) 11K (D) 36.4K

j. A thin-film capacitor has a capacitance of $0.4\text{pF}/(\mu\text{m})^2$. The thickness of the film is 400\AA . The relative dielectric constant for SiO_2 layer is equal to ____.

- (A) 3.52 (B) 4.52
(C) 5.52 (D) 8.52

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

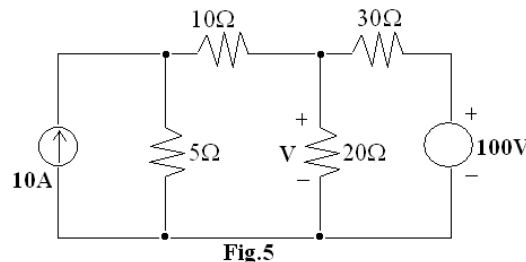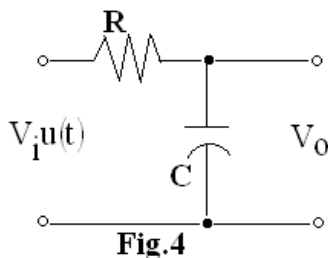Q.2 a. For the RC circuit shown in Fig.4, derive the expression for the output voltage, V_o across the capacitor C, if the input is a step of magnitude $V_i u(t)$. (8)



- b. For the circuit shown in Fig.5, find the voltage V across 20Ω resistance, by mesh analysis. (8)

Q.3 a. Draw the circuit diagram of a full wave bridge rectifier and sketch the output waveform across the load resistance, when the input to the rectifier is a sinusoidal voltage, $V_m \sin \omega t$. (6)

- b. A half wave rectifier with a capacitor filter is supplying a resistive load of 500Ω . It is supplied from $230V$, $50Hz$ ac mains. For the ripple factor to be equal to 2% , determine the value of the filter capacitor needed. Also calculate (i) dc load voltage (ii) dc load current and (iii) peak to peak ripple voltage across the capacitor. (10)

Q.4 a. Draw the output and input characteristics of an NPN transistor in common emitter configuration and explain about the different regions of operation. (8)

- b. Explain the operation of an enhancement MOSFET with suitable diagrams. (8)

Q.5 a. In a typical voltage divider bias circuit for a transistor, derive the expression for the stability factor $S(I_{CO})$. (5)

- b. Design the values of R_C , R_1 and R_2 in the amplifier circuit of Fig.6, so that the operating point is fixed at $V_{CE} = 4V$ and $I_C = 1mA$ with a bias stabilization factor $S(I_{CO})=20$. (8)

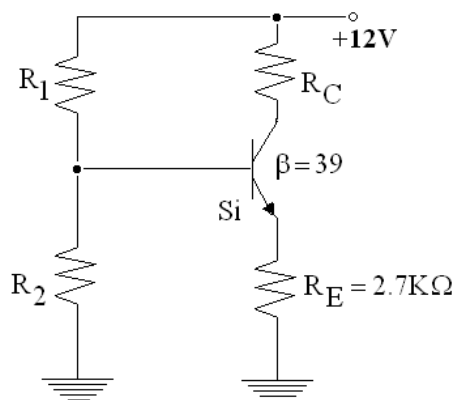


Fig.6

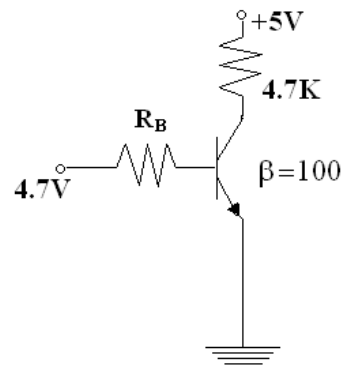


Fig.7

- c. In the circuit of Fig.7, determine the maximum value of R_B so that the transistor is in saturation. (3)

Q.6 a. Draw the circuit diagram of a single stage RC coupled amplifier and explain the purpose of each of the components used in the circuit. (8)

- b. In the RC coupled amplifier circuit of Fig.8, determine the cut-off frequencies, $f_{LC_{c1}}$ and $f_{LC_{c2}}$ due to C_{c1} and C_{c2} respectively. (8)

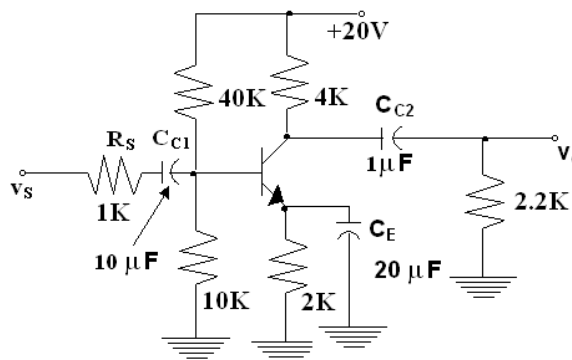


Fig.8

- Q.7** a. Draw the transformer coupled power amplifier and calculate its maximum possible efficiency. (8)
- b. A complementary symmetry class B output stage operated from a single supply voltage of +18V is to deliver power to a loud speaker load of 4Ω . If the input voltage is 5V rms, calculate the ac power output, dc power input, conversion efficiency and power dissipation in each of the transistors. (8)
- Q.8** a. Write six advantages of giving voltage series negative feedback to a voltage amplifier. (6)
- b. An amplifier has a gain of 60dB, bandwidth of 300 KHz, distortion of 15%, input impedance of $20K\Omega$ and an output impedance of $1K\Omega$. If voltage series negative feedback of 3.9% is given to this amplifier, calculate the gain, bandwidth, distortion, input impedance and output impedance of the amplifier with negative feedback. (6)
- c. In an RC phase shift oscillator using an ideal voltage amplifier, calculate the value of R, if $C = 5nF$ and the frequency of oscillation = 5KHz. (4)
- Q.9** a. Describe the photolithographic process in semiconductor fabrication using necessary sketches. (8)
- b. What is the length required to fabricate a $30K\Omega$ resistor whose width is $20\mu m$, given $R_s = 200\Omega/\text{square}$? What is the width required to fabricate a $5K\Omega$ resistor whose length is $25\mu m$. (8)