

AMIETE – ET/CS/IT

Time: 3 Hours

DECEMBER 2012

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. In an ideal Op-Amp open-loop voltage gain is

- | | |
|------------|--------------|
| (A) Zero | (B) Infinite |
| (C) Larger | (D) Medium |

b. Military grade op-amp temperature range is

- | | |
|-------------------|----------------------|
| (A) 0° C to 70° C | (B) -55° C to 125° C |
| (C) 0° C to 27° C | (D) -27° C to +40° C |

c. The main purpose of the difference amplifier in op-amp is

- | | |
|------------------------|------------------|
| (A) Better CMRR | (B) Better gain |
| (C) Noise cancellation | (D) All of these |

d. The current to voltage converters are called as

- | | |
|--------------------------------|-------------------------------|
| (A) Transconductance Amplifier | (B) Transresistance Amplifier |
| (C) Transadmittance Amplifier | (D) Converters |

e. Calculate phase-shift oscillator oscillating frequency if $R=6.49\text{ K}\Omega$ and $C=0.1\text{ }\mu\text{F}$

- | | |
|------------|------------|
| (A) 110 Hz | (B) 100 Hz |
| (C) 10 Hz | (D) 0.1 Hz |

f. The 555 timer can be used with supply voltage range of

- | | |
|-----------------------|-------------------|
| (A) $\pm 5\text{ V}$ | (B) +5 V to +18 V |
| (C) $\pm 18\text{ V}$ | (D) -5 V to -18 V |

- g. Which one of the following is a digital quantity?
- (A) Current-flowing out of an electric outlet
(B) Ten-position switch
(C) Temperature of a room
(D) Automobile speedometer
- h. How many bits are needed to represent decimal values ranging 0 to 12,500?
- (A) 16 (B) 14
(C) 10 (D) 8
- i. Simplified expression of $y = A \bar{B} D + A \bar{B} \bar{D}$ is
- (A) 1 (B) AB
(C) $A \bar{B}$ (D) $\bar{B} D$
- j. Simplified expression of $z = \overline{(A + C)(B + D)}$ is
- (A) 1 (B) $AB + \bar{B} D$
(C) $A\bar{C} + \bar{B} D$ (D) $AC + \bar{B} D$

PART (A)

Answer At least TWO questions. Each question carries 16 marks.

- Q.2** a. List the advantages of integrated circuits over discrete component circuit. (6)

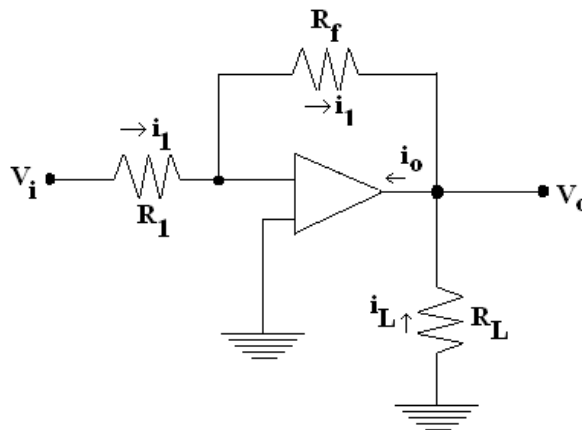


Fig. 1

- b. In Fig.1, given $R_1 = 10\text{ k}\Omega$, $R_f = 100\text{ k}\Omega$, $V_i = 1\text{ V}$, a load of $25\text{ k}\Omega$ is connected to the output terminal. Calculate
- (i) i_1 (ii) v_o
(iii) i_L and i_o (6)
- c. Draw an AC equivalent circuit of Fig. 2 using hybrid- Π model. (4)

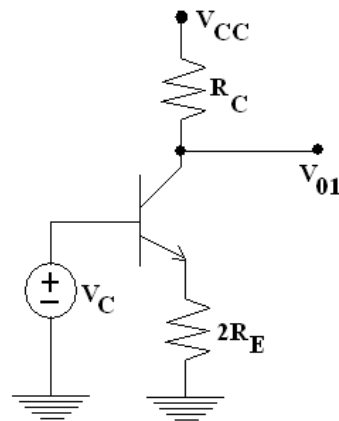


Fig. 2

- Q.3** a. For the non-inverting amplifier of Fig. 3, $R_1 = 1 \text{ k}\Omega$ and $R_f = 10 \text{ k}\Omega$. Calculate the following:
- The maximum output offset voltage due to V_{OS} and I_B . The opamp is LM307 with $V_{OS} = 10 \text{ mV}$ and $I_B = 300 \text{ nA}$ and $I_{OS} = 50 \text{ nA}$.
 - The value of R_{comp} needed to reduce the effect of I_B .
 - The maximum output-offset voltage if R_{comp} as calculated in (ii) is connected in the circuit. (8)

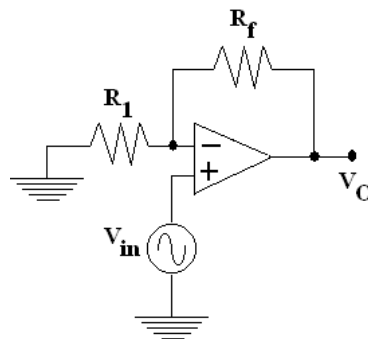


Fig. 3

- b. With the needful diagram show the difference between V to I and I to V converter. (8)
- Q.4** a. Draw the positive peak-detector circuit and explain its working operation. (8)
- b. In Fig.4, show that $V_o = \frac{1}{RC} \int V_i \cdot dt$. (8)

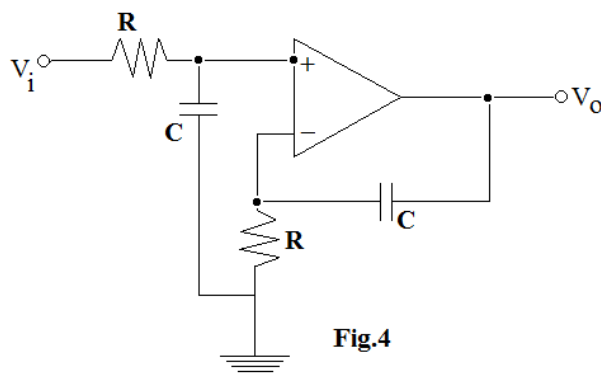


Fig.4

- Q.5** a. Explain the working of Successive Approximation Analog to Digital Converter. (8)
- b. Explain Astable-multivibrator circuit operation using 555 timers. (8)

PART (B)

Answer At least TWO questions. Each question carries 16 marks.

- Q.6** a. What are the advantages of digital techniques over analog? (6)
- b. A small process control uses octal codes to represent it's 12-bit memory addresses.
- How many octal digits are required?
 - What is the range of addresses in octal?
 - How many memory locations are there? (4)
- c. Convert the following:
- 0 1 1 1 1 0 0 0 0 1 (BCD) to decimal
 - B2F₁₆ to octal
 - 378₁₀ to hexa. (6)
- Q.7** a. Determine the output in Fig.5, for the condition A=0, B=1, C=1 and D=1. (4)

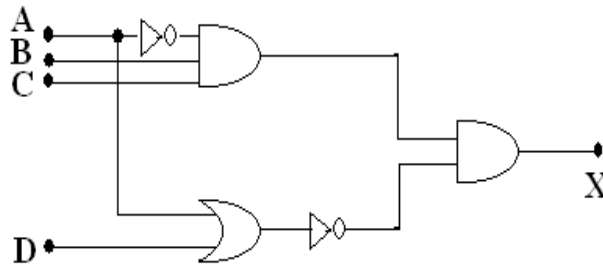


Fig. 5

- b. Implement INVERTER, AND and OR gates using NAND and NOR-gates. (8)
- c. Simplify the expression $X = (\bar{A} + B)(A + B + D)\bar{D}$ (4)
- Q.8** a. Explain the design procedure of full adder. (8)
- b. Write a short note on Demultiplexers. (8)
- Q.9** a. Draw and explain the NOR-gate latch working operation. (8)
- b. Design four-bit ring counter using D flip-flops. (8)