

Time: 3 Hours

DECEMBER 2013

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The characteristic impedance Z_o of transmission line is

- (A) Arithmetic mean of Z_{oc} and Z_{sc}
- (B) Geometric mean of Z_{oc} and Z_{sc}
- (C) Harmonic mean of Z_{sc} and Z_{oc}
- (D) Always equal to Z_{sc} and Z_{oc}

b. A transmission line becomes distortion less if

- (A) $G = 1/R$
- (B) $LG = CR$
- (C) It operate in AF range
- (D) It is properly matched

c. Norton's equivalent circuit consists of

- (A) voltage source in parallel with impedance
- (B) voltage source in series with impedance
- (C) current source in series with impedance
- (D) current source in parallel with impedance

d. The convolution of $f(t)*g(t)$ is

(A) $\int_0^{\infty} f(t)g(t-\tau)d\tau$

(B) $\int_0^t f(t)g(t-\tau)d\tau$

(C) $\int_0^t f(t-\tau)g(t)d\tau$

(D) $\int_0^t f(t)g(t-\tau)d\tau$

Code: DE57

Subject: NETWORKS AND TRANSMISSION

- e. If Z parameter of a two port network are $Z_{11}=5\Omega$, $Z_{22}=7\Omega$; $Z_{12}=Z_{21}=3\Omega$ then the A,B,C,D parameters are respectively given by

- (A) $\frac{5}{3}; \frac{26}{3}; \frac{1}{3}; \frac{7}{3}$ (B) $\frac{10}{3}; \frac{52}{3}; \frac{2}{3}; \frac{14}{3}$
 (C) $\frac{15}{3}; \frac{78}{3}; \frac{3}{3}; \frac{21}{3}$ (D) $\frac{3}{5}; \frac{3}{26}; \frac{3}{1}; \frac{3}{7}$

- f. An ideal filter should have

- (A) Zero attenuation in the pass band
 (B) Infinite attenuation in the pass band
 (C) Zero attenuation in the attenuation band
 (D) Infinite attenuation in the attenuation band

- g. A transmission line VSWR is a

- (A) vector quantity (B) scalar quantity
 (C) dimension quantity (D) exponential term

- h. Time constant of series RL circuit is

- (A) $\frac{R}{L}$ (B) $\frac{L}{R}$
 (C) RL (D) None of these

- i. In a circuit containing R, L and C, power loss can take place in

- (A) L only (B) R only
 (C) C only (D) All of these

- j. Propagation constant parameter is used in

- (A) Symmetrical networks (B) Asymmetrical networks
 (C) Both type of networks (D) Inverse networks

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

- Q.2** a. Determine the current in a circuit as shown in Fig.1, when the switch 's' is closed at $t=0$. Assume there is no initial charge on the capacitor or current in the inductor (8)

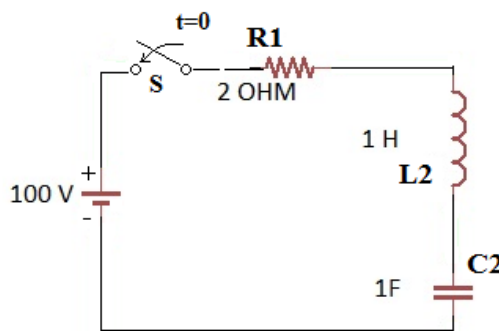


Fig.1

- b. For the network shown in Fig.2 determine the voltage across inductor.

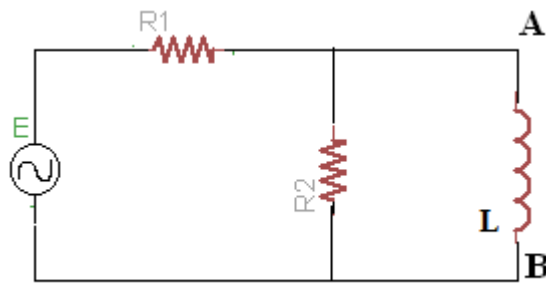


Fig.2

- Q.3** a. Find the Laplace transform of any function that repeats itself. (8)
- b. Write short note on- (8)
- (i) Initial and final value theorem
- (ii) Convolutional Integrals
- Q.4** a. State Reciprocity theorem and check whether the circuit shown in fig.3 obeys reciprocity theorem (8)

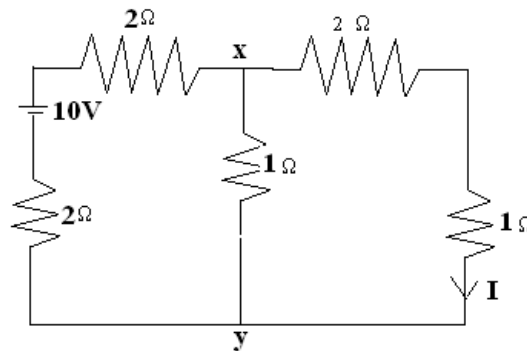


Fig.3

- b. State and prove the substitution theorem. (8)
- Q.5** a. The z-parameter for a 2-port network are $Z_{11}=30\Omega$, $Z_{22} = 40\Omega$, $Z_{21} = 20\Omega$. Find the equivalent T network. (8)
- b. For the given 2 port network calculate ABCD. Parameters and image impedances. (8)

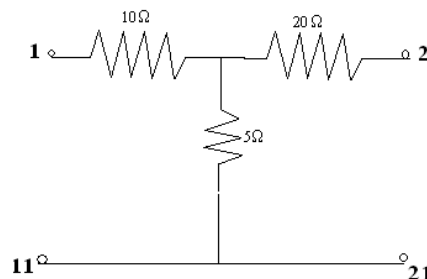


Fig.4

- Q.6** a. Draw and explain a series resonant circuit with the help of phasor diagram. (8)

- b. What is quality factor? Explain its effect on bandwidth. Determine Q factor of a coil for the series circuit having resonance frequency $f_r = 7.12 \text{ Hz}$ and $BW = 3.178 \text{ Hz}$ (8)

- Q.7** a. Explain the following
(i) Reflection coefficient (ii) Secondary line constants
(iii) Distortion less Transmission Line (9)
- b. A transmission line connects a transmitter of 1.2 MHz to the aerial located 100m away from it. If Z_0 of the lines be equal to 500Ω . What is the input impedance of this line if antenna end is a) open circuited b) short circuited. (7)
- Q.8** a. What is stub? Explain the different type of stub matching used in transmission lines. (10)
- b. Derive the relation between VSWR ('S') and Reflection coefficient ('K'). (6)
- Q.9** a. A Π section filter network consists of a series arm inductance of 10mH and two shunt arm capacitances of $0.16 \mu\text{F}$ each. Calculate the cut-off frequency and attenuation and phase shift at 12 KHz . What is the value of nominal impedance in the pass band? (8)
- b. Design k- type band pass filter having a design impedance of 500Ω and cut-off frequencies 1 KHz and 10 KHz . (8)