

GAUTENG DEPARTMENT OF EDUCATION

SENIOR CERTIFICATE EXAMINATION

ELECTRICIANS WORK SG

Possible Answers / Moontlike Antwoorde
Feb / Mar / Maart 2006

QUESTION 1
ELECTRICAL CURRENT THEORY

$$\begin{aligned}
 1.1.1 \quad XL &= 2\pi FL & (1) \\
 &= 2\pi \times 50 \times 0,2 & (1) \\
 &= 62,83 \text{ ohm} & (1)
 \end{aligned}$$

$$\begin{aligned}
 Z &= \sqrt{R^2 + (XL - XC)^2} & (1) \\
 &= \sqrt{8^2 + (62,83 - 12)^2} & (1) \\
 &= \sqrt{2\,647,6} & (1) \\
 &= 51,46 \text{ ohm} & (1) \\
 V &= I \times Z & (1) \\
 &= 1,2 \times 51,46 & (1) \\
 &= 61,75 \text{ V} & (1)
 \end{aligned}$$

[10]

$$\begin{aligned}
 1.1.2 \quad \cos\phi &= R / Z & (1) \\
 \cos\phi &= 8 / 51,46 \\
 \cos\phi &= 0,155 & (1) \\
 P &= VI \cos\phi & (1) \\
 &= 61,75 \times 1,2 \times 0,155 & (1) \\
 P &= 11,485 \text{ W} & (1)
 \end{aligned}$$

OR

$$\begin{aligned}
 P &= I^2 R & (1) \\
 &= 1,2^2 \times 8 & (2) \\
 &= 11,52 \text{ W} & (2)
 \end{aligned}$$

[5]

$$1.1.3 \quad X_c = \frac{1}{2\pi f C} \quad (1)$$

$$C = \frac{1}{2\pi f X_c} \quad (1)$$

$$C = \frac{1}{2 \times \pi \times 50 \times 12} \quad (1)$$

$$C = 265 \times 10^{-6} \text{ F.} \quad (1)$$

$$= 265 \mu\text{F} \quad (1)$$

[5]

[20]

1.2

Midordinates	Midordinates ²
6	36
13,5	182,25
15,15	240,25
15	225
10	100
3	9
63	792,5

$$\text{Average value} = e_1 + e_2 + e_3 + e_4 + \dots + e_6 / \text{no of midordinates} \quad (1)$$

$$= 63/6 \quad (2)$$

$$= 10,5 \text{ V} \quad (1)$$

$$\text{Rms value} = \sqrt{e_1^2 + e_2^2 + e_3^2 + \dots + e_6^2} / \text{no of midordinates} \quad (1)$$

$$= \sqrt{792,5 / 6} \quad (2)$$


$$= 11,49 \text{ V} \quad (1)$$

$$\text{Form factor} = \text{rms} / \text{ave} \quad (1)$$

$$= 11,49 / 10,35 \quad (2)$$

$$= 1,094 \quad (1)$$

GRAPH

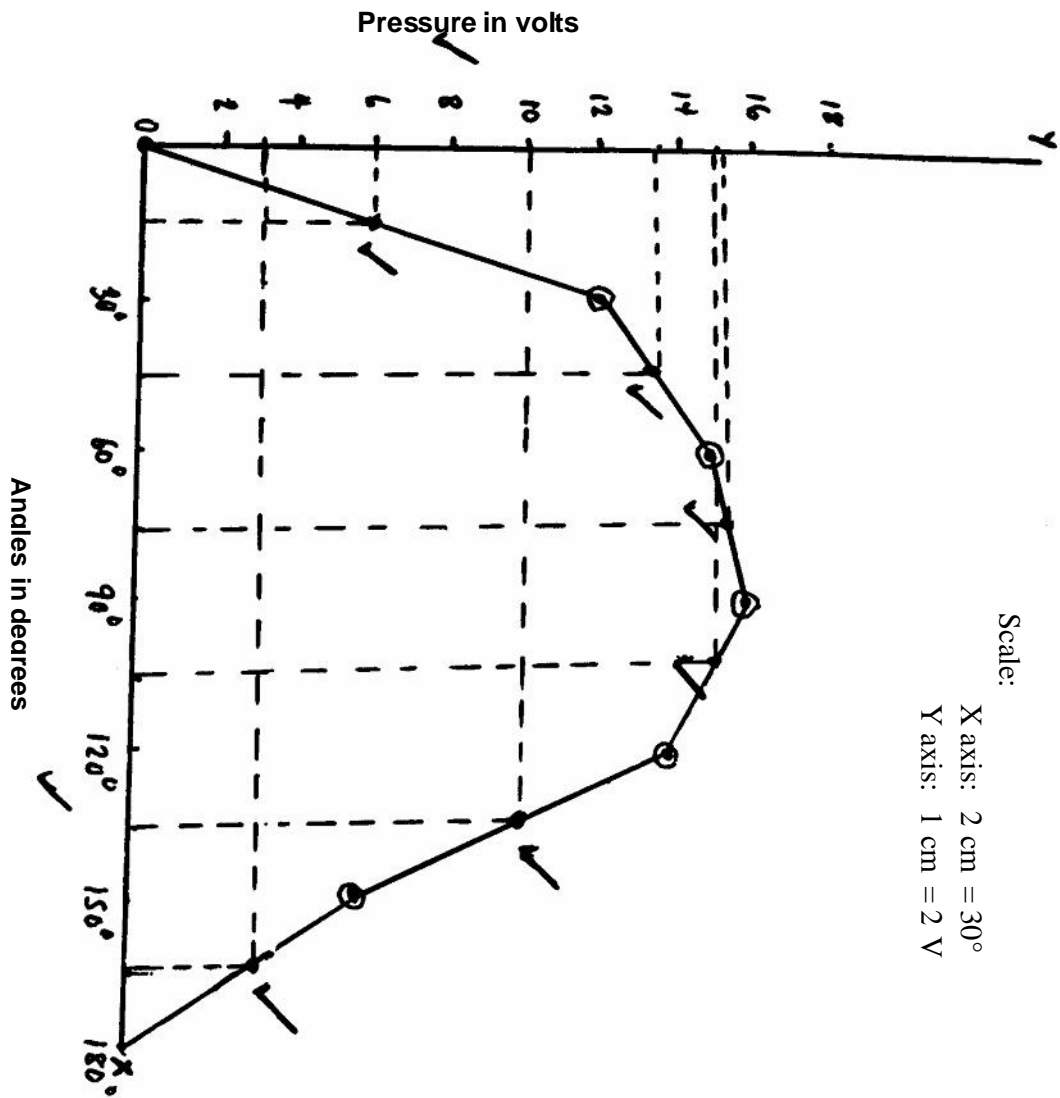

(8)
[20]

- | | | | |
|-------|-----------|----------------------|-----|
| 1.3.1 | I_{rms} | $= 0,707 \times I_m$ | (1) |
| | | $= 0,707 \times 75$ | (1) |
| | | $= 53,025 \text{ A}$ | (1) |
| 1.3.2 | $2\pi f$ | $= 563$ | (1) |
| | f | $= 563/2\pi$ | (1) |
| | | $= 89,6 \text{ Hz}$ | (1) |

1.3.3 $i = 75 \sin(563t)$ (1)
 $= 75 \sin(563 \times 3 \times 10^{-3})$ (1)
 $= 75 \sin(1,689 \text{ rad})$
 $= 75 \sin(1,689 \times 57,3)$ (1)
 $= 75 \sin 96,77$
 $= 74,47 \text{ A}$ (1)

[10]

1.4 Welding machines (1)
 Induction motors (1)
 Transformer s (1)

[3]

1.5 $F = 1 / T$ (1)
 $= 1 / 0,005$ (1)
 $= 200 \text{ Hz}$ (1)


[3]

1.6 0° (2)

1.7 $? \text{ rad} = 180^\circ$ (2)


[60]**QUESTION 2**

2.1.1

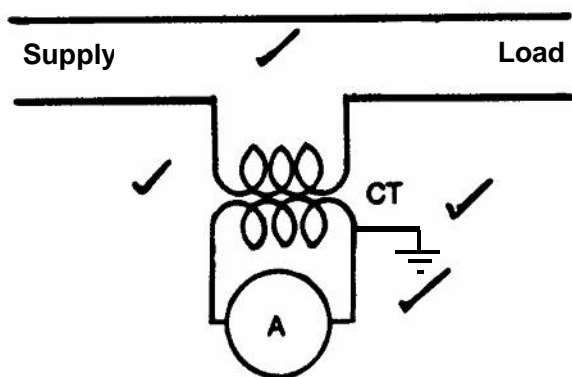

(4)

2.1.2

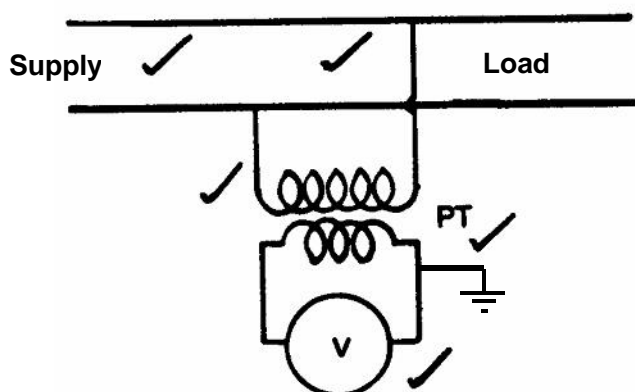

(5)

[9]

2.2.1 Construction

It comprises a number of reeds (thin steel strips) 'tuned' to vibrate at different frequencies by varying their length.

They are placed in front of a laminated iron core around which an exciting coil is wound.

(5)

2.2.2 Operation

The exciting coil is connected across the supply of which the frequency is to be measured, which sets up an alternating flux. This alternating flux will cause the reed tuned to that frequency to vibrate and its tip, which is painted, will appear to be drawn out.

The reeds close by will also vibrate but to a lesser extent.

(5)

[10]

2.3 $\text{EFFICIENCY} = \text{P OUTPUT} / \text{P INPUT} \times 100\%$

$$\text{INPUT} = \text{OUTPUT} / \text{EFFICIENCY} \times 100\%$$

(1)

$$= 125\,000 / 0,85$$

(1)

$$= 147\,058,823 \text{ W}$$

(1)

$$\text{Pin} = \sqrt{3} \times V_L \times I_L \times \cos \phi$$

(1)

$$I_L = \text{Pin} / \sqrt{3} \times V_L \times \cos \phi$$

(1)

$$= 147\,000 / 1,732 \times 380 \times 0,9$$

(2)

$$= 248,258 \text{ A}$$

(1)

[8]

2.4 In star $V_L = \sqrt{3} \times V_p$

(1)

$$= V_L / \sqrt{3}$$

(1)

$$= 380 / \sqrt{3}$$


(1)

$$= 219,39 \text{ V}$$

(1)

$$I_L = I_p = 25 \text{ A}$$

(1)

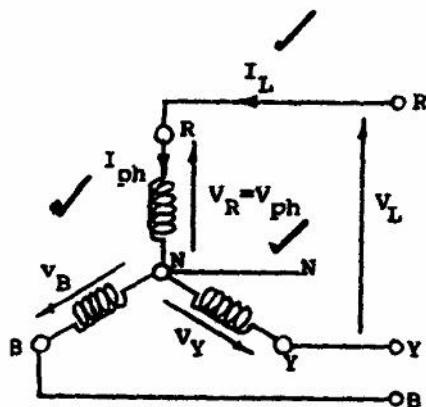

$$V_L = 380 \text{ V}$$

$$V_P = 219,39 \text{ V}$$

$$I_L = I_P = 25 \text{ A}$$

Star connection

(5)

[10]

$$\begin{aligned} 2.5 \quad P_{in} &= \sqrt{3} \times V_L \times I_L \times \cos \phi \\ &= \sqrt{3} \times 380 \times 25 \times 0,86 \\ &= 14\,150,855 \text{ W} \\ &= 14,150 \text{ kW} \end{aligned}$$

(1)

(1)

(1)

[3]

[40]

QUESTION 3

- 3.1 The voltage ratios must be the same. (2)
 The primary as well as the secondary connections must be the same. (2)
 They must be designed for the same frequency. (2)
 The relation between reactance and resistance should fall within the same limits. (2)

[8]

$$\begin{aligned} 3.2.1 \quad P_S &= V_L \times I_L & (1) \\ I_L &= P_S / V_L \quad V_S = \text{Supply Voltage} & (1) \\ &= 120\,000 / 2\,000 & (1) \\ &= 60 \text{ A} & (1) \end{aligned}$$

$$\begin{aligned} 3.2.2 \quad P_S &= V_{L2} \times I_{L2} & (1) \\ I_{L2} &= P_S / V_{L2} & (1) \\ &= 120\,000 / 380 & (1) \\ &= 315,79 \text{ A} & (1) \end{aligned}$$

OR

$$\begin{aligned} V_P / V_S &= I_S / I_P & (1) \\ I_S &= 2\,000 \times 60 / 380 & (2) \\ I_S &= 315,79 \text{ A} & (1) \\ (\text{NOTE: } I_{L2} = I_S = 315,79 \text{ A}) & & \end{aligned}$$

3.2.3

$$V_P / V_S = N_P / N_S$$
$$N_P = V_P \times N_S / V_S$$
$$= 2\,000 \times 150 / 380$$
$$= 789,47 \text{ turns}$$

(1)

(1)

(1)

(1)

[12]

3.3

$$P_S = V \times I$$
$$I = P_S / V$$
$$= 250\,000 / 7\,000$$
$$= 35,71 \text{ A}$$

(1)

(1)


(1)

(1)

[4]

$P_S = \text{Skyndr ywing} = \text{VA App arent power}$

3.4

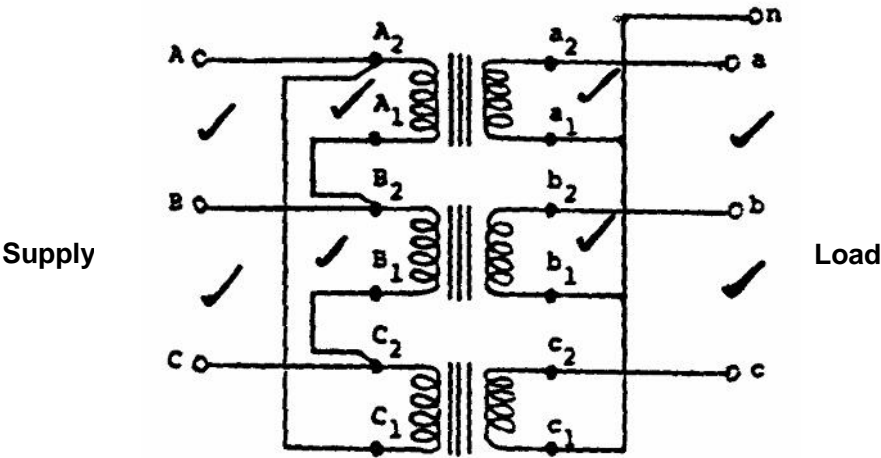

[8]

3.5

Its purpose is to dry the air which pas ses into the trans former tank when the air above the tank contracts, thus preventing mo isture from entering the trans former.

[3]

[35]

QUESTION 4

4.1

The speed of rotation of the magnetic flux is called synchr onous speed.

(2)

The speed that the Rotor rotates is called the Rot or speed and is always less than the sync hronous spe ed.

(2)

[4]

4.2 True speed $= \frac{F}{p} (1 - 5)$ (1)

$= \frac{50}{3} (1 - 8\%)$ (1)

$= 16,667 (1 - 0,08)$ (1)

$= 16,667 (0,92)$ (1)

$= 15,33 \text{ rev. per sec}$ (1)


$= 15,33 \times 60$ (1)

$= 920 \text{ om wente lings per min.}$ (1)

[Explanat ion: $S = \frac{n_s - n_r}{n_s}$ and $n_s = \frac{f \times 60}{p}$ and $p = \text{pole pairs, i.e.}$ (3)

[7]

4.3

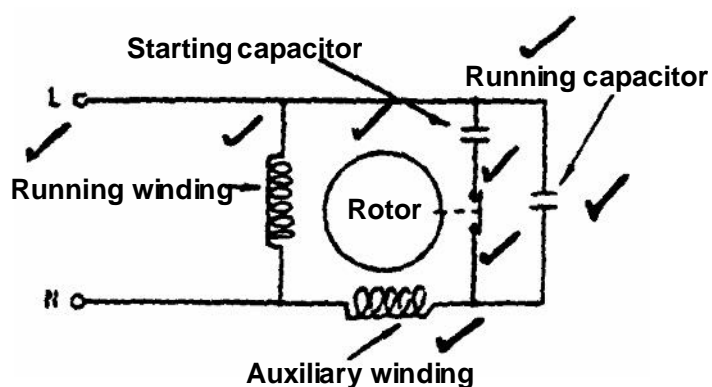

CAPACITOR START-AND-RUN MOTOR

[8]

4.4 Frequen cy (1)

No of pole pairs (1)

[2]


4.5 To switch or activate the main contac t. (2)

AND

For safety pur poses (c annot restart automat ically). (2)

[4]

4.6

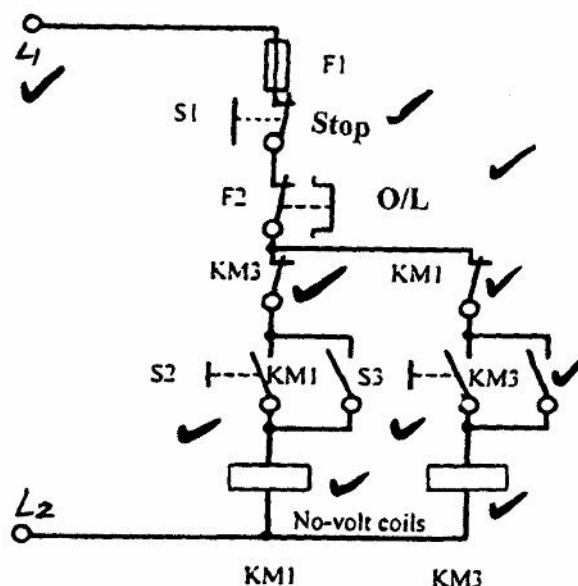

FOR WARD-REVERSE-STARTER CONTROL CIRCUIT

[10]


[35]

QUESTION 5

- 5.1
- Both current and voltage are amplified and therefore this can be regarded as a power amplifier.
 - The output signal is inverted with respect to the input signal.
 - The input and output impedance are in the medium range i.e. between approximately 1,5 and 5 kilo-ohms.


[6]

5.2

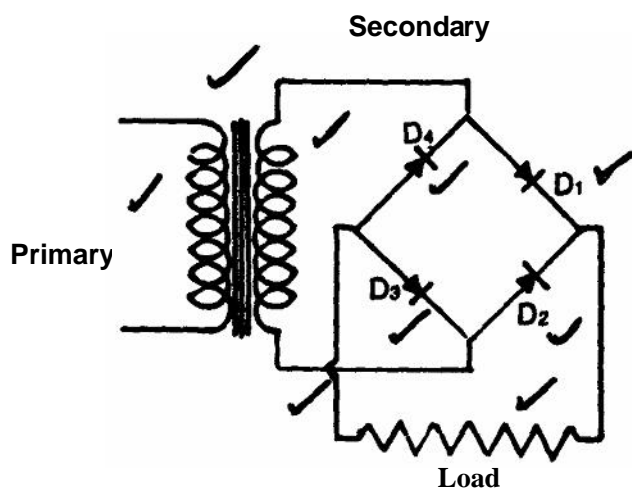

[9]

5.3

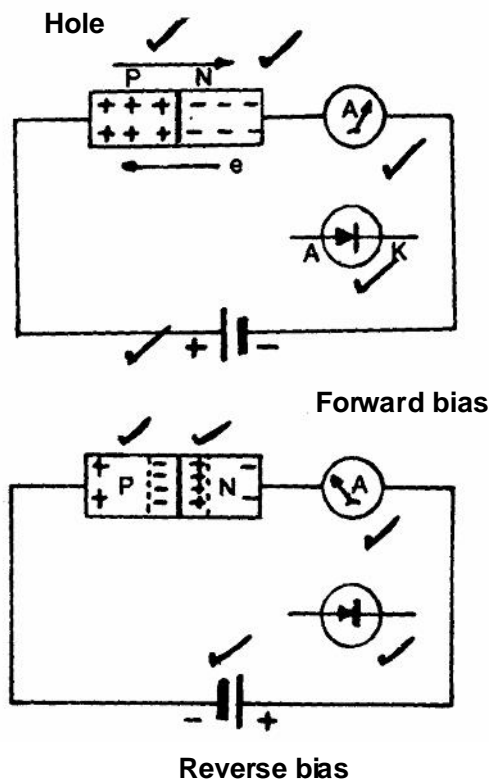

[10]

- 5.4
1. Switch off the power supply. (1)
 2. If the supply cannot be switched off the person must be pulled away using an insulated material. (1)
 3. If necessary the conductors must be cut with pliers or hexed off with an axe. (1)
 4. Ensure that you do not get shocked as well. (1)
 5. Examine the person and if necessary you can perform basic treatment or have a doctor called. (1)

[5]

[30]

TOTAL: 200