


POSSIBLE ANSWERS FOR / MOONTLIKE ANTWOORDE VIR :

**ELECTRONICS SG
ELEKTRONIKA SG**

704-2/0

VRAAG 1/QUESTION 1

1.1.1

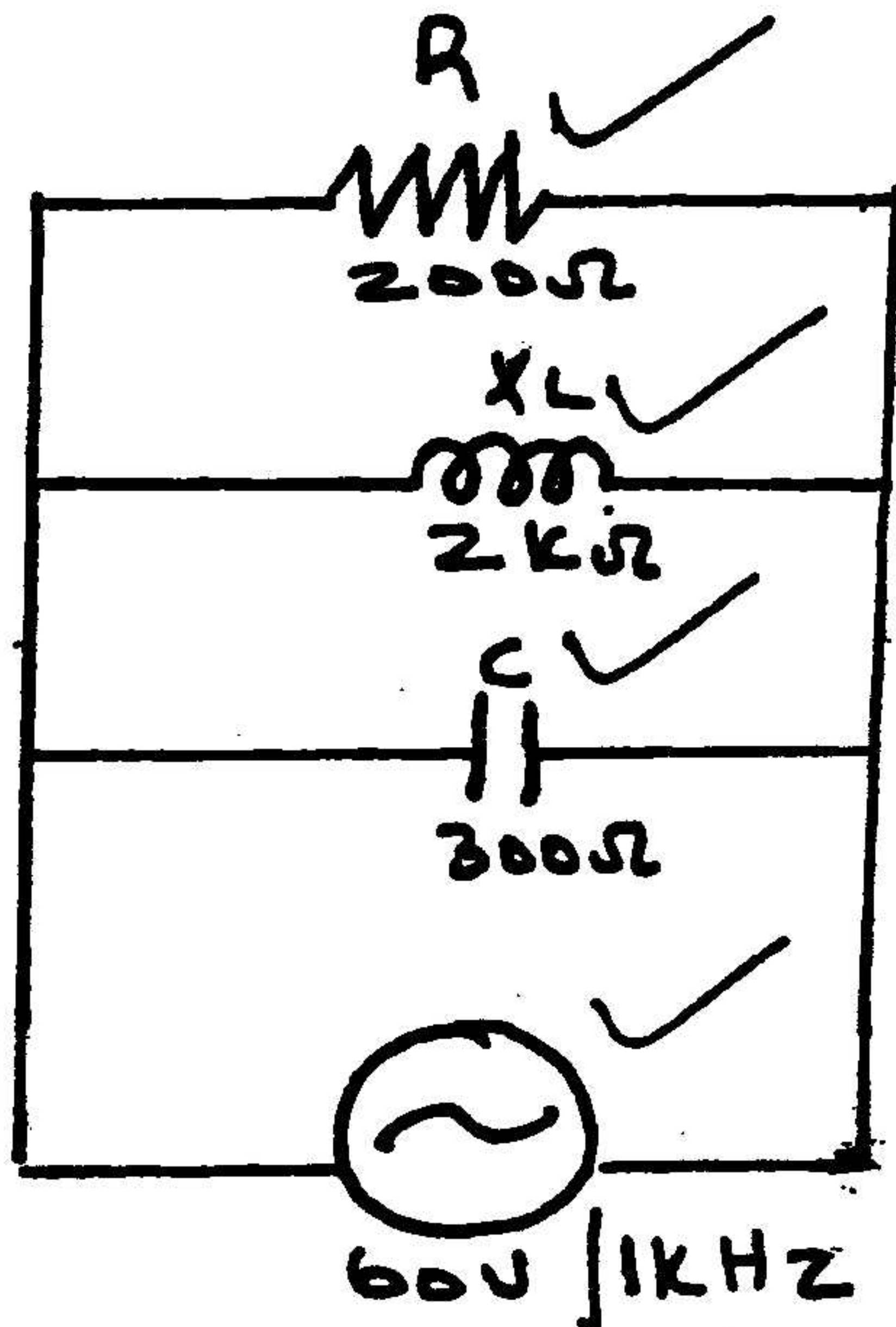

(4)

1.1.2

A $I_R = V/R = \frac{60 \text{ V}}{200 \Omega} = 0,3 \text{ A}$

$I_L = V/X_L = \frac{60 \text{ V}}{2000 \Omega} = 0,03 \text{ A}$

$I_C = \frac{V}{X_C} = \frac{60 \text{ V}}{300 \Omega} = 0,2 \text{ A}$

(9)

B $I_X = I_C - I_L$
 $I_X = 0,2 \text{ A} - 0,03 \text{ A}$
 $I_X = 0,17 \text{ A}$

(3)

C $I_T = \sqrt{I_R^2 + I_X^2}$
 $I_T = \sqrt{(0,3)^2 + (0,17)^2}$
 $I_T = \sqrt{0,09 + 0,0289}$
 $I_T = 0,345 \text{ A}$

(5)

D $\cos \phi = \frac{I_R}{I_T} = \frac{0,3}{0,345} = 0,869$

or/of (3)

$\tan \phi = \frac{I_X}{I_R} = \frac{0,17}{0,3} = 0,566$

or/of

$\sin \phi = \frac{I_X}{I_T} = \frac{0,17}{0,345} = 0,493$

$$E \quad \phi = \cos^{-1} 0,869 = 29,5^\circ \quad (2)$$

$$\phi = \tan^{-1} 0,566 = 29,5^\circ$$

$$\phi = \sin^{-1} 0,439 = 29,5^\circ$$

$$F \quad C = \frac{1}{2\pi f \times X_C}$$

$$C = \frac{1}{2\pi \times 1000 \times 300}$$

$$C = \frac{1}{1884955,59}$$

$$C = 0,00000053F$$

$$C = 530nF \text{ or/of } 0,53\mu F$$


$$G \quad L = \frac{X_L}{2\pi f} = \frac{2000}{2\pi \times 1000} = 0,3183H = 318,3 \text{ mH} \quad (3)$$

$$H \quad P = V \times I \times \cos\phi$$

$$P = 60 \times 0,345 \times 0,869$$

$$P = 17,988 \text{ W}$$

1.1.3

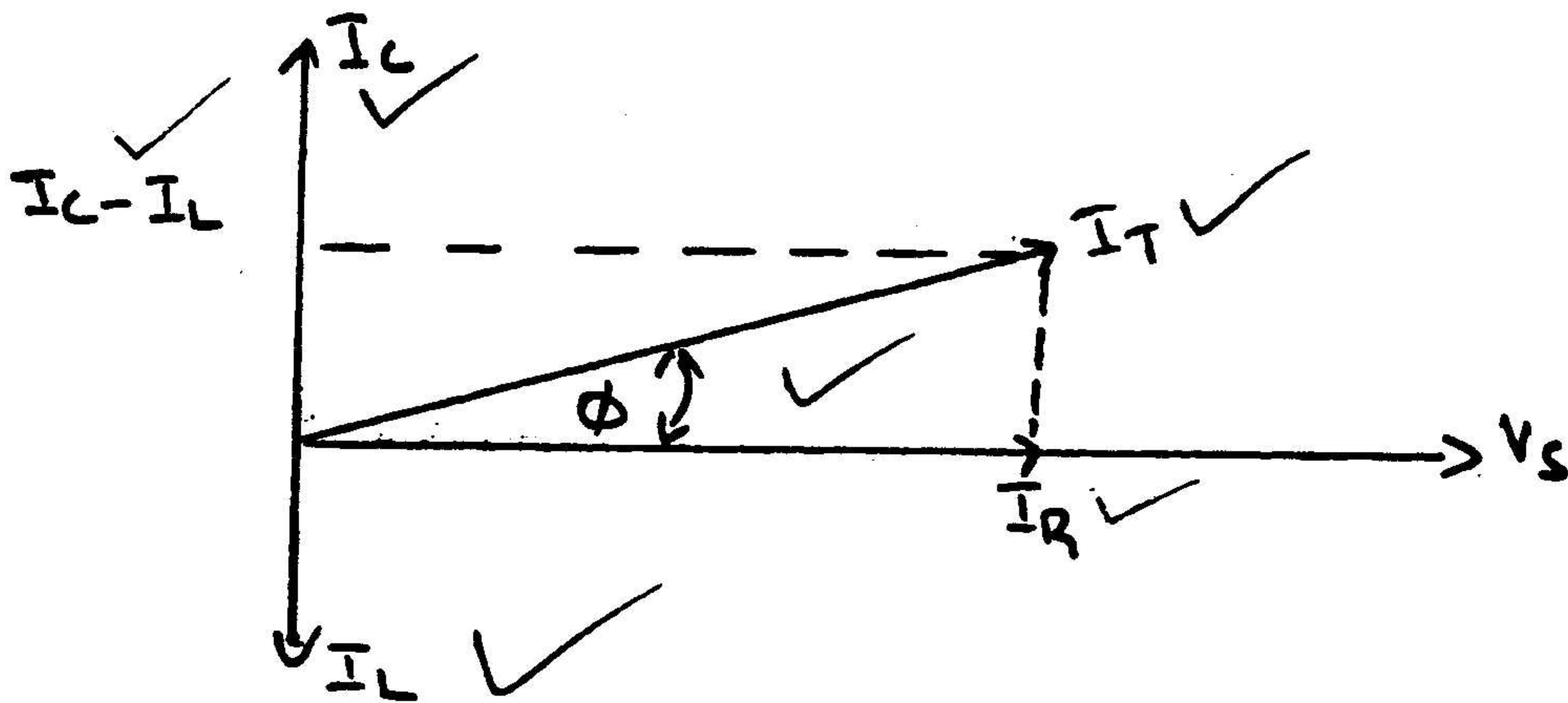

VRAAG 2/QUESTION 2

$$2.1.1 \quad V_L = 320 \quad \cos\phi = 0,866 \quad \text{efficiency} = 90\%$$

$$V_P = \frac{V_L}{\sqrt{3}} = \frac{320 \text{ V}}{\sqrt{3}} = 184,75 \text{ V}$$

(3)

2.1.2 IN STAR / STER

$$I_L = I_{ph} = 25A$$

2.1.3 $P_{in} = \sqrt{3} \times V_L \times I_L \times \cos\phi$



$$P_{in} = \sqrt{3} \times 320 \times 25A \times 0,866$$

$$P_{in} = 11,999 \text{ KW}$$

2.2


R Y B

2.3

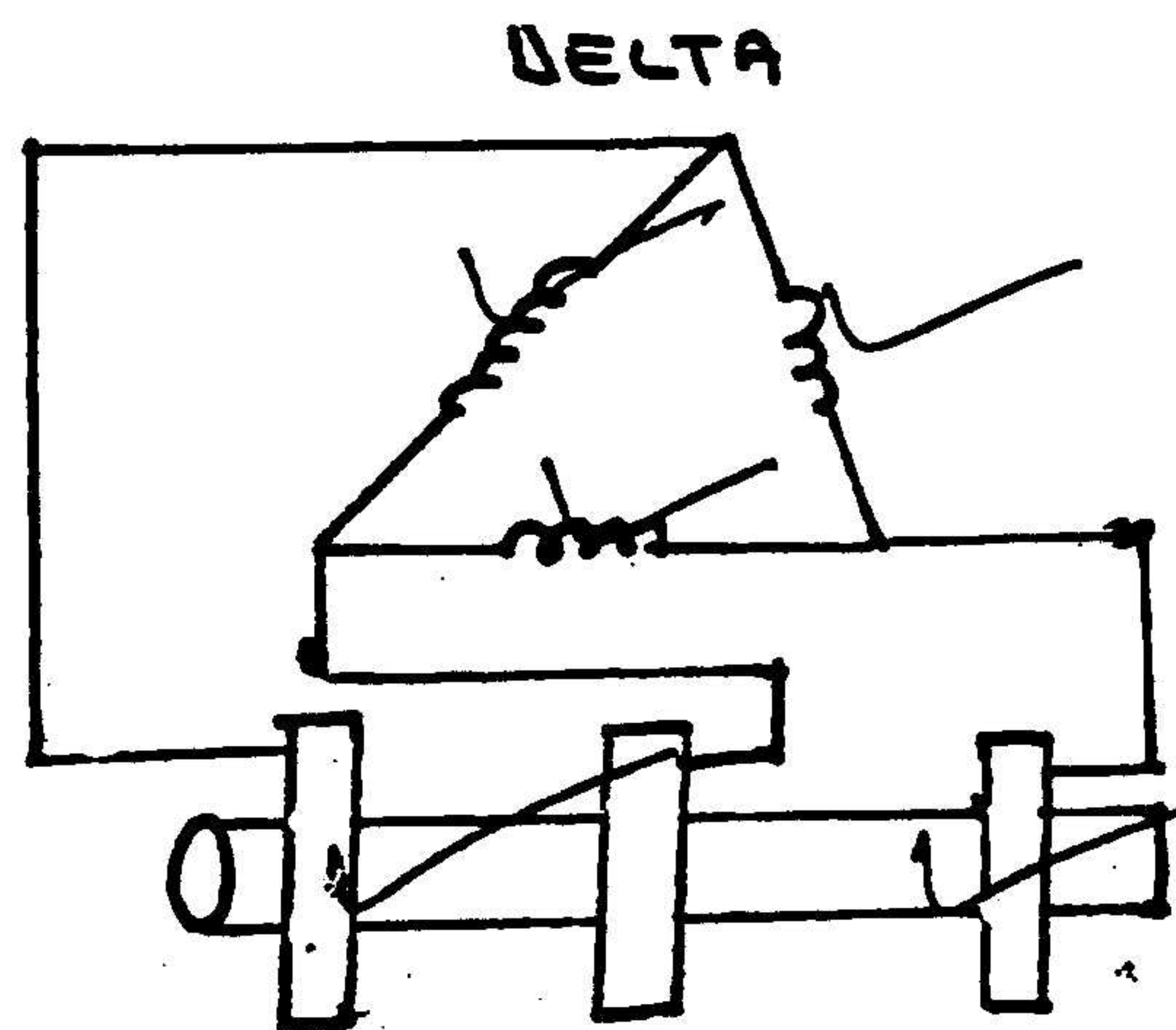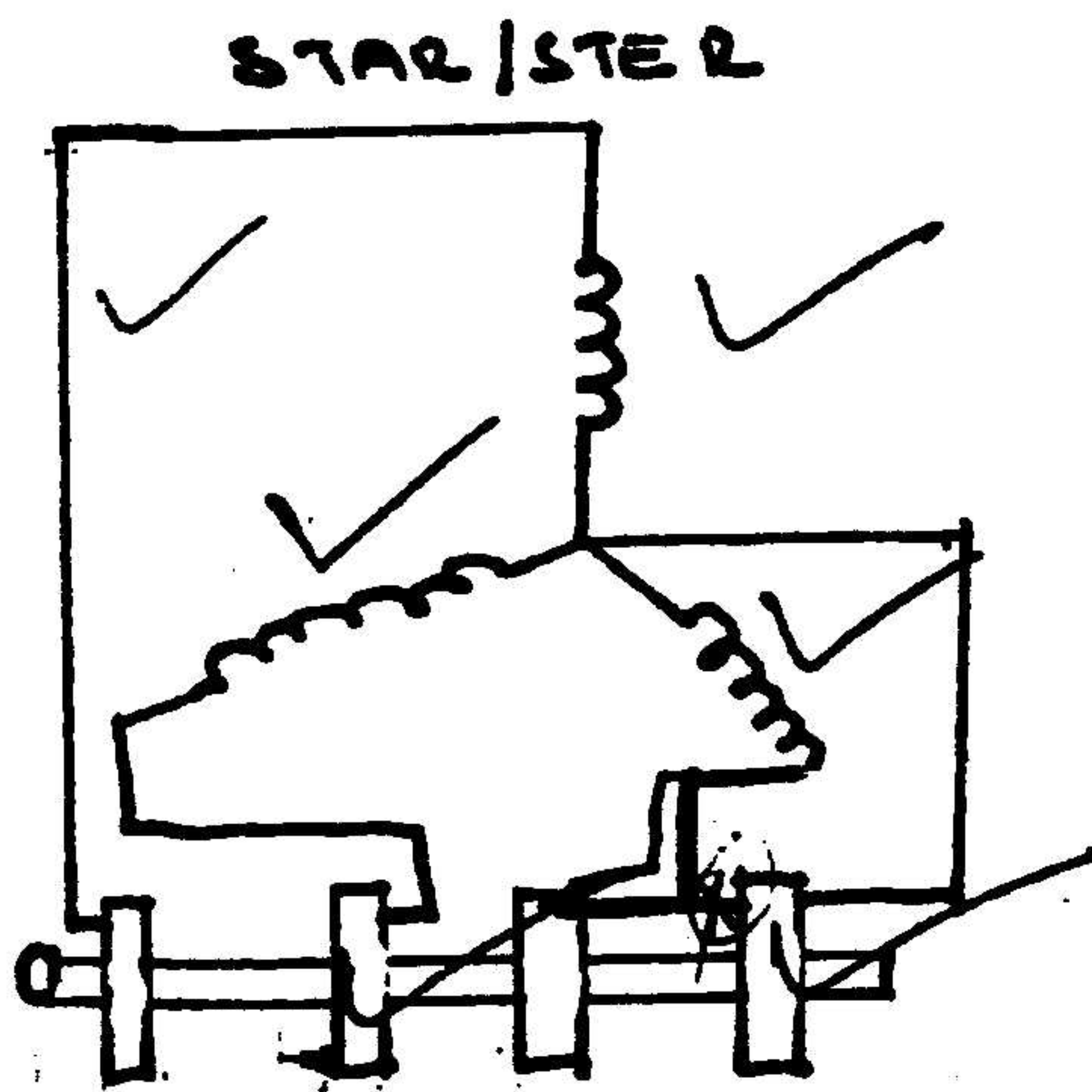


VRAAG 3 / QUESTION 3


3.1.1

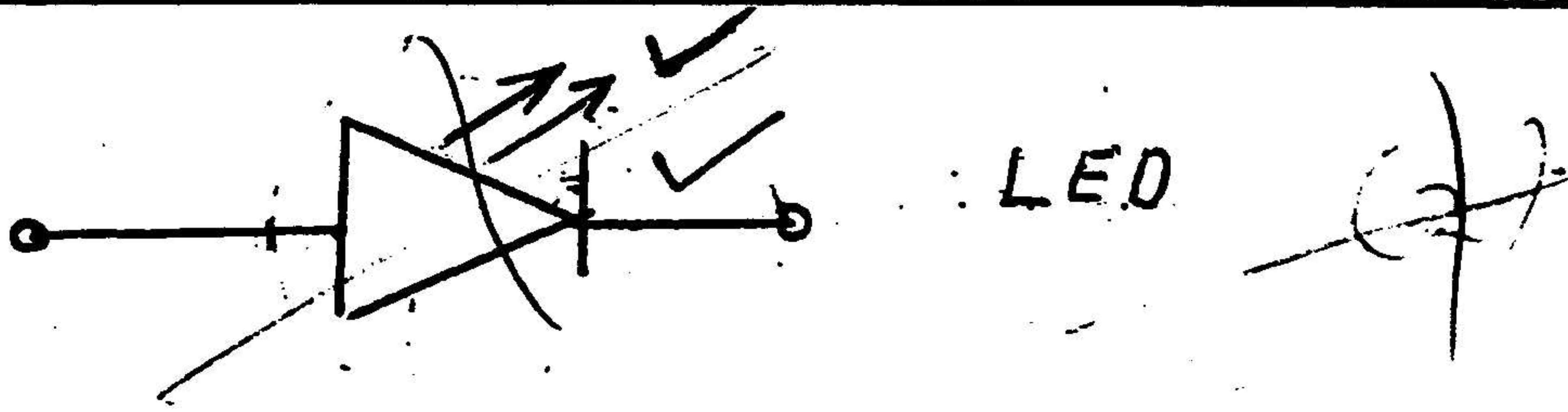


3.1.2

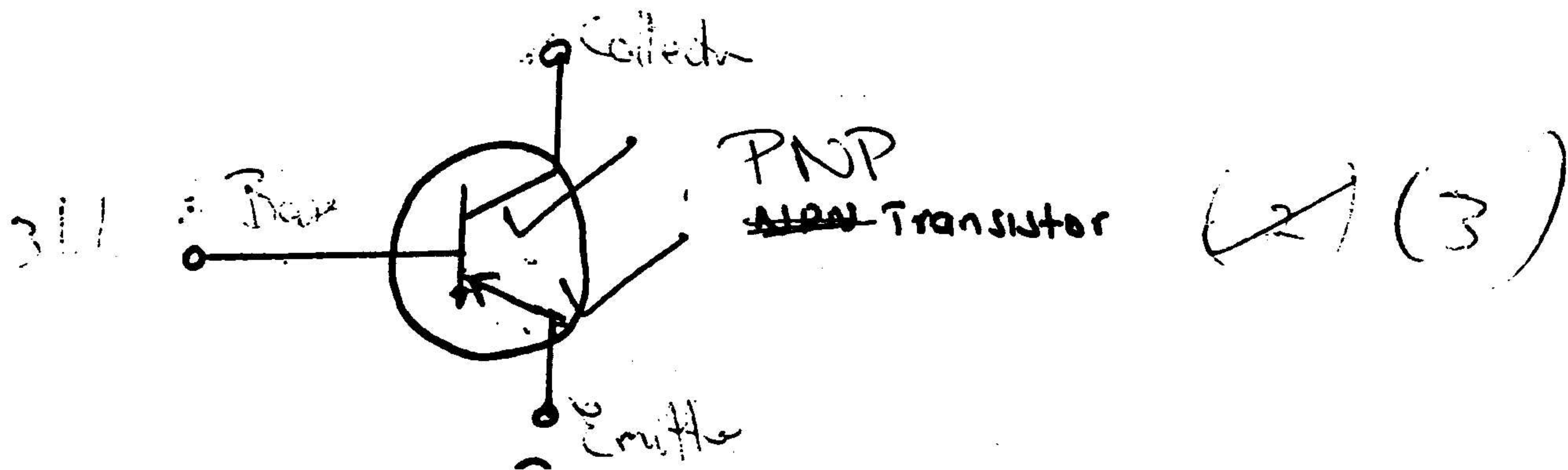

3.1.3

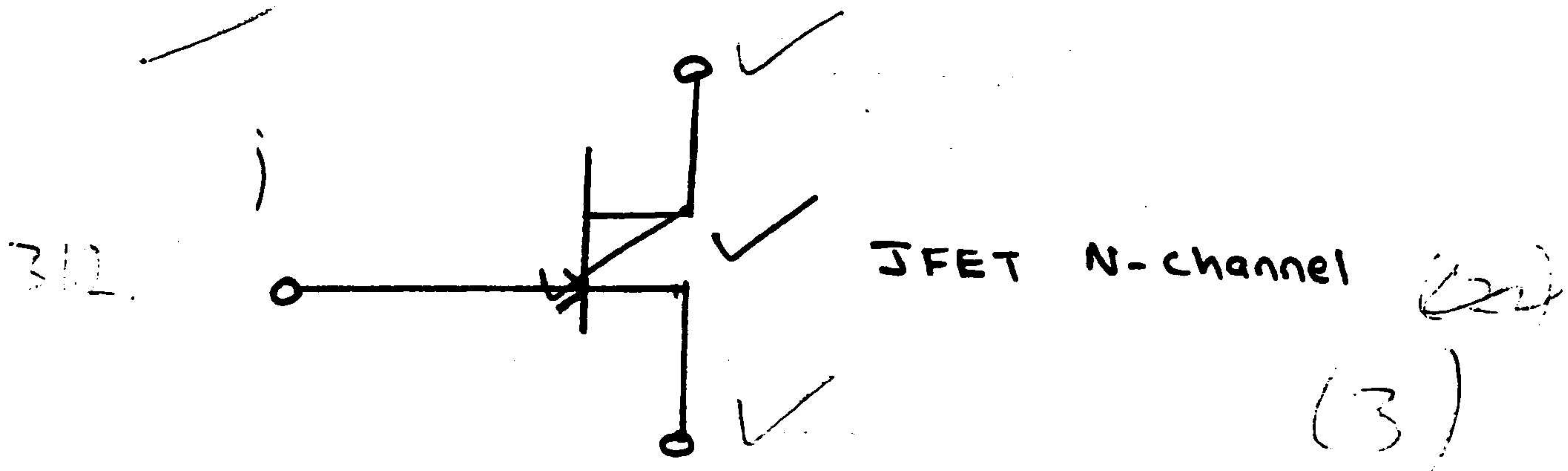


3.1.4

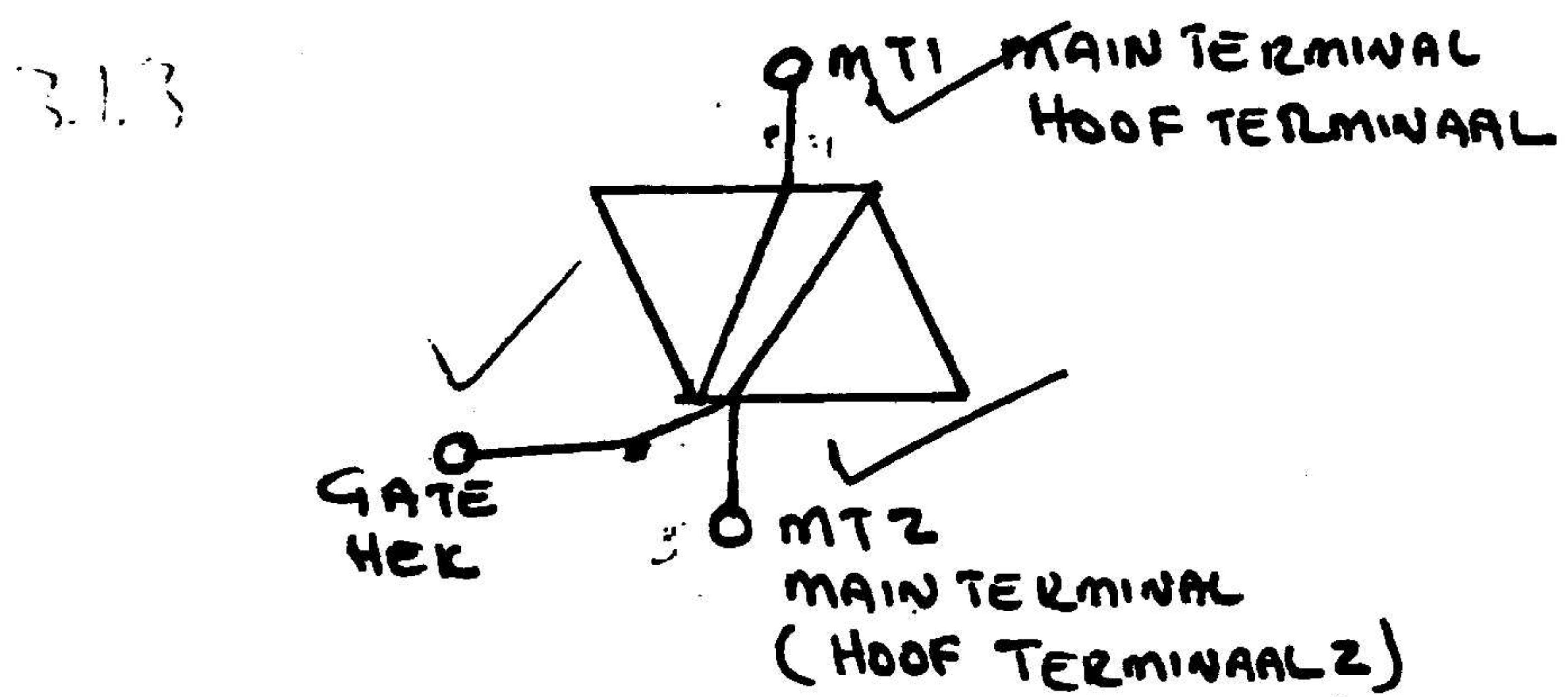


3.1.5

3.1.5

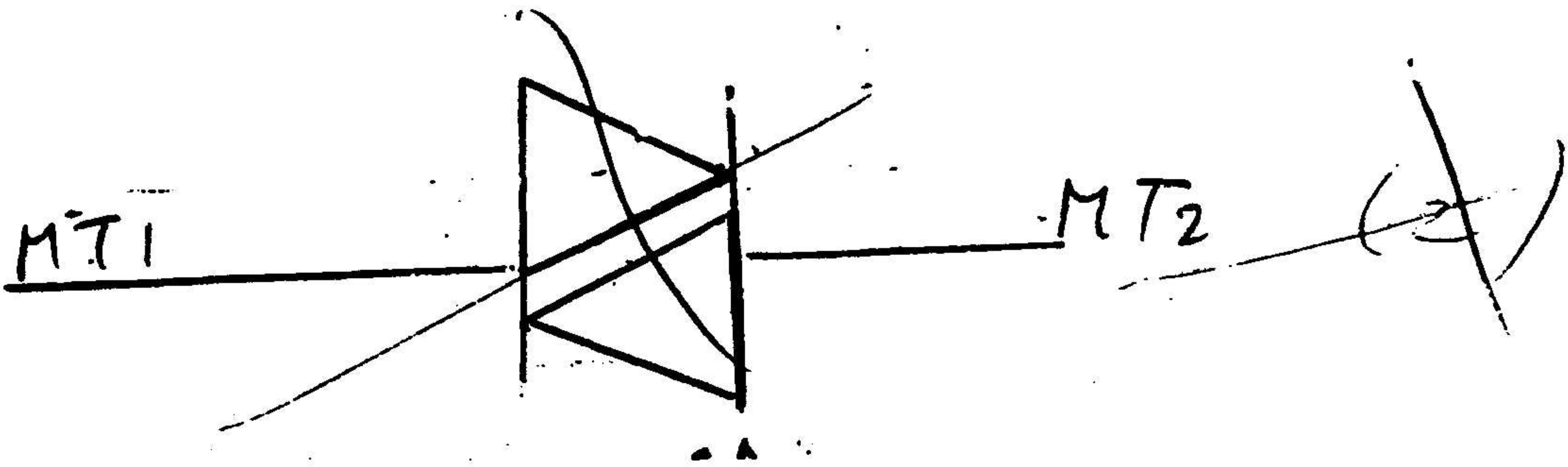


3.1.6

3.1.4

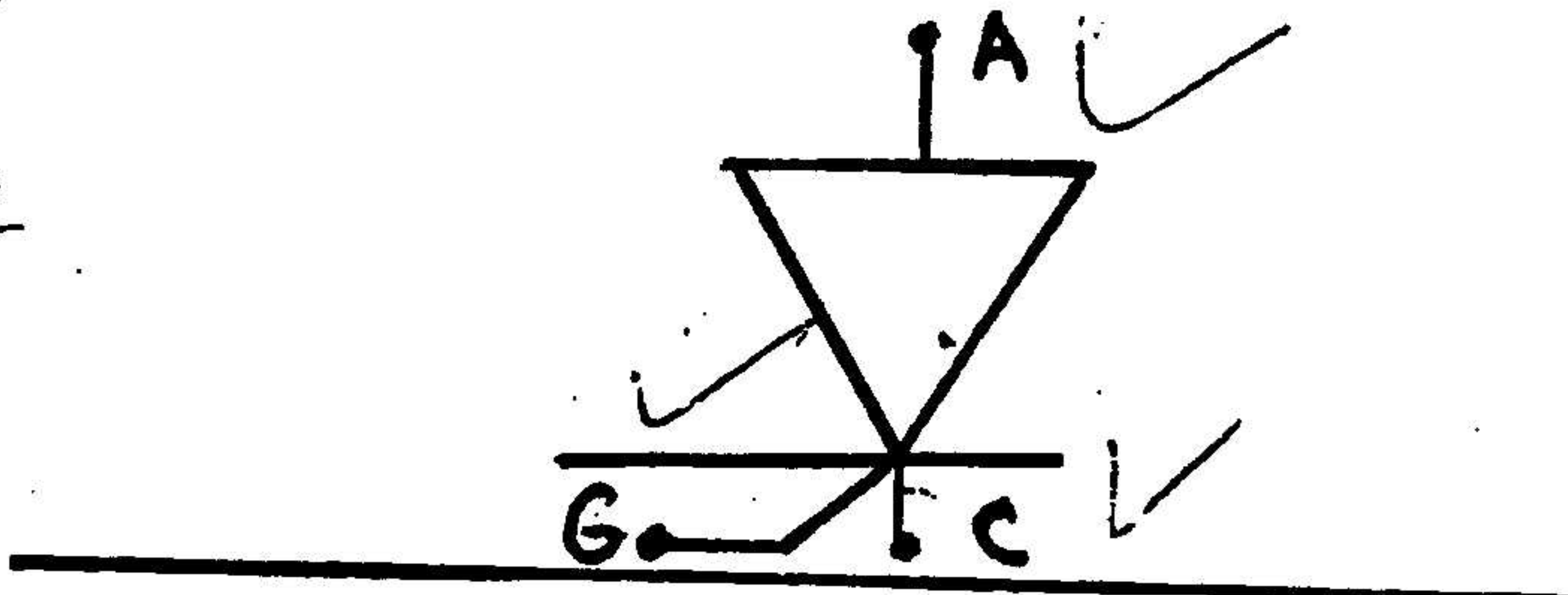


3.2

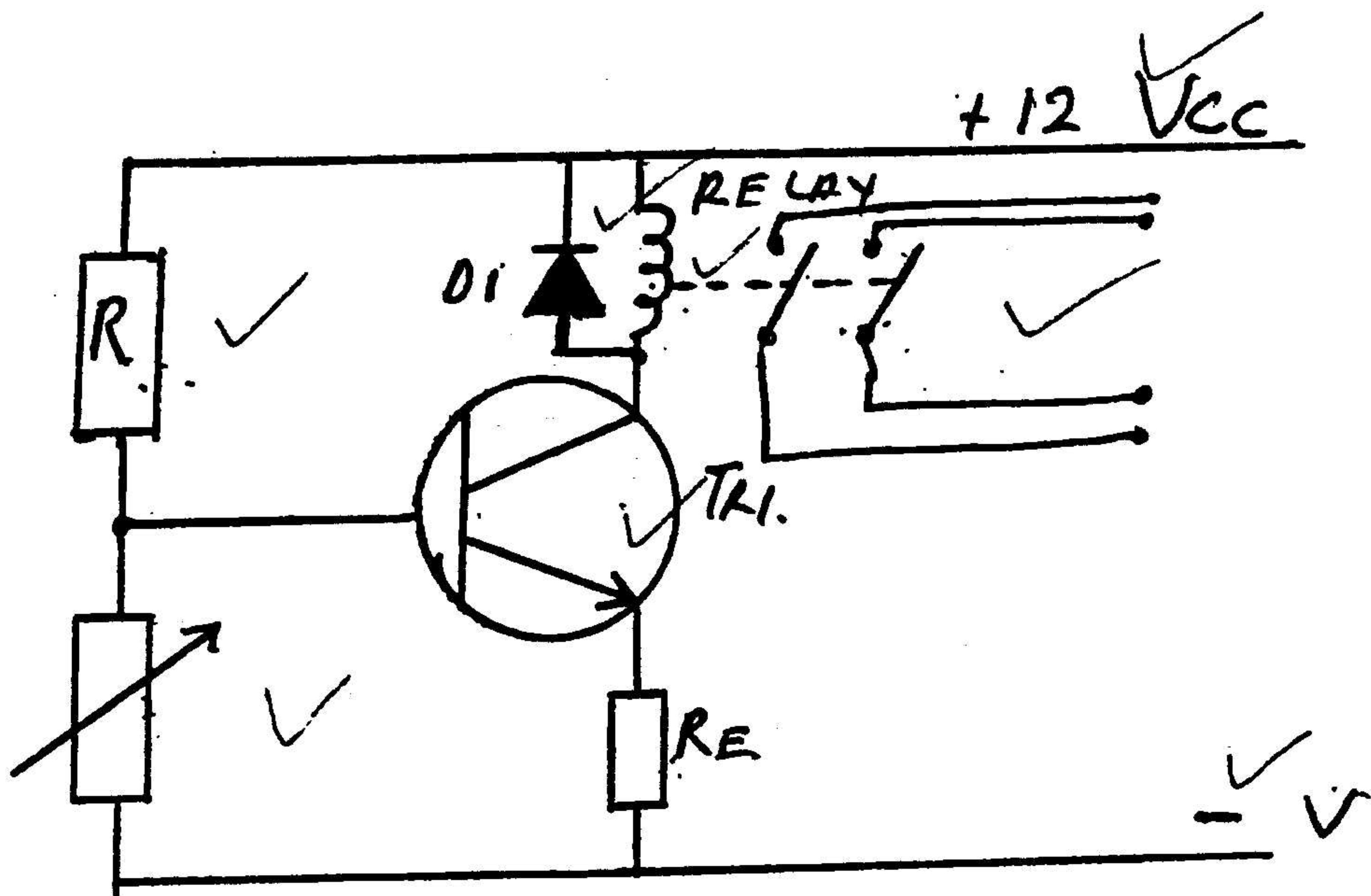

VRAAG 4 / QUESTION 4

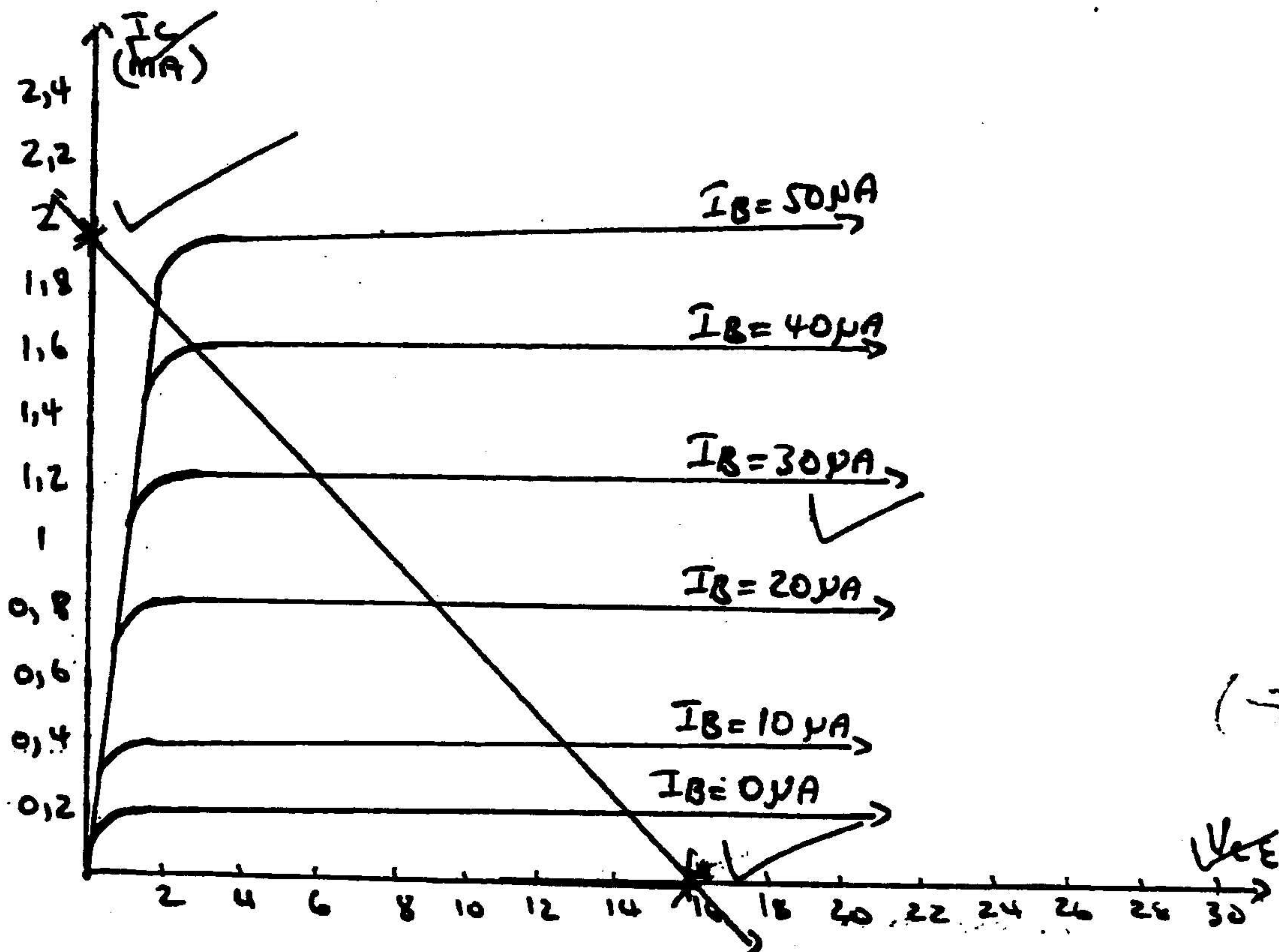4.1 Kirchhoff's law: $V_{CE} = V_{CC} = 16 \text{ V}$ ✓ (2)

$$I_C = \frac{V_{CC}}{R_C} = \frac{16 \text{ V}}{8000} = 0,002 \text{ A} = 2 \text{ mA} \quad (3)$$




- 4.2
- 1) A bulky size of the circuit
 - 2) More expensive
 - 3) Poor frequency response
 - 4) Heavy to carry

Any two ✓ ✓

(2)

- 4.3 Transformer coupled amplifier / Transformator koppeling
Versterker

(20)

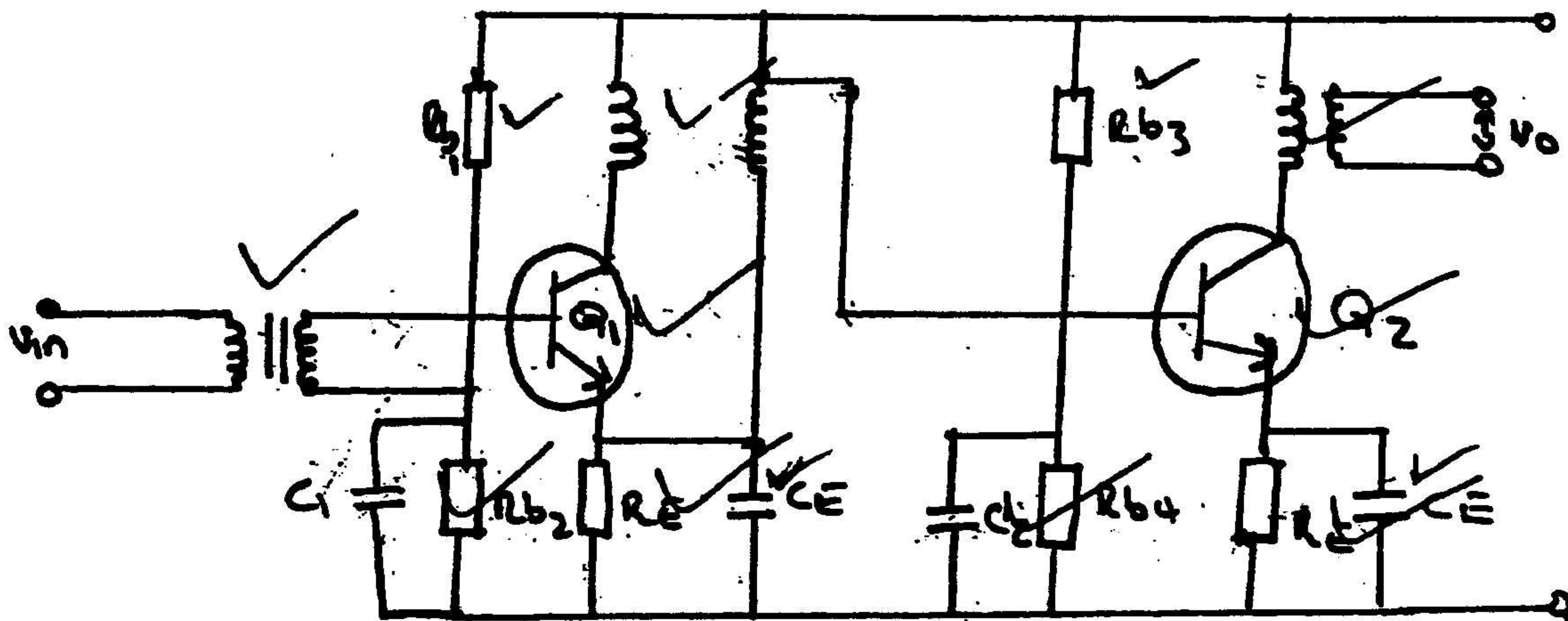

- Improved power consumption can be obtained since the transformer is used for impedance matching ✓
- The lower the frequency applied to the transformer, the lower its reactance and the higher the frequency, the higher the reactance ✓
- The amount of the gain can also be controlled by applying certain frequencies to different configurations of the transformer coupled amplifier. ✓


Amplification technique: The output of one amplifier feeds the input of the other amplifier. A transformer is used to interconnect the stages. ✓

R_1 , R_2 , R_3 and R_4 provide Q_1 and Q_2 with the required biasing ✓
 R_e is used for the temperature compensation ✓
 C_E is used for emitter stabilisation ✓

Verbeterde kragverbruik en meer doeltreffend omdat die transformator gebruik vir impedansie aanpassing.
 Dit is wanneer die impedansie van een kring gelyk is aan die impedansie van kring waaraan dit gekoppel word.


R_1 , R_2 , R_3 en R_4 voorsien Q_1 en Q_2 van die vereiste basis spanning
 R_e word gebruik as temperatuurkompensasie
 C_E word gebruik vir emitter stabilisering

5.1

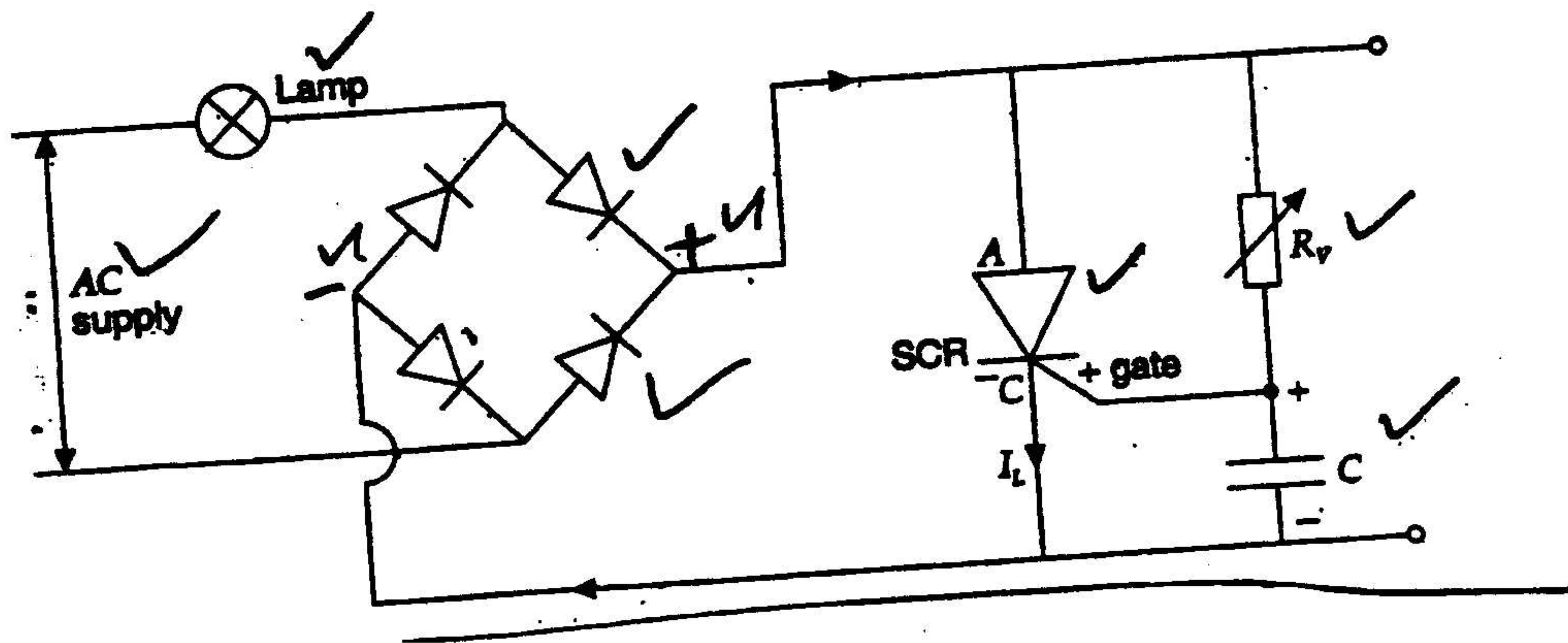


5.2 Measuring voltages / spanning ✓
 Calculate of Currents / stroom ✓
 Calculate of Frequency / Frekwensie ✓
 Phase difference between two signals ✓


5.3.1

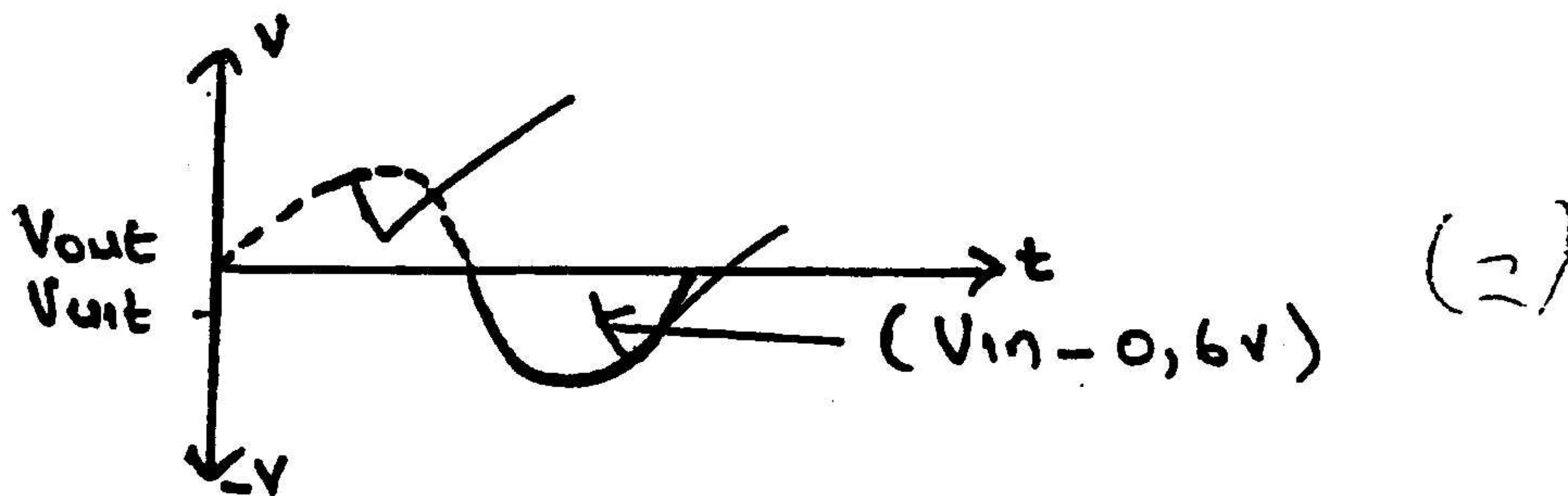


5.3.2

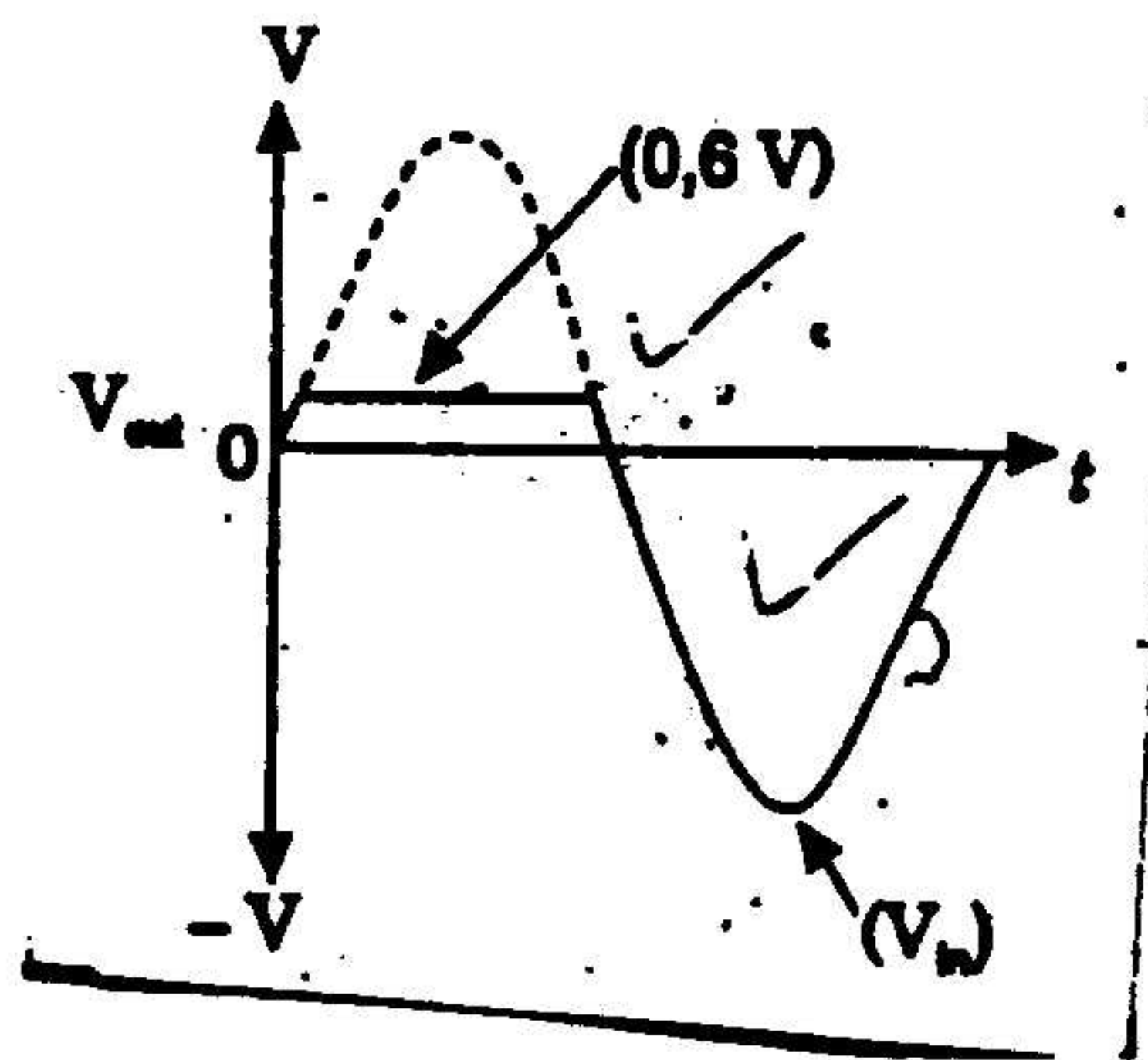

5.3.3

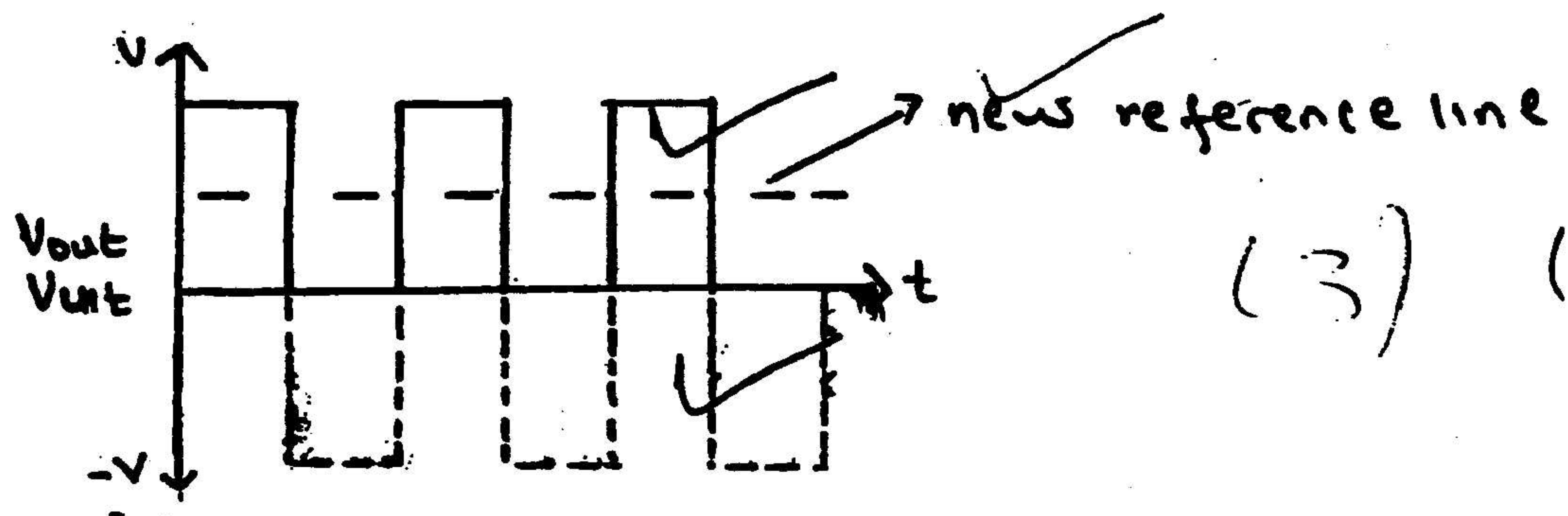

5.3.4

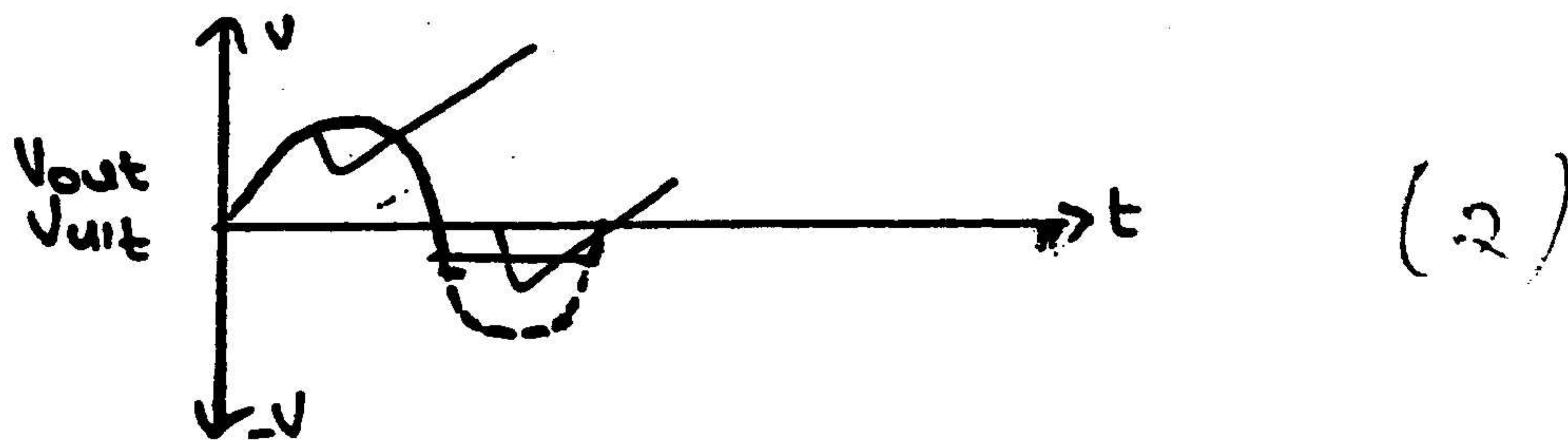


[21]

VRAAG 6 / QUESTION 6

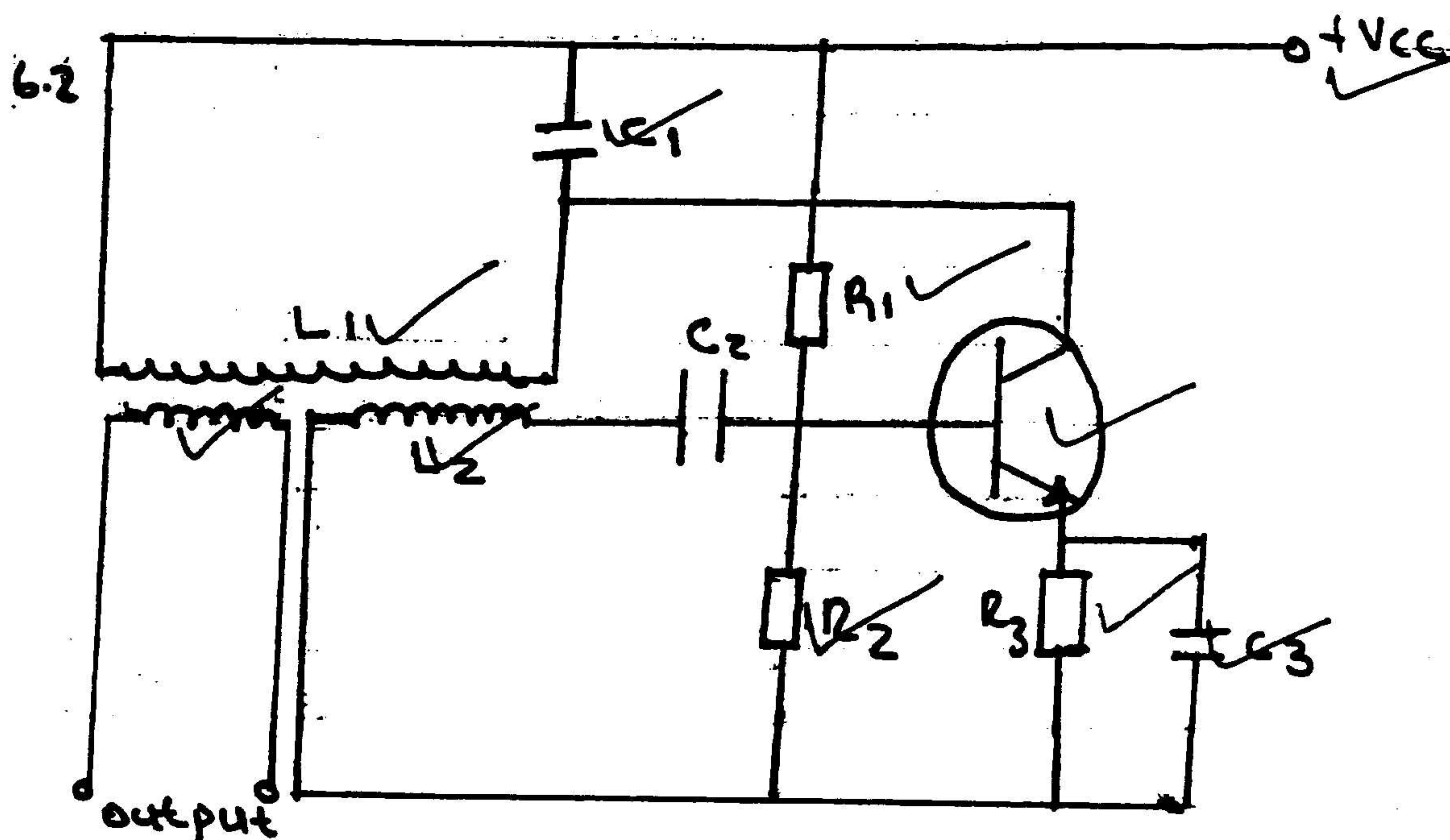6.1

- Differentiation in component values caused through temperature and fatigue
 - A change in impedance of the transistor
 - A change in supply voltage
 - Transients
- Any three (3)




When the supply is switched on, the biasing circuit will allow the transistor to switch on and conduct. ✓
 The current will thus flow through the inductor L_1 . As the current flow ✓
 through L_1 , an e m f is induced in L_2 . The positive induced e ✓


m f in L 2 will switch the transistor more on, resulting in the increase of the current in the inductor L 1 while C 1 charges. More current will be induced in L 2 and the transistor will be driven into saturation state. The charge on the capacitor C 1 is almost that of VCC.

VRAAG 7 / QUESTION 7

7.1

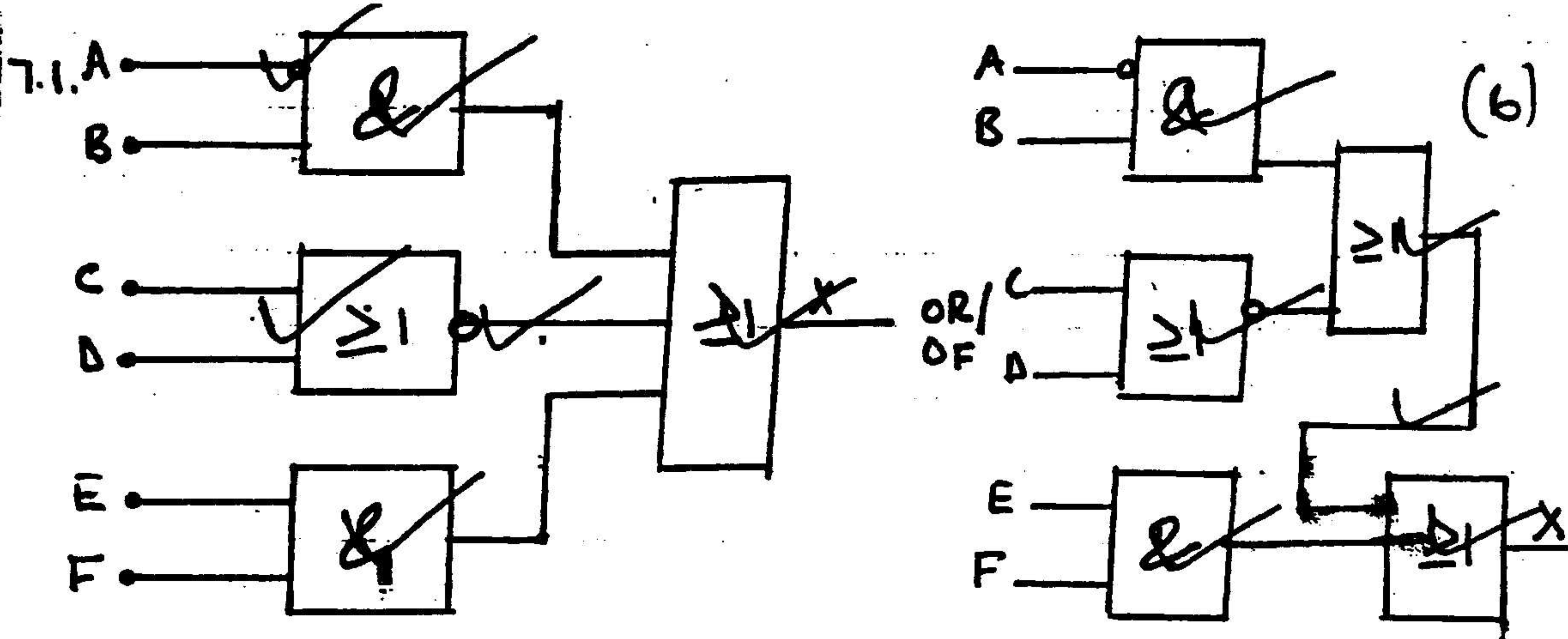

7.2

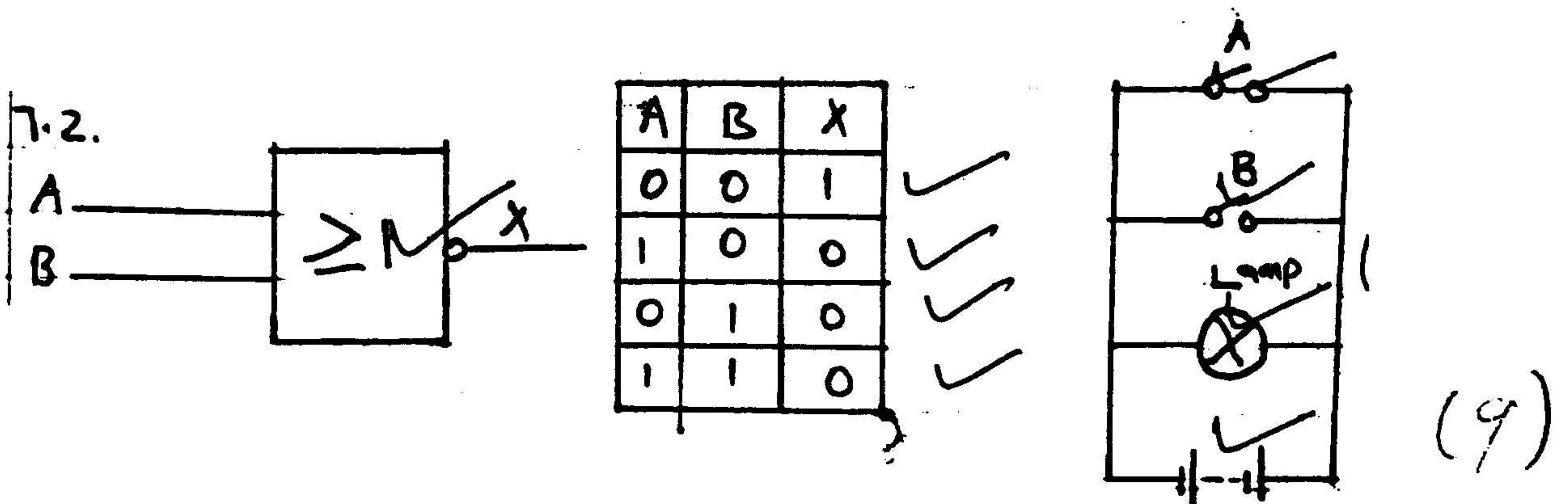

$$7.3 \quad (X + Y) (X + Z) = X + YZ$$


$$\begin{aligned} F &= X X + XY + XY + YZ \checkmark \\ F &= X + (XY + XY) \checkmark + YZ \\ F &= X + XY \checkmark + YZ \\ &= X (1 + Y) + YZ \\ &= X (1) \checkmark + YZ \\ &= X + YZ \checkmark \end{aligned}$$

(6)

[21]

VRAAG 8 / QUESTION 8

8.1

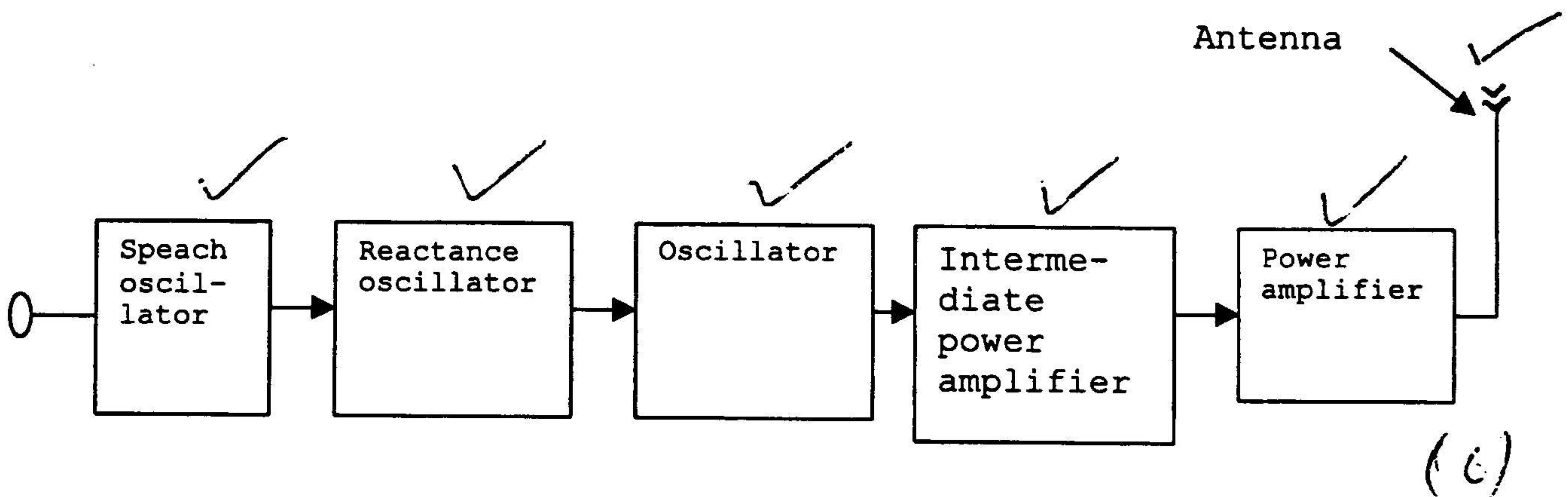

8.2

- 1) Make a solid study of the Oscilloscope textbook
- 2) Body must be earth
- 3) Probe must be in good condition
- 4) Use the lowest possible intensity
- 5) Prevent sharp light
- 6) Don't exceed maximum input voltage

(6)

- 1) Maak 'n deeglike studie van die ossilloskoophandboek
- 2) Sorg dat die ossilloskoopomhulsel goed geaard is
- 3) Isolاسie van toetsgeleiers in goeie toestand
- 4) Gebruik laagste moontlike intensiteit
- 5) Verhoed sterk lig by ossilloskoop
- 6) Moet nie maksimum spanninginset oorskry nie

$$8.3 \quad (1) \quad V \text{ peak} = \text{Volts/Division} \times \text{No of division} \checkmark \\ = 5 \text{ V/cm} \times 8 \text{ cm} \checkmark$$

$$= 40 \text{ V} \quad \checkmark$$

$$\begin{aligned} (11) \text{ Vrms/Wgk} &= V_p \times 0,707 \quad \checkmark \\ &= 40 \times 0,707 \quad \checkmark \\ &= 28,28 \text{ V} \quad \checkmark \end{aligned}$$

(6)

[18]

VRAAG 9 / QUESTION 9

9.1 Foam / Skuim CO₂ $\checkmark$ (2)

9.2 Do not wear loose clothes

Do not operate the machine without the teacher's permission

Do not play in the workshop

Do not enter or leave the workshop without the teacher's permission.

(4)

(Any acceptable answer)

- 9.3
- 1) Having sex with an infected person without using a condom
 - 2) Sharing needles or syringes with an infected person
 - 3) Through blood transfusion
 - 4) From infected mother to unborn child

[10] 100

(2)

[18]