

X025/201

NATIONAL
QUALIFICATIONS
2009

TUESDAY, 9 JUNE
1.00 PM – 3.30 PM

ELECTRONIC AND
ELECTRICAL
FUNDAMENTALS
INTERMEDIATE 2

100 marks are allocated to this paper.

Answer **all** questions in Section A (50 marks).

Answer **two** questions from Section B (25 marks each).

A Datasheet is provided for question 10(c).

In all your answers to questions requiring calculations, all working **must** be shown.





Section A

Attempt all the questions in this section (50 marks)

1. Convert the following numbers.

- | | | | |
|-----|--------------|------------------------|------------|
| (a) | 10001101_2 | binary to decimal | 2 |
| (b) | 171_{10} | decimal to hexadecimal | 2 |
| (c) | $B7_{16}$ | hexadecimal to binary | 2 |
| | | | (6) |

2. Identify the following circuit symbols.

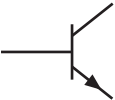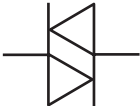- | | | |
|-----|--|------------|
| (a) |  | 2 |
| (b) |  | 2 |
| | | (4) |

3. For the circuit shown in Figure Q3 below, determine:

- | | | |
|-----|------------------------|------------|
| (a) | the voltage V_{CD} ; | 2 |
| (b) | the voltage V_{BC} . | 2 |
| | | (4) |

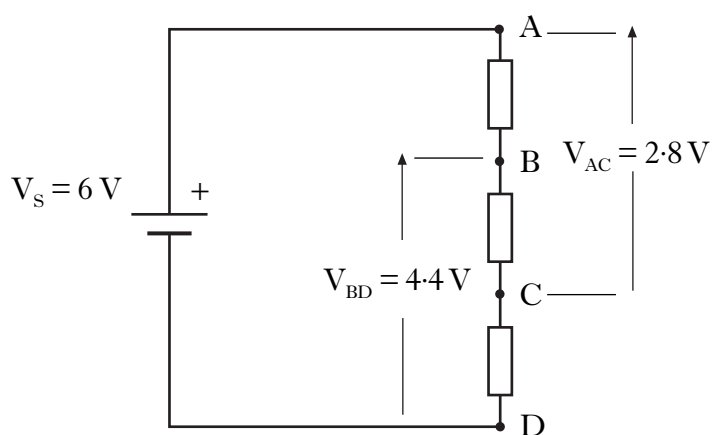


Figure Q3

4. Referring to Figure Q4 shown below,

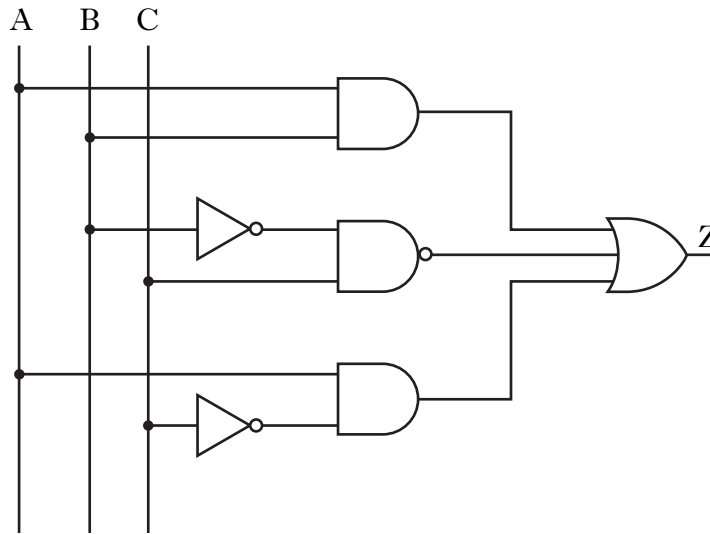


Figure Q4

- | | |
|--|------------|
| (a) determine the Boolean expression for output Z; | 3 |
| (b) draw the truth table for the circuit. | 4 |
| | (7) |

5. For the circuit shown in Figure Q5 below:

- | | |
|--|------------|
| (a) identify the circuit configuration; | 1 |
| (b) state the circuit voltage gain in terms of input and output voltages; | 2 |
| (c) state the circuit voltage gain in terms of resistors R_1 and R_2 ; | 2 |
| (d) state the phase relationship between input and output voltage. | 1 |
| | (6) |

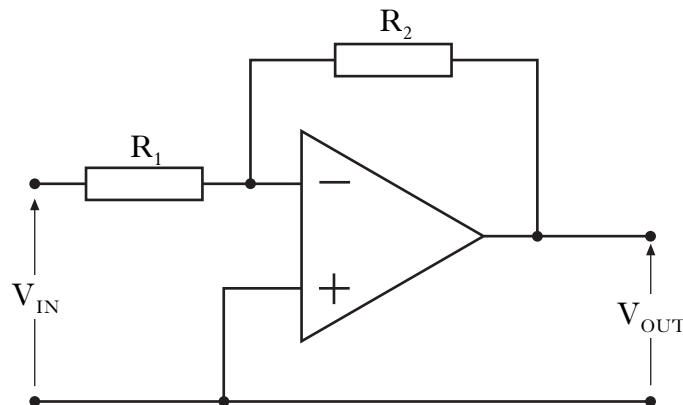


Figure Q5

[Turn over

6. Figure Q6(a) and Figure Q6(b) show a current carrying conductor placed between the poles of a magnet. For each Figure, sketch the resultant magnetic field around each conductor.

State whether you are using 'conventional' or 'electron' current flow.



2

Figure Q6(a)



2

(4)

Figure Q6(b)

7. With reference to the circuit shown in Figure Q7:

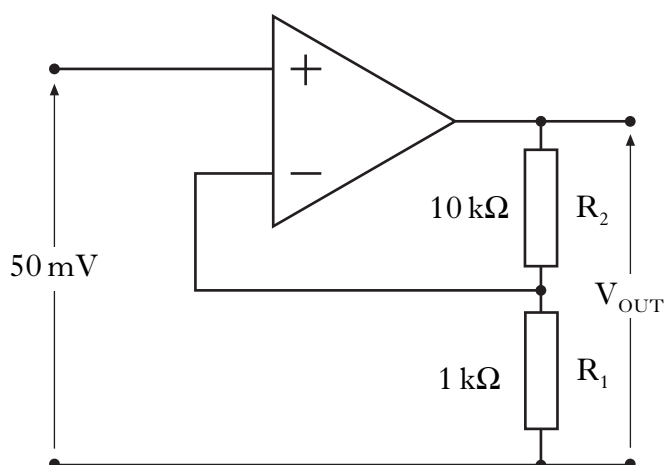


Figure Q7

- identify the circuit configuration;
- calculate the circuit gain;
- calculate the output voltage;
- state the phase relationship between input and output voltages.

1

2

2

1

(6)

8. (a) For the Boolean expression,

$$Z = (A + B).(A + \bar{B} + C).(B + \bar{C})$$

draw the logic circuit diagram.

3

- (b) Show by diagram how two 2-input AND gates can be connected to perform the logic function of a 3-input AND gate.

2

(5)

9. For the circuit shown in Figure Q9, determine:

- (a) the voltage across resistor R_2 ;

1

- (b) the current through resistor R_2 ;

1

- (c) the value of resistor R_1 ;

1

- (d) the voltage across resistor R_4 ;

2

- (e) the value of resistor R_4 ;

1

- (f) the supply current.

2

(8)

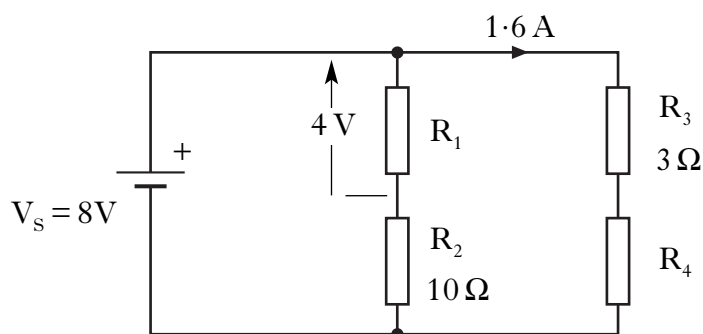


Figure Q9

[Turn over

Section B

Attempt any TWO questions in this section (50 marks)

Each question is worth 25 marks

10. (a) For the circuit shown in Figure Q10(a),

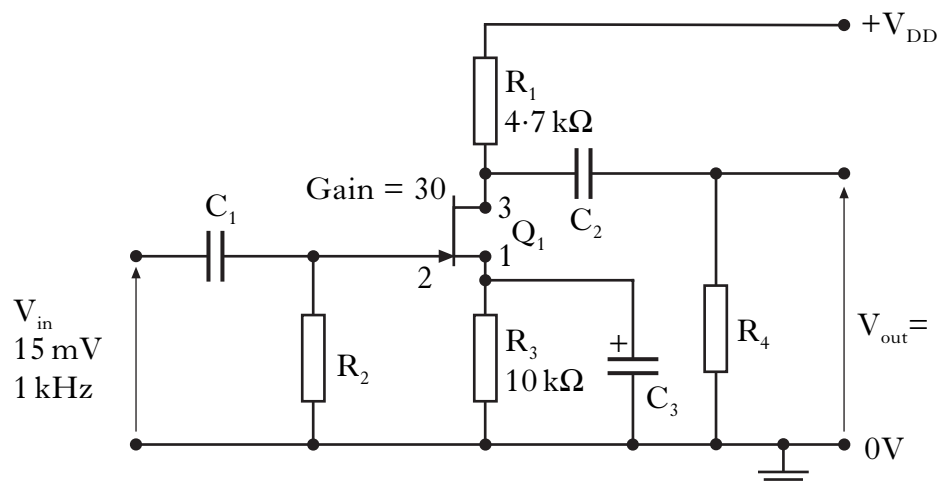


Figure Q10(a)

- (i) name the circuit and its configuration; 2
 - (ii) name terminals 1, 2 and 3 of component Q_1 ; 3
 - (iii) calculate the output voltage; 2
 - (iv) sketch the input and output waveforms to show the phase relationship between them (numerical values are not required); 2
 - (v) state the purpose of capacitors C_1 and C_2 . 2
- (b) With reference to the circuit shown in Figure Q10(b):

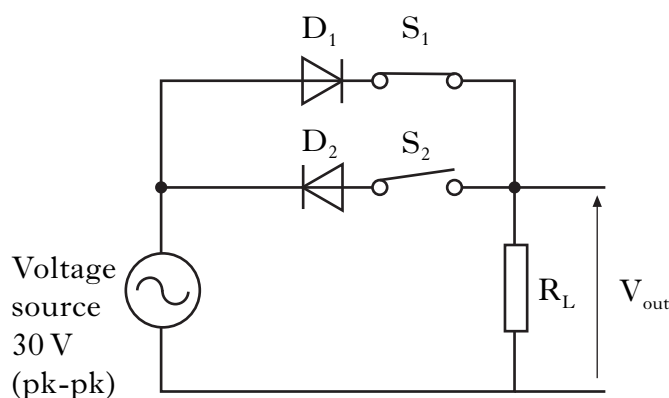


Figure Q10(b)

- (i) what is the purpose of the diode D_1 ? 1
- (ii) explain the operation of the circuit when switch S_1 is closed and switch S_2 is open; 2
- (iii) the forward voltage drop of diodes D_1 and D_2 is 0.7 V. Sketch the input and output waveforms showing peak values for each. 4

10. (continued)

- (c) The waveform shown in Figure Q10(c) is fed into the input of the circuit shown in Figure Q10(d).

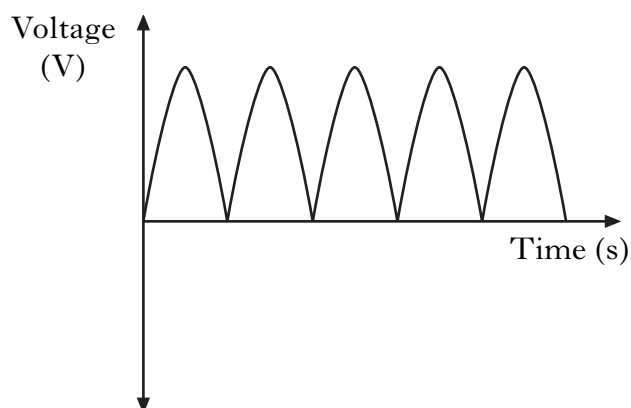


Figure Q10(c)

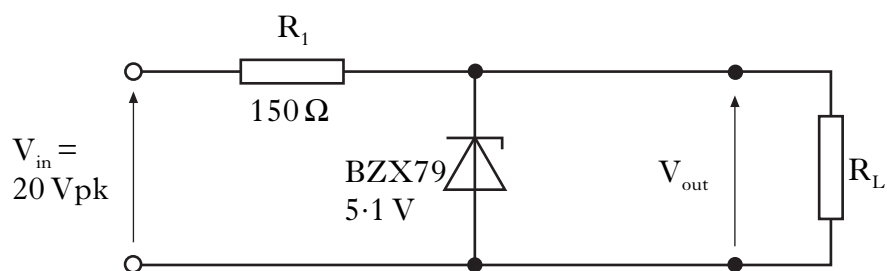


Figure Q10(d)

- | | |
|--|-------------|
| (i) State the operating voltage of the zener diode. | 1 |
| (ii) Sketch the output waveform across the load resistor R_L . | 3 |
| (iii) Using the data sheet provided: | |
| (A) determine the maximum power rating of the zener diode; | 1 |
| (B) calculate the maximum current rating of the zener diode. | 2 |
| | (25) |

[Turn over]

11. (a) An a.c. sinusoidal voltage is given by $e = 20 \sin \theta$ mV.

- (i) State the maximum value of this voltage. 1
- (ii) Calculate the rms value of the voltage. 2
- (iii) Calculate the instantaneous value of the voltage when $\theta = 45^\circ$. 2

(b) The coil AB shown on Figure Q11(b) has an effective length of 4.5 m. The conductor moves at a constant speed of 6 m s^{-1} through a uniform magnetic field of flux density 0.45 T .

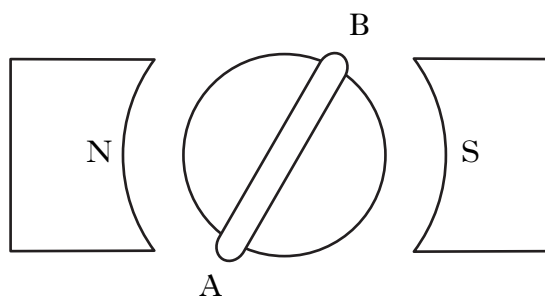


Figure Q11(b)

- (i) Determine the induced emf when the coil cuts the magnetic field at 45° . 2
- (ii) State the angle relative to the vertical at which the minimum voltage will occur. 1

11. (continued)

(c) For the circuit diagram in Figure Q11(c),

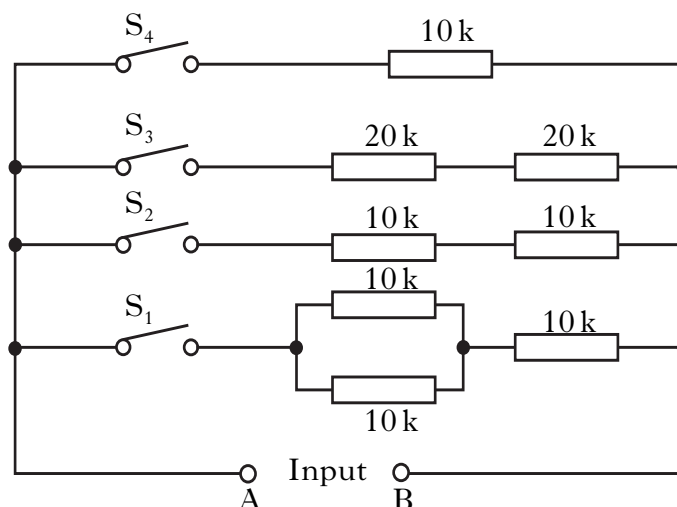


Figure Q11(c)

- | | | |
|-------|---|------|
| (i) | Calculate the total resistance of the circuit when switches S_1 and S_2 are closed and switches S_3 and S_4 are open. | 2 |
| (ii) | Calculate the total resistance when switches S_2 and S_3 are closed and switches S_1 and S_4 are opened. | 2 |
| (iii) | Which switches should be left open to give the highest resistance between A and B? | 1 |
| (iv) | Which switches should be closed to give the lowest resistance between A and B? | 2 |
| (v) | If only one switch can be closed, which switch would give the lowest current? | 2 |
| (d) | (i) Calculate the power dissipated in a $15\text{ k}\Omega$ resistor when the current is 2 mA . | 2 |
| | (ii) Calculate the energy used, in joules, if this current continues for 45 minutes. | 2 |
| | (iii) The power rating of the resistor is 0.125 W . Calculate the maximum current that can flow through the resistor without exceeding the power rating. | 4 |
| | | (25) |

[Turn over

12. (a) Add the following binary numbers.


(i) $1011_2 + 1001_2$

2

(ii) $0101_2 + 0011_2$

2

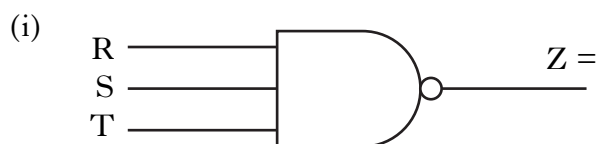(b) State the Boolean expression and construct the truth table for the following logic gates.



4



4

(c) Draw, using BS symbols, the logic diagram for the following Boolean expression.

$$Z = (R + \bar{S} + \bar{T}).(R + S + \bar{T}).(R + \bar{S} + T)$$

4

(d) The circuit shown in Figure Q12(d) is used to control a warning lamp, which operates when the output of the circuit is on.

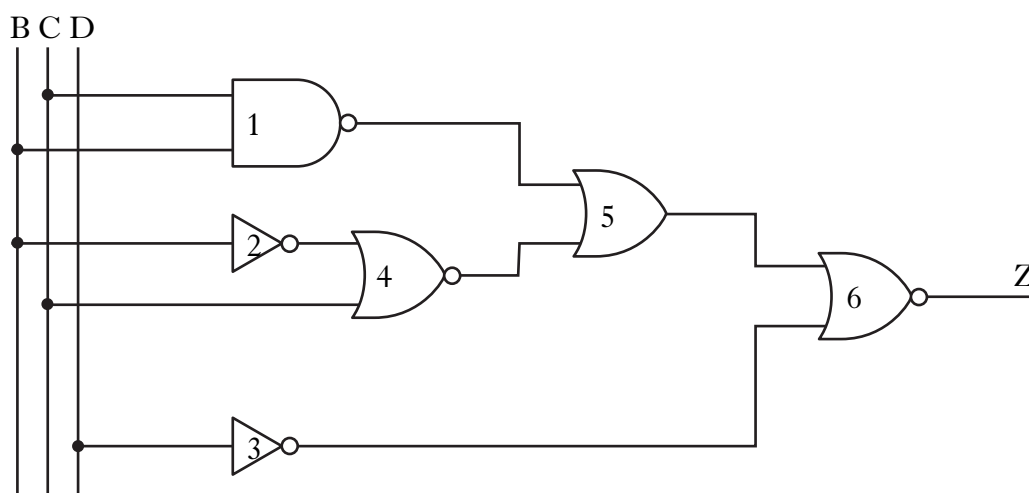


Figure Q12(d)

(i) Determine the Boolean expression for the circuit.

3

(ii) Construct the truth table for the circuit.

4

(iii) Use the truth table to determine an alternative Boolean expression.

2

(25)

[END OF QUESTION PAPER]

[BLANK PAGE]

[BLANK PAGE]

X025/202

NATIONAL
QUALIFICATIONS
2009

TUESDAY, 9 JUNE
1.00 PM – 3.30 PM

ELECTRONIC AND
ELECTRICAL
FUNDAMENTALS
INTERMEDIATE 2
Datasheet for Q10(c)



Datasheet for Question 10 (c)

ZENER DIODES

<i>Diode Series</i>	<i>Zener Voltage Range (V)</i>	<i>Power (mW)</i>	<i>Non Repetitive Power (W)</i>	<i>Max Junction Temp (°C)</i>
UDZ (SMT)	2.02 – 36.87	200	N/A	N/A
PLVA400A	5.2 – 7.0	400	30	175
BZX79	2.4 – 75	500	30	200
BZX85	2.7 – 200	1300	N/A	175
BZX284(SMT)	2.4 – 75	400	N/A	N/A
BZT03C	6.2 – 150	3.25W	N/A	N/A
1N5333	3.9 – 120	5W	N/A	N/A
1N53	3.3 – 200	5W	N/A	N/A
BZY93	8.2 – 75	20W	N/A	N/A

LEDs

<i>Diode Type</i>	<i>Part No</i>	<i>I_F</i> mA (max)	<i>V_F</i> V (typ)	<i>V_R</i> V (max)	<i>Intensity @ 10 mA mcd</i>		<i>View Angle (deg)</i>	<i>Peak wavelength (nm)</i>
					<i>min</i>	<i>max</i>		
Red	L424HDT	25	2	5	0.5	3.2	100	700
H E red	L424DT	30	2	5	3.2	12.5	100	625
Pure orange	L424NDT	30	2	5	3.2	12.5	100	610
Green	L424GDT	25	2.2	5	1.3	8	100	565
Yellow	L424YDT	30	2.1	5	1.3	8	100	590

[END OF DATASHEET]