

X036/301

NATIONAL
QUALIFICATIONS
2009

MONDAY, 8 JUNE
1.00 PM – 4.00 PM

TECHNOLOGICAL
STUDIES
HIGHER

100 marks are allocated to this paper.

Answer **all** questions in Section A (60 marks).

Answer **two** questions from Section B (20 marks each).

Where appropriate, you may use sketches to illustrate your answer.

Reference should be made to the Higher Data Booklet (2008 edition) which is provided.



SECTION A

Attempt all the questions in this Section. (Total 60 marks)

1. A combinational logic system controls the air-conditioning system in a gym. A time clock (C), a temperature sensor (T) and an override switch (S) provide input signals to the combinational-logic system.

The completed truth table for the combinational-logic system is shown in Figure Q1.

Time Clock (C)	Temperature Sensor (T)	Override Switch (S)	Air Conditioner (Z)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Figure Q1

- (a) Referring to the truth table in Figure Q1, write a Boolean expression for the air conditioner (Z) in terms of the three inputs C, T and S. 2
- (b) Draw the logic diagram for the air conditioner, using only AND, OR and NOT gates. 3
- (c) Draw an equivalent logic circuit using only NAND gates. Simplify where possible. 2

The logic system is supplied by a 9V battery. TTL and CMOS integrated circuits (ICs) are available.

- (d) (i) State which type of IC would be more suitable for this application. 1
- (ii) State **two** advantages of this type of IC. 1
- (9)**

2. Figure Q2 shows a circuit for controlling a motor connected to a fan.

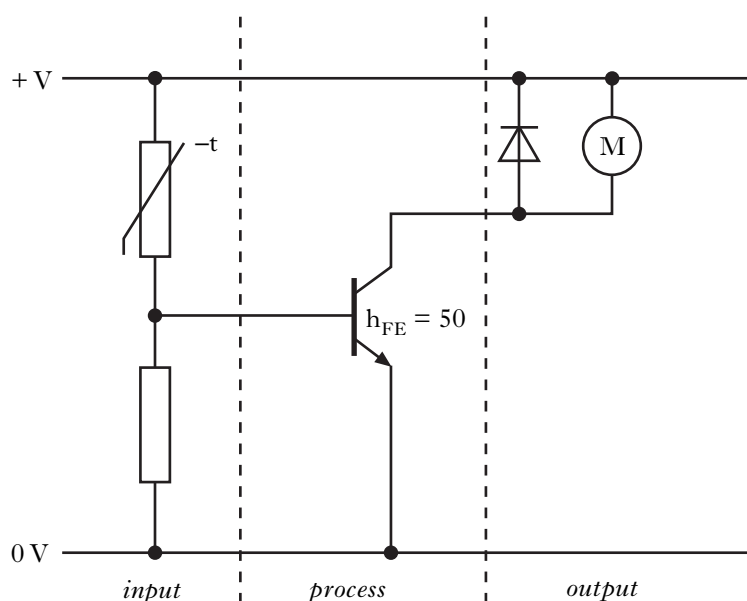


Figure Q2

- (a) State the name of the protective component in the circuit and explain its function. 1
- (b) Explain the function of the circuit by describing how the *input* sub-system responds to increasing temperature, and how the resulting signal from the *input* sub-system affects the *process* and *output* sub-systems. 3

It is found that a current gain of 1500 is necessary for the circuit to function satisfactorily. The required gain can be achieved by adding a second transistor to the circuit.

- (c) (i) Redraw the circuit showing this new arrangement of two transistors. 3
- (ii) State the name of this arrangement of two transistors.
- (iii) Calculate the required current gain of the additional transistor. 3

An alternative circuit that functions correctly uses a single MOSFET transistor.

- (d) Describe the main difference in the operation of a MOSFET transistor compared with a bipolar transistor. 1
- (8)**

[Turn over

3. A stepper motor rotates in steps of 7.5° and is controlled by pins 7, 6, 5 and 4 of a microcontroller. The program shown below controls the stepper motor. *Marks*

```
init:      let dirs = %11110000
main:      for b0 = 1 to 12
            let pins = %10100000
            pause 20
            let pins = %10010000
            pause 20
            let pins = %01010000
            pause 20
            let pins = %01100000
            pause 20
        next b0
    end
```

When the program is run, the stepper motor rotates in a clockwise direction.

- (a) (i) Calculate the number of degrees through which the stepper motor rotates. 2
- (ii) Calculate the length of time for which the stepper motor rotates. 2
- (b) Write a program in PBASIC that will rotate the stepper motor **anticlockwise** through 720° , with a 5 ms time delay between steps. 2

An alternative method of controlling a stepper motor involves the use of a stepper motor driver IC.

- (c) State **two** advantages of using a stepper motor driver IC as compared with the system described above. 2
- (6)**

4. Figure Q4 shows a load-extension graph for a tensile test on a sample of a special type of steel.

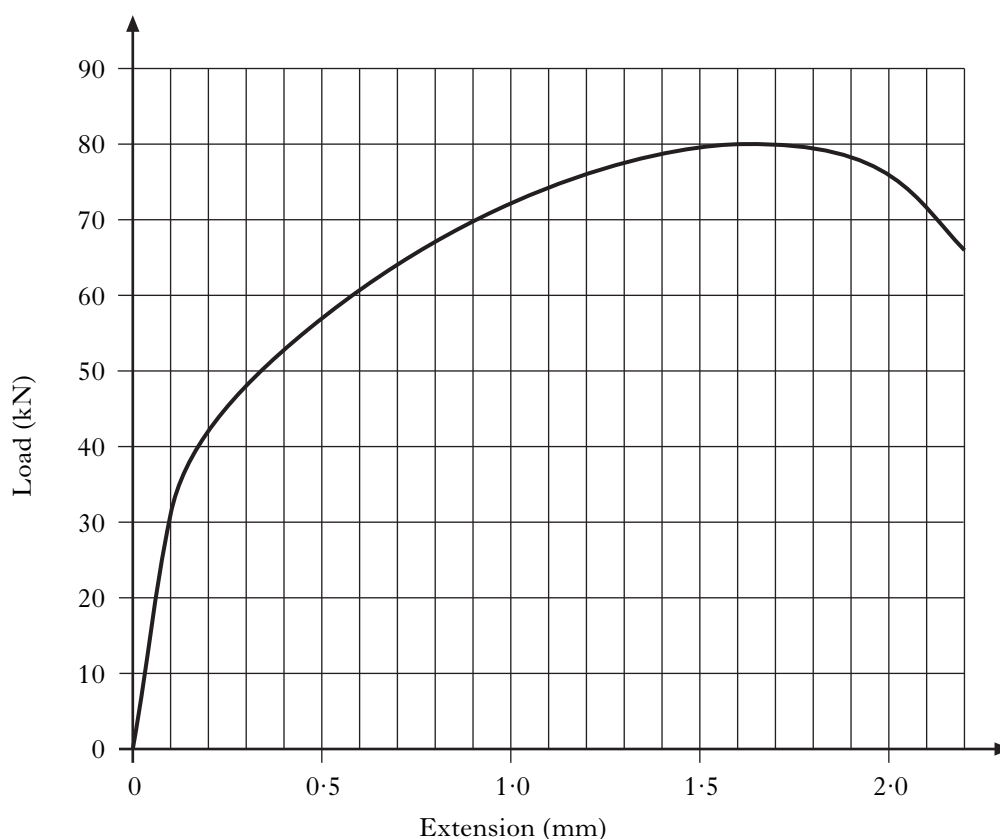


Figure Q4

- (a) State whether this material is brittle or ductile. 1

The test specimen was 50 mm long with a cross-sectional area of 80 mm^2 .

- (b) Calculate Young's Modulus for the material. 3

- (c) Calculate the **ultimate** tensile stress for the material. 1

A bar with a rectangular cross-section of $30 \text{ mm} \times 10 \text{ mm}$ is manufactured from the material. The bar is to be loaded in tension with a Factor of Safety of 6.

- (d) (i) Calculate the safe working stress for the bar. 1

- (ii) Calculate the safe working load for the bar. 1

(7)

[Turn over

- Marks*
5. A pharmaceutical manufacturing process requires accurate monitoring of temperatures. This is achieved by a system which includes two temperature sensors, a multiplexer, an analogue-to-digital converter and a microcontroller.
- (a) Describe the function of a multiplexer. 1
- A PBASIC sub-procedure *tempmonitor* uses the pre-written sub-procedure *adcread* to take a reading, and the pre-written sub-procedure *eevwrite* to store a reading in an EEPROM.
- Tempmonitor* takes a reading from sensor A and stores it in page 0 of the EEPROM. 1.8 seconds later *tempmonitor* takes a reading from sensor B and stores it in page 1 of the EEPROM.
- (b) Draw a flowchart to represent the sub-procedure *tempmonitor*. 6
- (7)

6. An energy-saving system is installed in a new office block. If the natural light level in an office is high enough, the lights turn off automatically. The control circuit is shown in Figure Q6.

Marks

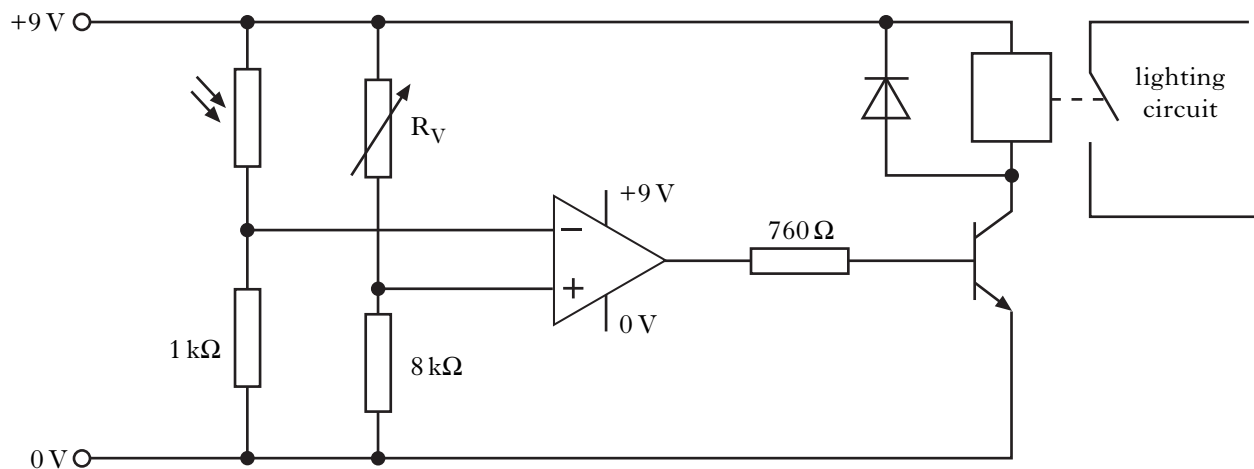


Figure Q6

(a) Calculate the value of R_V so that the light circuit switches off at 650 lux. 2

(b) Calculate the base current when the op-amp output is high. 2

The resistance of the relay is 15Ω .

(c) (i) Calculate the collector current when the transistor saturates. 1

(ii) Calculate the minimum current gain of the transistor. 1

(iii) State which of the transistors shown in the table below is most suitable for this circuit. 1

(7)

Device	$V_{CE(max)}$ (V)	$I_c(max)$ mA	h_{FE}
2N3704	30	600	100
BC108	25	200	100
BC142	60	1000	20
BC182	50	100	120
BC548b	30	100	220
BFY51	30	1000	40

[Turn over

7. A cycle-carrier is fitted to a car as shown in Figure Q7(a).

Marks

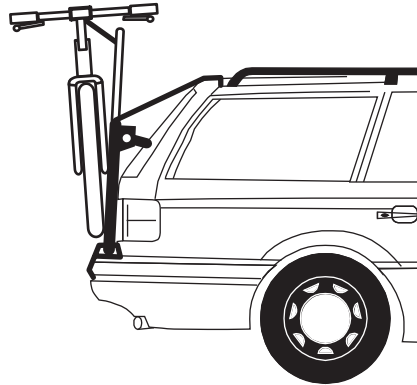


Figure Q7(a)

A simplified diagram of part of the cycle-carrier frame is shown in Figure Q7(b). To simplify calculations the frame has been rotated to the horizontal.

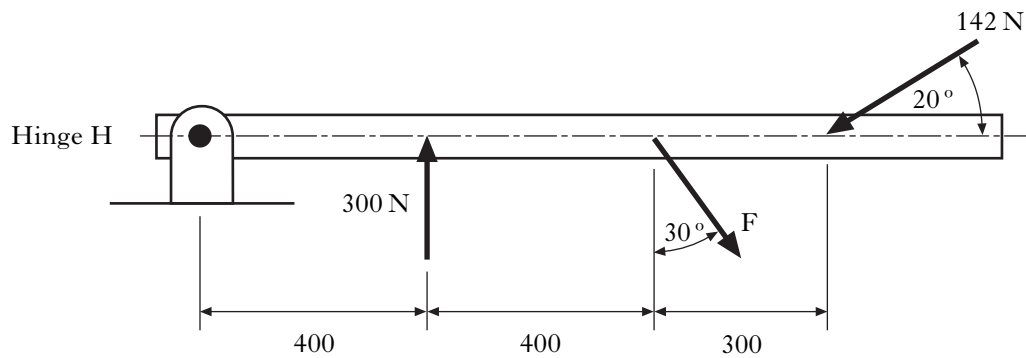


Figure Q7(b)

- (a) Calculate the magnitude of the force F . Use the Principle of Moments.
- (b) Calculate the **magnitude** and **direction** of the reaction at hinge H.

3
6
(9)

8. The circuit in Figure Q8(a) is used to control the speed of a motor, by varying the output voltage. It includes a processing sub-system, based on two op-amps, which processes four signals from a microcontroller.

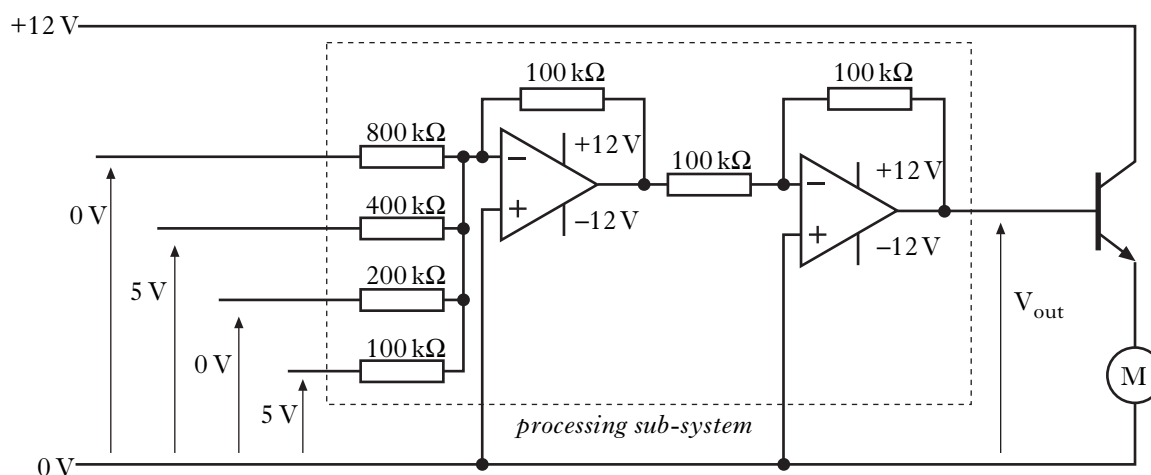


Figure Q8(a)

- (a) State the name of the processing sub-system. 1
- (b) Calculate the output voltage V_{out} for the input voltages shown in Figure Q8(a). 2

An alternative method of controlling motor-speed involves switching a motor on and off rapidly, and adjusting the lengths of the “on” and “off” time periods.

- (c) State the full name of this alternative method of controlling motor speed. 1

Figure Q8(b) shows a typical graph of the voltage against time.

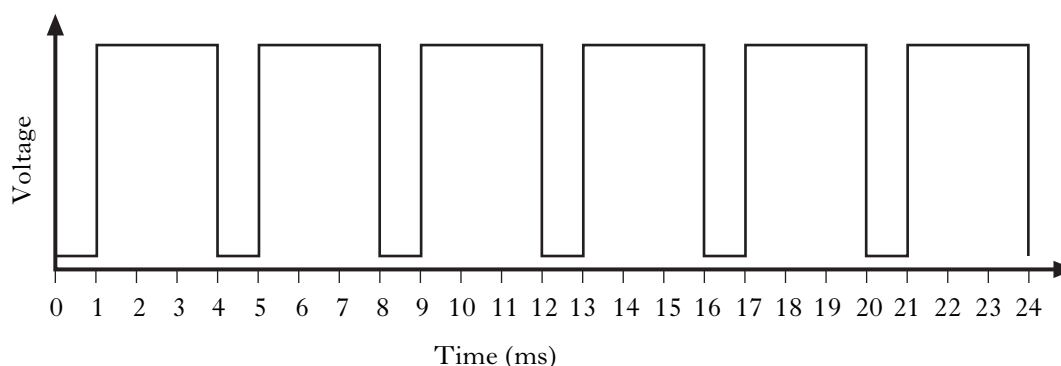


Figure Q8(b)

- (d) State the mark:space ratio for this graph. 1

In Figure Q8(b), the voltage is high for 75% of the time.

A motor initially at rest receives a voltage which is high for 20% of the time. After 0.5 seconds the voltage is high for 30% of the time. Every 0.5 seconds this percentage rises by 10% until the voltage is continuously high.

- (e) (i) State how the motor would respond to this changing signal. 2
- (ii) State the purpose of controlling the motor this way. (7)

[END OF SECTION A]

Attempt any TWO questions in this Section.

Each question is worth 20 marks.

9. An airbag safety system for a vehicle is shown in Figure Q9(a).

During a collision, four sensors each produce an analogue signal proportional to the crash severity. The airbag control unit determines which of the four airbags, if any, is to be deployed.

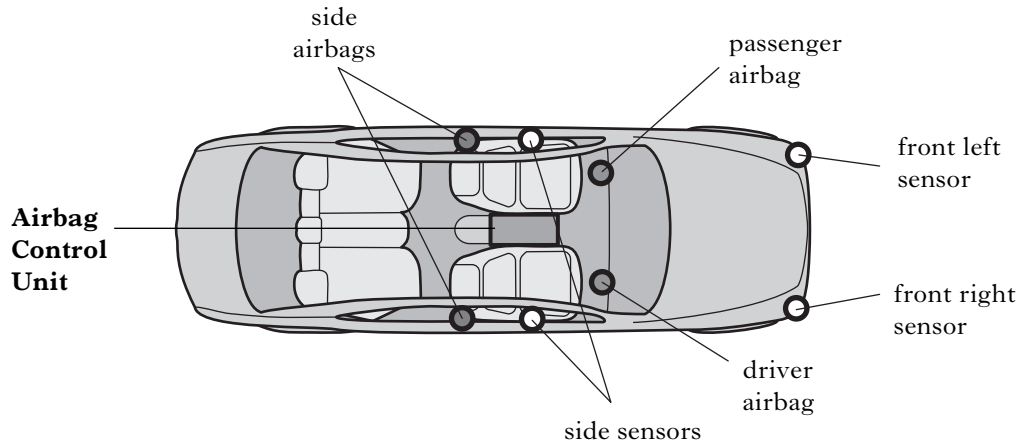


Figure Q9(a)

The airbag control unit conditions the four sensor signals before they are processed by an analogue-to-digital converter (ADC). A microcontroller uses the data from the ADC to control the airbags.

- (a) Draw a block diagram showing the main sub-systems of the airbag safety system. 3

The maximum output signal from one sensor is 6.8 V. The 8-bit ADC has a reference voltage of 5 V.

- (b) Draw an appropriate circuit based on op-amps to condition the signal from the sensor. Show all calculations and appropriate resistor values. 3

- (c) Calculate the voltage produced by the **sensor** when the binary signal from the ADC is 10110111. 2

9. (continued)

The sub-procedure *frontbags* controls the driver and passenger airbags. The flowchart for this sub-procedure is shown in Figure Q9(b).

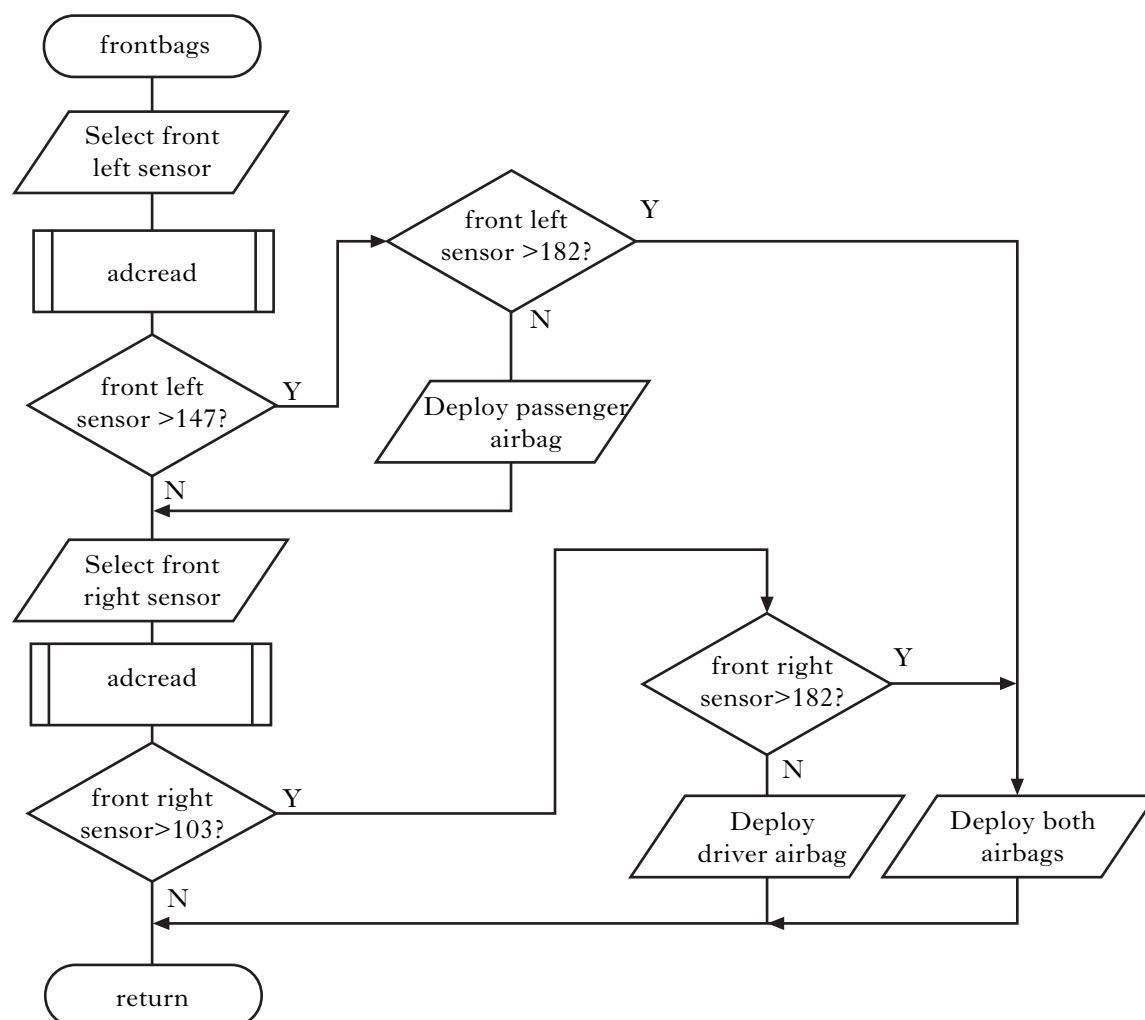


Figure Q9(b)

The front left sensor is selected when $\text{pin0} = 0$.
 The front right sensor is selected when $\text{pin0} = 1$.
 The passenger airbag is deployed when $\text{pin6} = 1$.
 The driver airbag is deployed when $\text{pin7} = 1$

The pre-written sub-procedure *adcread* reads a value from the ADC and stores it in the variable DATA.

(d) Write, in PBASIC, the sub-procedure *frontbags*.

9

[Turn over

9. (continued)

When the ignition is turned on the system performs a check of the sensors. If a fault is detected a warning lamp is illuminated. The op-amp-based system shown in Figure Q9(c) performs this check.

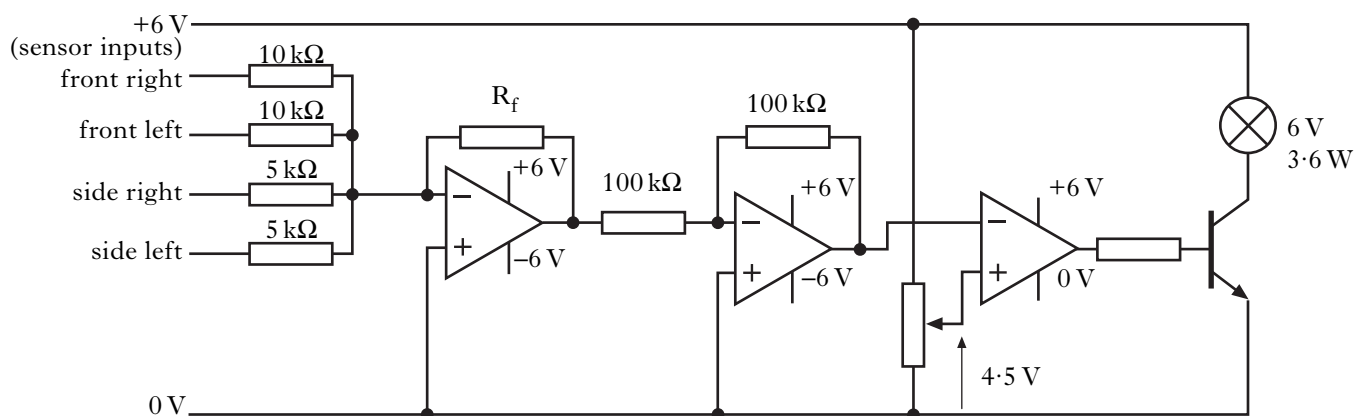


Figure Q9(c)

When the car is stationary a front sensor should have an output voltage of 1.2 V and a side sensor should have an output of 0.6 V.

- (e) Calculate an appropriate value for R_f so that the warning lamp will light if any of the sensors produce a test voltage output below the correct value. 2

A bipolar transistor-based driver circuit controls the lamp.

When a fault exists, the base current is 15.5 mA and the voltage across the lamp is 6 V.

- (f) Calculate the minimum current gain for the driver circuit. 1

(20)

10. A diagram of a lighting gantry above a stage is shown in Figure Q10(a).

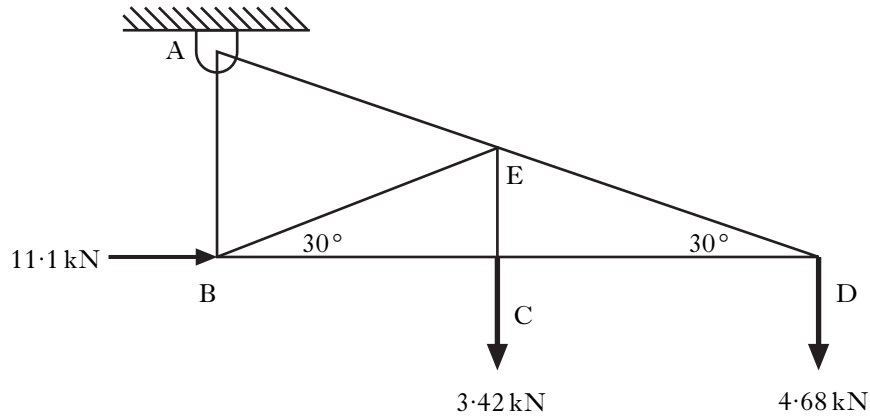


Figure Q10(a)

- (a) Using *nodal analysis* for the conditions shown in figure Q10(a), calculate the **magnitude** and **nature** of the forces in frame members DE, CD, BC and BE.

6

Spotlights are supported by a bracket at C as shown in Figure Q10(b). **Four** mild steel bolts support the bracket and are under tension.

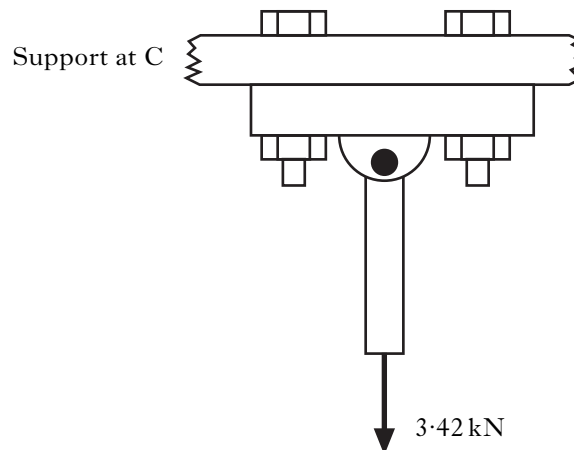


Figure Q10(b)

The tensile force in each of the four bolts due to tightening is 80 N, and the applied loading on the bracket is 3.42 kN. A Factor of Safety of 8 is applied.

- (b) Calculate the minimum diameter of each bolt.

5

[Turn over

10. (continued)

A motor in each spotlight moves a lens backwards or forwards to adjust the focus of the light. The motor is controlled by the circuit shown in Figure Q10(c).

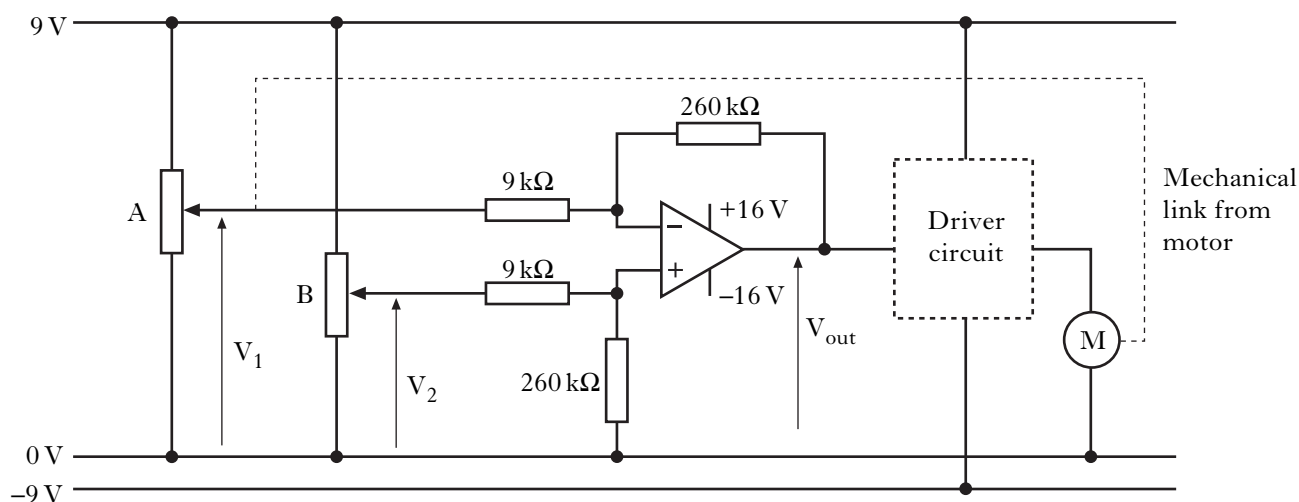


Figure Q10(c)

- (c) Sketch an appropriate transistor-based driver circuit that will control the motor.

Show **all** connections.

2

- (d) For the circuit shown in Figure Q10(c):

(i) calculate V_1 when V_2 is 4.08 V and V_{out} is 9.68 V;

2

(ii) calculate the maximum difference between V_1 and V_2 before the op-amp saturates.

1

When the motor is stationary, the setting of potentiometer B is altered.

- (e) Explain the operation of the control system after the setting of potentiometer B is altered.

2

It was found that the motor stopped before the spotlight reached the desired position.

- (f) Suggest a modification to the circuit that will enable the spotlight to reach the required position.

1

It was suggested that the op-amp configuration shown in Figure Q10(c) could be replaced by a comparator.

- (g) Describe **one** effect this would have on the motor.

1

(20)

11. A security system has a digital keypad as shown in Figure Q11(a). A correct code must be entered on the keypad to open a door. The logic system shown in Figure Q11(b) processes the signals from the keys 0–9. When a key is pressed a **high** signal is placed on an input line to the logic system, otherwise the signal on the input line is **low**.



Figure Q11(a)

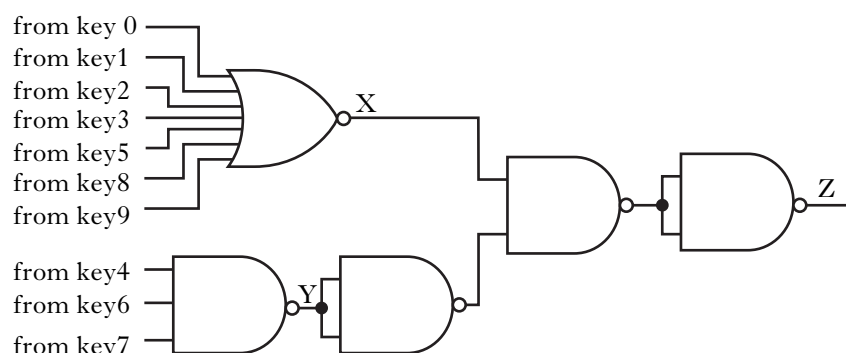


Figure Q11(b)

- (a) (i) Draw a truth table with signals X and Y as inputs, and signal Z as the output. 1
- (ii) **From the truth table**, write a Boolean expression for the output Z in terms of X and Y. 1
- (b) Explain what a user must do, in order to cause a high signal at Z. 1
- A high signal at Z opens the door; a low signal at Z closes the door.
- (c) State **two** disadvantages of this security system. 2

The logic system is to be replaced by a microcontroller-based system to process the signals from the keypad. Figure Q11(c) shows the connections to the microcontroller, enabling the twelve keys of the keypad to be monitored by a microcontroller with only eight I/O pins.

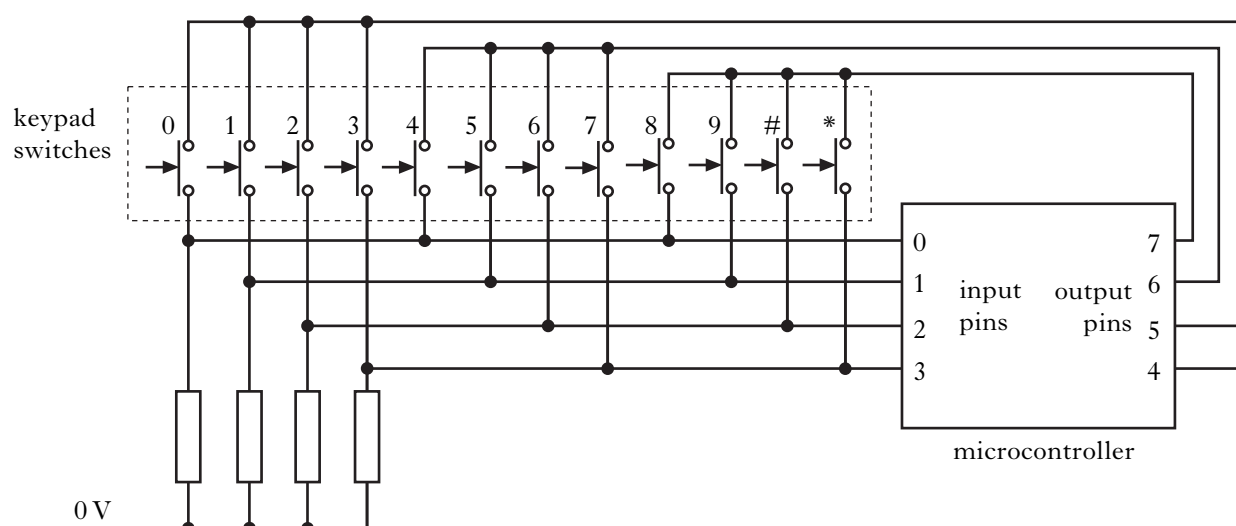


Figure Q11(c)

- (d) Referring to Figure Q11(c):
- (i) state which keys are monitored when output pin 6 of the microcontroller is high; 1
- (ii) state which input pin will go high if the # key is pressed when output pin 7 is high. 1

11. (continued)

The control program is represented by the flowchart shown in Figure Q11(d).

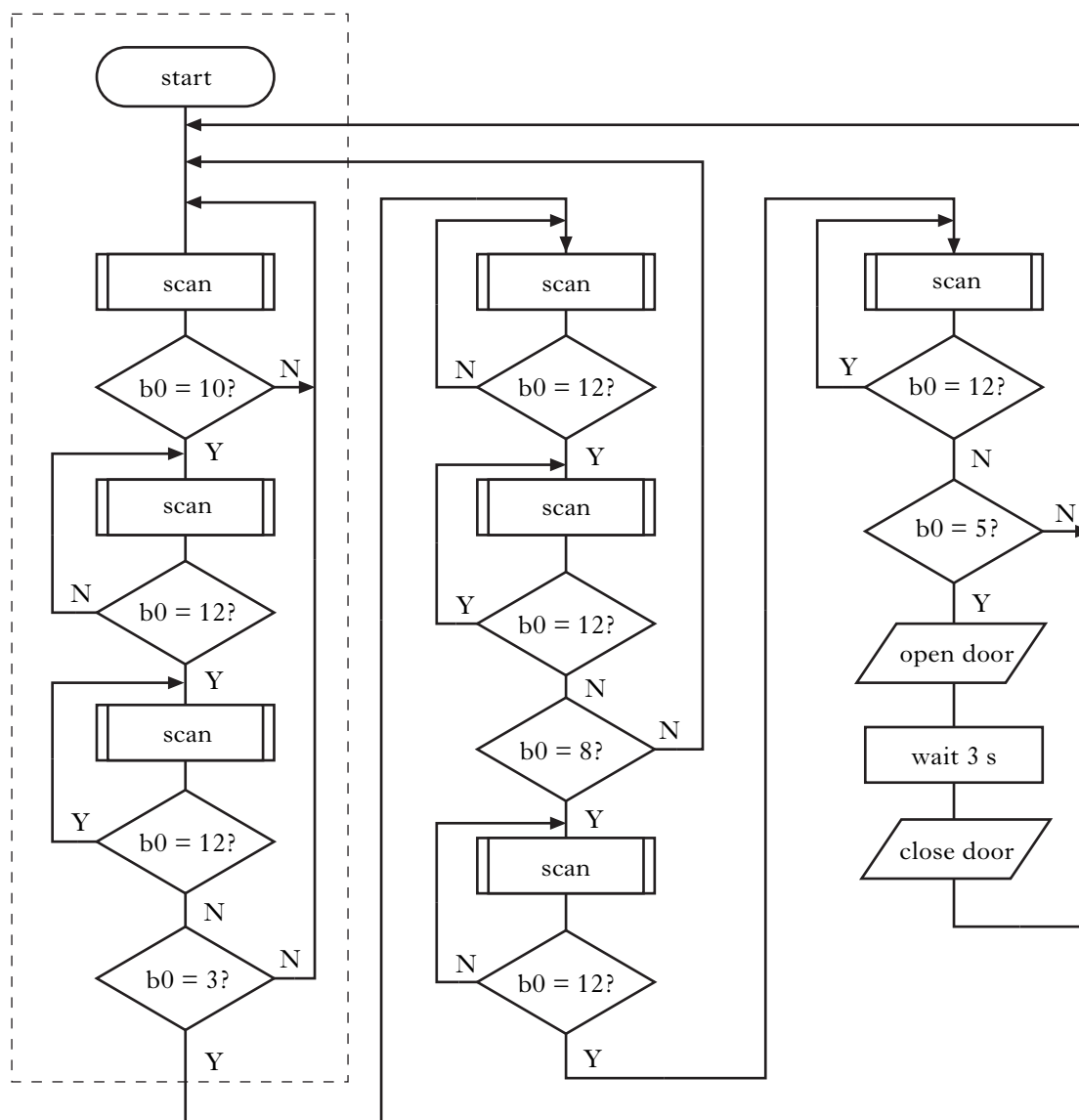


Figure Q11(d)

- (e) Write, in PBASIC, the section of control program represented by the portion of flowchart **within the dashed box**. Assume that the I/O port has been initialised.

6

The value of the key pressed during the sub-procedure *scan* is stored in the variable *b0*.

When the # key is pressed, $b0 = 10$.

If no key is pressed, $b0 = 12$.

- (f) State the user inputs required at keys 0–9 and the # key, in order to open the door.

2

11. (continued)

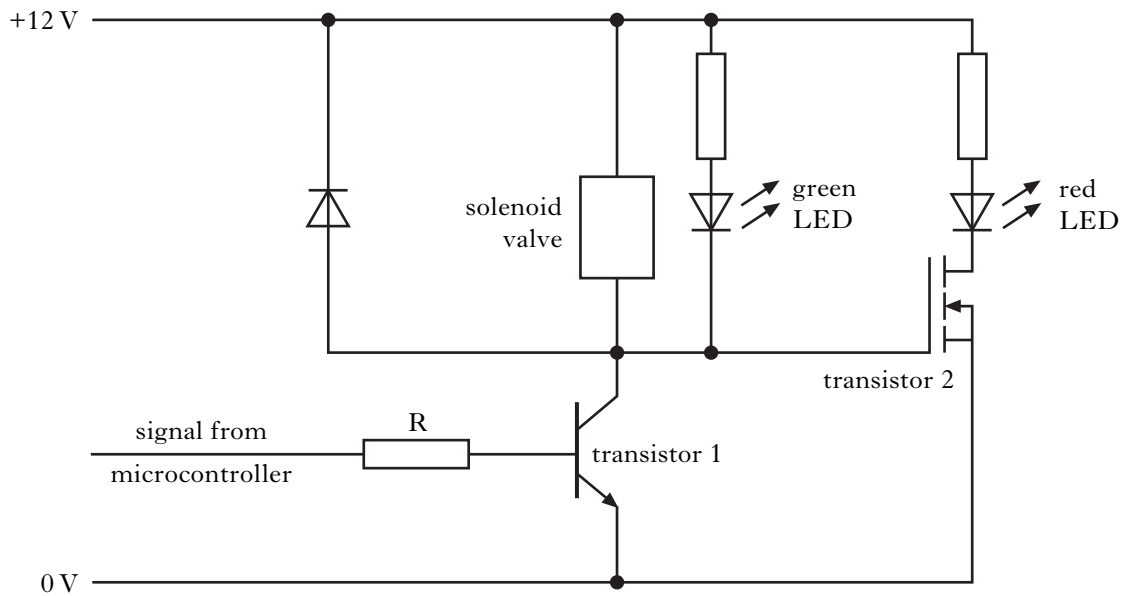


Figure Q11(e)

The output-driver circuit for the security system is shown in Figure Q11(e). When the solenoid valve is activated, a hydraulic cylinder outstrokes, opening the door. A high signal from the microcontroller is at 5 V, and causes 0.8 mA of current to flow from the microcontroller to the output-driver circuit.

- (g) Calculate the required value of resistor R. 1
- (h) State whether the microcontroller output signal is high or low when the red LED is on. Justify your answer. 2

The solenoid has a resistance of $50\ \Omega$. Each LED draws 20 mA when it is switched on. When transistor 1 is switched on and saturated, $V_{CE} = 0.2\text{ V}$.

- (i) Calculate the minimum current gain of transistor 1. 2

(20)

[END OF QUESTION PAPER]

[BLANK PAGE]

[BLANK PAGE]

[BLANK PAGE]