



2009 Technological Studies

Advanced Higher

Finalised Marking Instructions

© Scottish Qualifications Authority 2009

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from the Question Paper Operations Team, Dalkeith.


Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's Question Paper Operations Team at Dalkeith may be able to direct you to the secondary sources.

These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

Section A


Q1

(a)

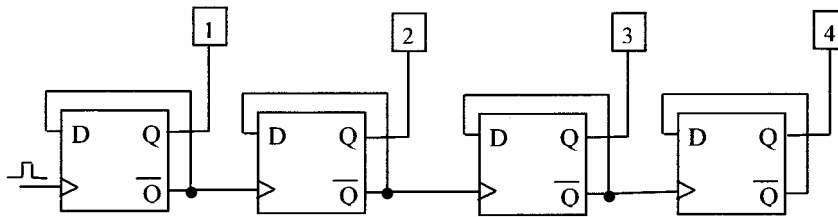

1 for 4 D-types set to toggle ($\frac{1}{2}$ for 1-3)
 1 for 3 Q bar to clock connections ($\frac{1}{2}$ for 2)
 $\frac{1}{2}$ for clock on first D-type
 $\frac{1}{2}$ for Q outputs

(b)

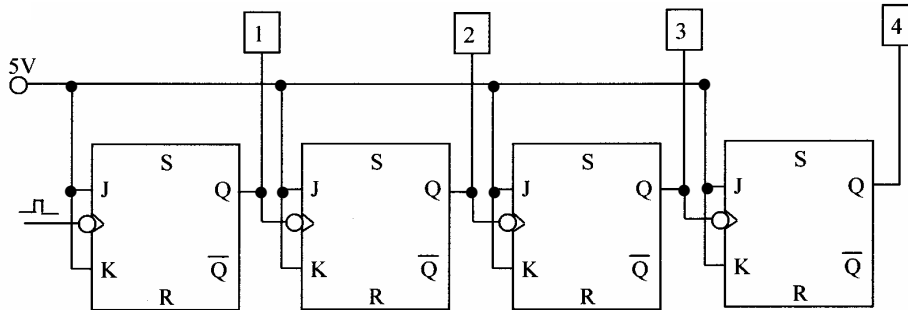

1 for 4 JKs set to toggle ($\frac{1}{2}$ for 1-3)
 1 for 3 Q to clock connections ($\frac{1}{2}$ for 2)
 $\frac{1}{2}$ for clock on first JK
 $\frac{1}{2}$ for Q outputs

Marks	
1 1 $\frac{1}{2}$ $\frac{1}{2}$	3
1 1 $\frac{1}{2}$ $\frac{1}{2}$	3
(6)	
$\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$	2
1 1 1 1	4
(6)	

Q2

(a)

A-D convertor
 LCD Driver
 Data memory/Flash memory
 Suitable number of I/O pins

(b)

Flowchart – Algorithm
 Write code – Text editor
 Assembly code – Assembler
 Download to PIC – Programmer


- (a)
 - (i) The control of the outputs is based on one event happening after another in a sequence.
 - (ii) Time based – each step is controlled by a fixed time pulse.
Event based – each step is controlled by a sensed condition.
- (b) IC1 is a 4-bit binary counter
which counts from 0-15 in binary
IC2 is a binary coded decimal decoder
which converts the binary into a decimal value 0-15
- (c) See Worksheet Q3

[illegible]


(a)	debounce:	movlw	d'200'	}
		movwfw	LOOPCOUNT	
	test:	btfss	PORTB,2	}
		goto	debounce	
		movlw	d'1'	}
		call	pause	
		decfsz	LOOPCOUNT	}
		goto	test	
		return		}
(b)	main:	btfss	PORTB,0	}
		goto	main	
		movlw	d'100'	}
		movwfw	CUPCOUNT	
	dispense:	bcf	PORTB,5	}
		call	debounce	
		bsf	PORTB,4	}
		movlw	d'5'	
		call	wait	}
		bcf	PORTB,4	
		bsf	PORTB,6	}
		movlw	d'15'	
		call	wait	}
		bcf	PORTB,6	
		bsf	PORTB,7	}
		movlw	d'100'	
		call	wait	}
		bcf	PORTB,7	
		decfsz	CUPCOUNT,F	}
		goto	dispense	
		bsf	PORTB,5	}
		goto	main	

Q5

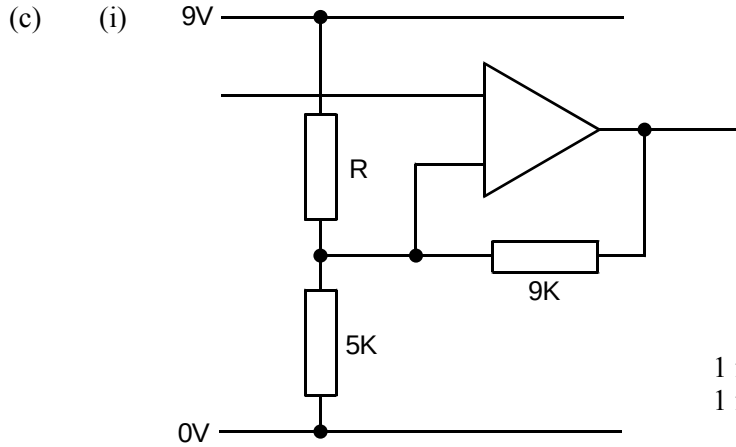- (a) Wein Bridge
- (b) It converts the sine wave to a square waveform.
Waveform will have the same frequency.



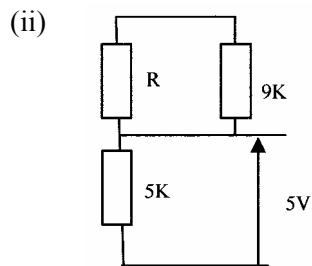1 for correct diagram
1 for correct annotation



$$\frac{R_p}{5} = \frac{4}{5}$$

$$R_p = \frac{4 \times 5}{5}$$

$$R_p = 4k\Omega$$

$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{9}$$

$$\frac{1}{R} = \frac{1}{R_p} - \frac{1}{9}$$

$$\frac{1}{R} = \frac{1}{4} - \frac{1}{9}$$

$$R = 7.2k\Omega$$

- (d) Relaxation Oscillator
Voltage Controlled Oscillator (VCO)



Marks	
1	1
1/2	1
1/2	
1	2
1	
1	
1/2	
1/2	
1	5
1/2	
1/2	1
	(10)

Q6

(a) (i) To prevent members being subjected to bending.

(ii) 3

(b)

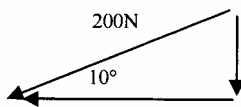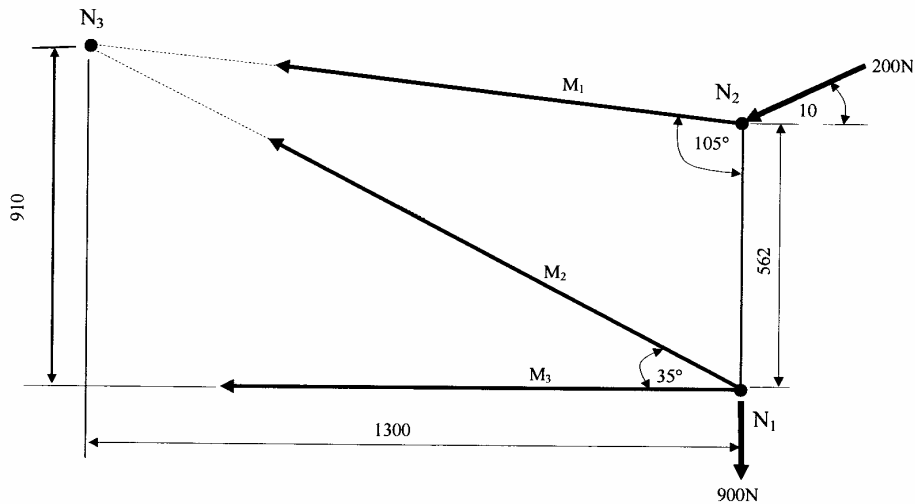

$$V_{200} = 200 \sin 10^\circ = 34.7 \text{ N}$$

$$H_{200} = 200 \cos 10^\circ = 197 \text{ N}$$

$$\text{Calc height } N_3 = 910$$

$$\text{Height diff } N_3 - N_2 = 348$$

Take moments about N_3 $\Sigma M = 0$

$$\Sigma \text{CWM} = \Sigma \text{ACWM}$$

$$(M_3 \times 910) + (900 \times 1300) + (1300 \times 34.7) + (348 \times 197) = 0$$

$$M_3 = -1411 \text{ N}$$

$$M_3 = 1411 \text{ N (strut)}$$

Take moments about N_1 $\Sigma M = 0$


$$\Sigma \text{CWM} = \Sigma \text{ACWM}$$

$$0 = (562 \times H_{M1}) + (197 \times 562)$$

$$H_{M1} = -197 \text{ N}$$

$$M_1 = 197 / \cos 15^\circ$$

$$M_1 = 204 \text{ N (strut)}$$

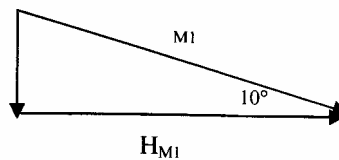

Take moments about N_2 $\Sigma M = 0$

$$\Sigma \text{CWM} = \Sigma \text{ACWM}$$

$$(M_2 \times 460) - (1411 \times 562) = 0$$

$$M_2 = 1722 \text{ N (tie)}$$

Marks	
1	1
1	1
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
2	
1	
1	
1	
1	
1	9
	(11)

Q7

(a) 45 rev/min which is 0.75 rev/sec or 36 steps/sec $1000/36 = 28 \text{ ms/step}$

(b) (i) `main:      btfss      PORTB,1`
 `goto        test2`
 `call        speed1`
 `test2:    btfss      PORTB,2`
 `goto        test3`
 `call        speed2`
 `test3:    btfss      PORTB,3`
 `goto        test3`
 `call        speed3`
 `goto        main`

(ii) `speed2:    movlw      b'11000000' }`
 `movwf      PORTB        }`
 `movlw      d'28'        }`
 `call        pause        }`
 `movlw      b'01010000' }`
 `movwf      PORTB        }`
 `movlw      d'28'        }`
 `call        pause        }`
 `movlw      b'00110000' }`
 `movwf      PORTB        }`
 `movlw      d'28'        }`
 `call        pause        }`
 `movlw      b'10100000' }`
 `movwf      PORTB        }`
 `movlw      d'28'        }`
 `call        pause`
 `return`

Marks	
1	1
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	4
1/2	
1/2	
1/2	
1/2	
1/2	
1/2	3
1/2	
	(8)

Section B

Q8

(a)
$$f = \frac{1.44}{(R_1 + 2R_2)C}$$

$$R_2 = \frac{1}{2} \left[\frac{1.44}{0.33 \times 1 \times 10^{-6}} - 1000 \right]$$

$$R_2 = 2.18 \text{ M}\Omega$$

- (b)
- A – SR latch initiates flashing sequence
 - A – it is reset by the correct number of flashes
 - B – NAND gate allows the clock to control the Light test input
 - C – BCD-7 segment decoder converts the binary value
 - C – this value is displayed as a digit on the 7 segment display
 - D – shift register will cause digit 1 to flash
 - D – followed by digit 2 etc to flash in sequence
 - D – the data input is provided by the SR bistable
 - E – 3-bit binary counter JK up counter
 - E – it will count up to 6 (before resetting)
 - E – then to clock the shift register
 - F – AND gate allows whole system to be reset after all 3 digits have been flashed.

- (c) See Worksheet Q8

(d)

$$BM = \frac{FL}{8}$$

$$BM = \frac{1000 \times 200}{8}$$

$$BM = 25 \times 10^3 \text{ Nmm}$$

Marks	
$\frac{1}{2}$	2
1	
$\frac{1}{2}$	6
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
5	5
$\frac{1}{2}$	1
$\frac{1}{2}$	

(e) (i) $\delta = 100\text{N/mm}^2$

$B = 20$

$$\delta = \frac{My}{I}$$

$$I = \frac{My}{\delta}$$

$$I = \frac{25 \times 10^3 \times \frac{D}{2}}{100}$$

$$I = \frac{BD^3}{12}$$

$$I = \frac{20D^3}{12}$$

$$\frac{20 \times D^3}{12} = \frac{25 \times 10^3 \times D}{100 \times 2}$$

$$D^2 = \frac{12 \times 25 \times 10^3}{100 \times 2 \times 20}$$

$$D = \sqrt{75}$$

$$D = 8.66\text{mm}$$

(ii) For stainless steel $E = 190 - 200\text{kN/mm}^2$ (any value in this range)

$$I = \frac{BD^3}{12}$$

$$I = \frac{20 \times 8.67^3}{12}$$

$$I = 1086$$

$$\delta = \frac{FL^3}{192EI}$$

$$\delta = \frac{1000 \times 200^3}{192 \times 190 \times 10^3 \times 1086}$$

$$\delta = 0.202\text{mm}$$

Marks	
$\frac{1}{2}$	4
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
1	
$\frac{1}{2}$	2
$\frac{1}{2}$	
$\frac{1}{2}$	
	(20)

Q9

(a)	Testbeam:	btfsc goto btfsc goto btfsc goto goto	PORTB,0 buttonA PORTB,1 buttonB PORTB,2 buttonC Testbeam	} }
	ButtonA:	rrf goto	LOADTIME,F Beams	
	ButtonB:	rlf goto	LOADTIME,F Beams	
	ButtonC:	rlf rlf rlf goto	LOADTIME,F LOADTIME,F LOADTIME,F Beams	}
	Beams:	movlw movwf call clrf goto	b'11000000' PORTB delay PORTB Testbeam	

(b) $\Sigma M = 0$
 $(3 \times 0.5) + (4 \times 2.25) + (0.8 \times 3 \times 1.5) = (R_2 \times 3)$
 $R_2 = 4.7 \text{ kN}$
 $\Sigma F_V = 0$
 $R_1 + R_2 = 3 + (0.8 \times 3) + 4$
 $R_1 = 8.2 - 4.7$
 $R_1 = 4.7 \text{ kN}$

(c) See Worksheet Q9

Marks	
$\frac{1}{2}$	8
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
1	
1	
1	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	2
	2

- (d) (i) Assume L is the distance to the maximum bending moment from the left hand end. At the turning point the differential of the expression will be equal to 0.

$$M = 4.7L - \left(0.8 \times \frac{L^2}{2}\right) - 3(L - 0.5)$$

$$M = 4.7L - 0.4L^2 - 3L + 1.5$$

$$M = 1.7L - 0.4L^2 + 1.5$$

$$\frac{dM}{dL} = 1.7 - 0.8L = 0$$

$$L = \frac{1.7}{0.8} = 2.125m$$

$$\text{Max BM} = (4.7 \times 2.125) - (3 \times 1.625) - (0.8 \times 2.125 \times 1.0625) = 3.31kNm$$

Alternatively using the SF diagram the SF at 0.5 from the LHE is 1.3 and the force is 0.8/m.
So $1.3 \times 0.8 = 1.04$ from 0.5 is where SF = 0 (max BM) so max BM is $0.5 + 1.04 = 1.54m$

(ii)	BM from left	Bending moment calculation
	0m & 3m	0kNm
	0.5m	$(4.7 \times 0.5) - (0.8 \times 0.5 \times 0.25) = 2.25kNm$
	1m	$(4.7 \times 1) - (3 \times 0.5) - (0.8 \times 1 \times 0.5) = 2.8kNm$
	1.5m	$(4.7 \times 1.5) - (3 \times 1) - (0.8 \times 1.5 \times 0.75) = 3.15kNm$
	2m	$(4.7 \times 2) - (3 \times 1.5) - (0.8 \times 2 \times 1) = 3.3kNm$
	2.25m	$(4.7 \times 2.25) - (3 \times 1.75) - (0.8 \times 2.5 \times 1.25) - (0.25 \times 4) = 3.3kNm$


See Worksheet Q9

Curve correct polarity
Correctly plotted points

Marks	
1	
1	2
1/2	
1/2	
1	
1	
1	
1/2	
1/2	6
	(20)

Q10

(a) (i)

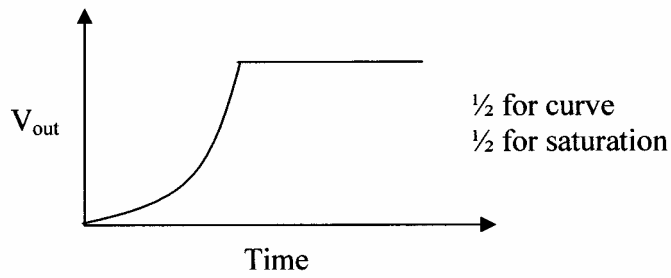

(ii) $V_{in} = 5V$

$$V_2 = -\frac{1}{RC} \int V_{in} dt$$

$$= \frac{1}{3 \times 10^3 \times 47 \times 10^{-6}} \times 5t$$

$$V_2 = 35.5t$$

$$V_{out} = \frac{1}{11 \times 10^3 \times C} \times \int 35.5t dt$$

$$V_{out} = \frac{1.61 \times 10^{-3} t^2}{C}$$

(b) (i) $t = 0.1s$

$$V_2 = -35.5t$$

$$V_2 = -35.5 \times 0.1$$

$$V_2 = -3.55V$$

(ii) $V_{out} = \frac{1.61 \times 10^{-3} t^2}{C}$

$$2 = \frac{1.61 \times 10^{-3} 0.1^2}{C}$$

$$C = \frac{1.61 \times 10^{-3} 0.1^2}{2}$$


$$C = 8.05 \times 10^{-6}$$

$$C = 8\mu F$$


Marks	
$\frac{1}{2}$ $\frac{1}{2}$	1
$\frac{1}{2}$	
1	
1	
$\frac{1}{2}$	3
$\frac{1}{2}$	
$\frac{1}{2}$	1
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	
$\frac{1}{2}$	2

				Marks	
(c)	main:	btfss	PORTB,2	1/2	7
		goto	main	1/2	
		bsf	PORTB,7	1/2	
		call	getx		
		call	gety	1/2	
		btfss	PORTB,2	1/2	
		bcf	PORTB,7	1/2	
		goto	main	1/2	
	gety:	movfw	TR	1/2	
		addwf	TL	1/2	
		movfw	TL	1/2	
		movwf	TOPSUM	1/2	
		movfw	BR		
		addwf	BL		
		movwf	BOTTOMSUM	}	
		movfw	BOTTOMSUM		
		subwf	TOPSUM	1/2	
		movwf	YPOS	1/2	
		return		1/2	
		(d)	testbar:	movlw	
subwf	YPOS			1/2	
btfss	STATUS,C			1/2	
goto	testbar			1/2	
movlw	d'39'			}	
subwf	YPOS				
btfsc	STATUS,C				
goto	testbar				
movlw	d'150'			1/2	
movwf	COUNTER			1/2	
flash:	bsf		PORTB,4	1/2	
	movlw		d'6'		
	call		wait	1/2	
	bcf		PORTB,4		
	movlw		d'14'		
	call		wait	1/2	
	decfsz		COUNTER,F	1/2	
	goto		flash		
	return			1/2	
					6
				(20)	


Worksheet Q3

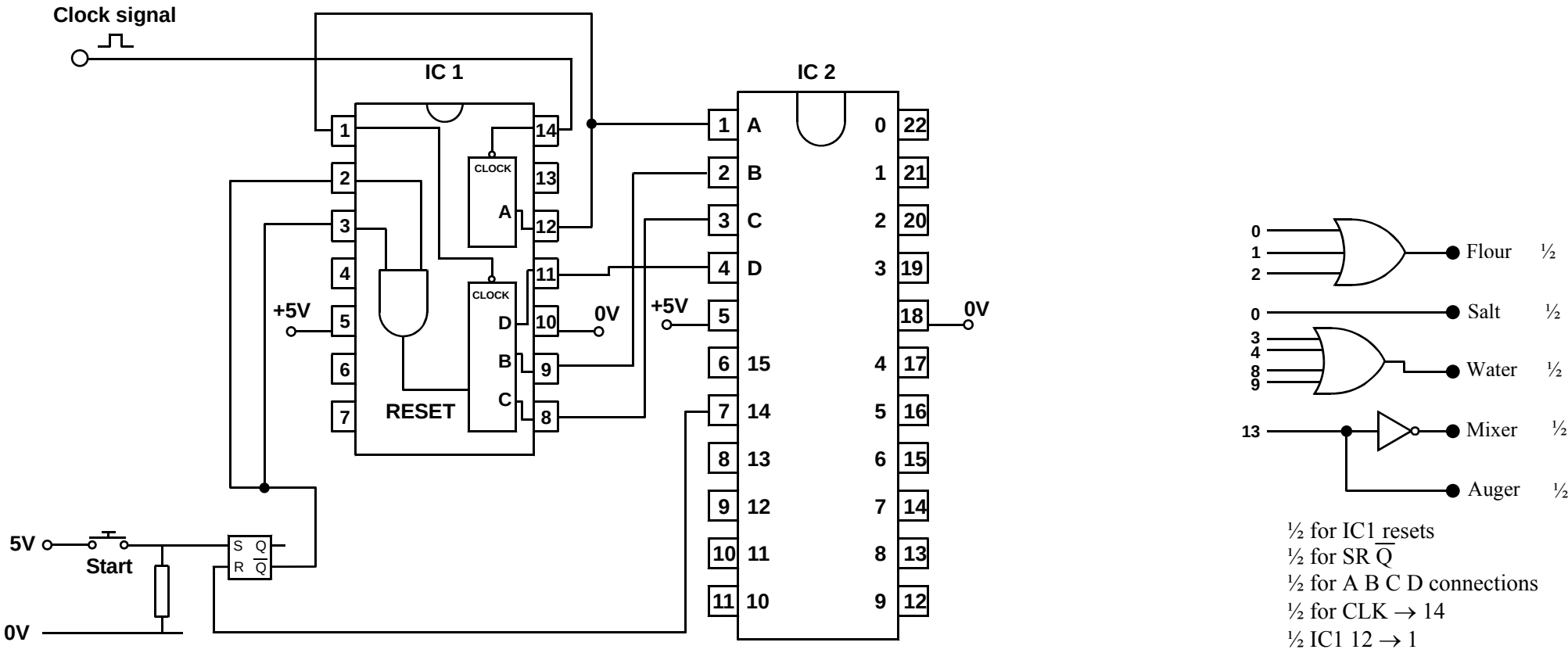

Information Sheet Q8

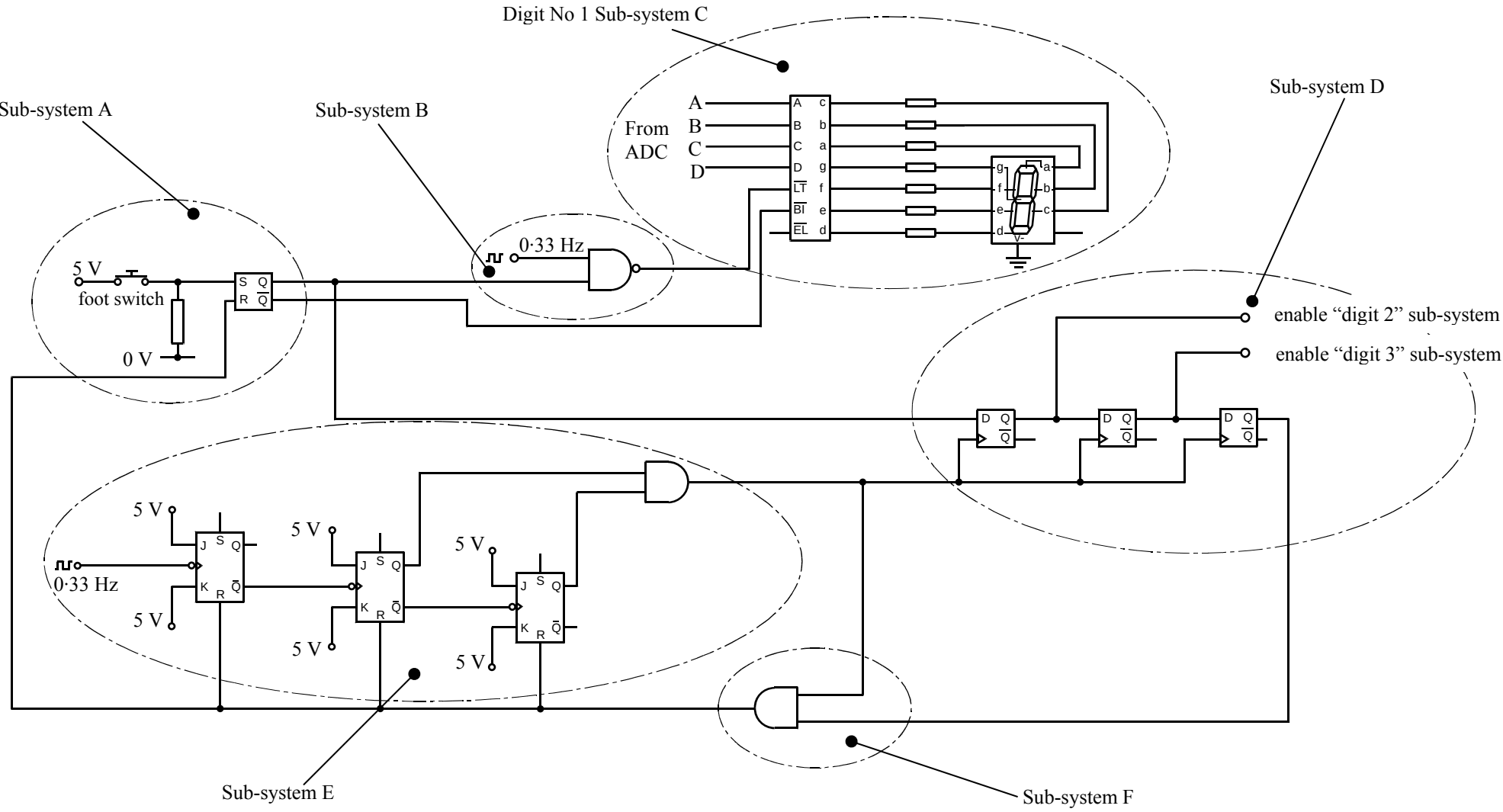


Worksheet Q8

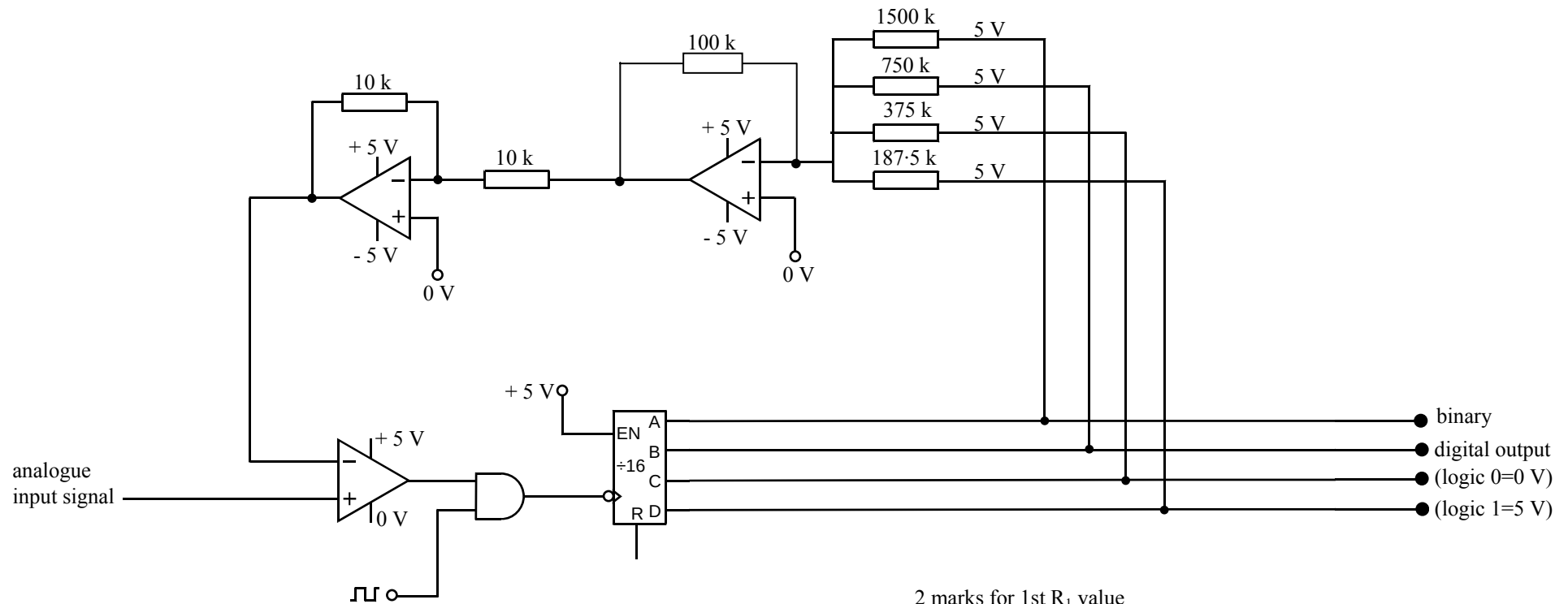

2 marks for 1st R_1 value
 $\frac{1}{2}$ for $\div 2$ other 3
 $\frac{1}{2}$ for summing amp diagram
 $\frac{1}{2}$ power supplies
 $\frac{1}{2}$ for output connections

Worksheet Q9

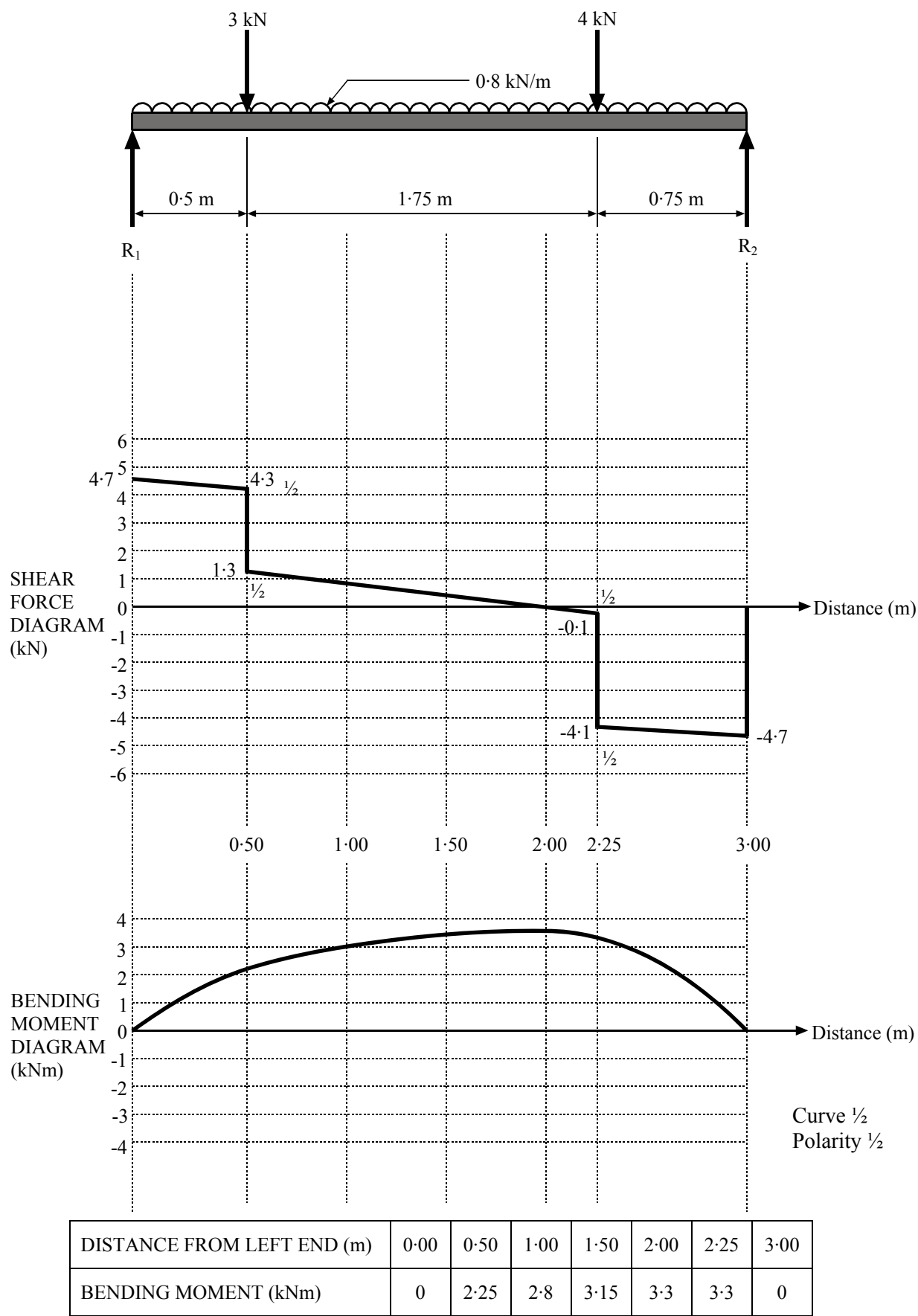

[END OF MARKING INSTRUCTIONS]