



2009 Technological Studies

Higher

Finalised Marking Instructions




© Scottish Qualifications Authority 2009


The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from the Question Paper Operations Team, Dalkeith.


Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's Question Paper Operations Team at Dalkeith may be able to direct you to the secondary sources.

These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

Section A

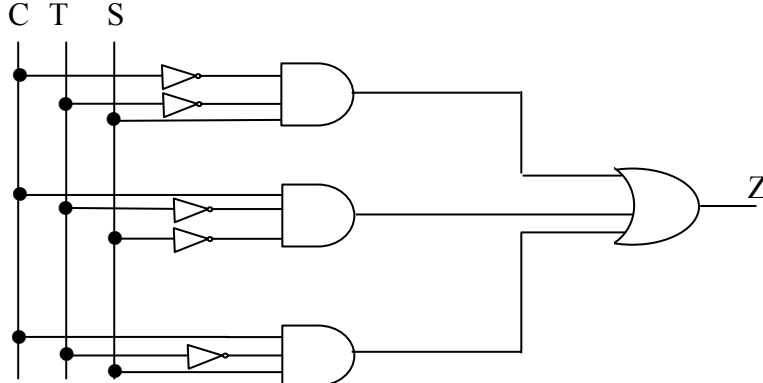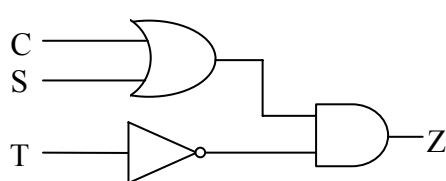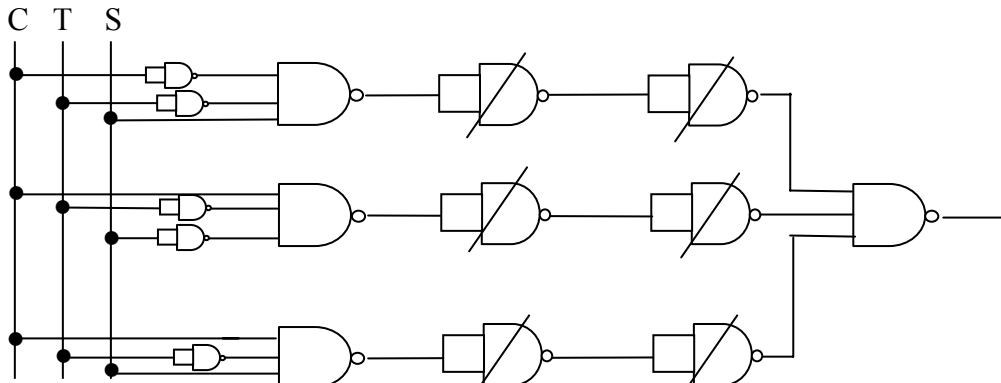
Question		Mark Allocation		Marks	
1.	(a)	$Z = (\overline{C}.\overline{T}.S) + (C.\overline{T}.\overline{S}) + (C.T.S)$	$\frac{1}{2}$ mark for each item in brackets $\frac{1}{2}$ for linking with OR function	$1\frac{1}{2}$ $\frac{1}{2}$	2
		OR			
	(b)	$Z = \overline{T} . (C + S)$	$(C + S)$ function $\overline{T}$. function	1 1	2
					
		Also can be implemented with just three NOT gates	NOT gates Correct input connection to NOT gates $\frac{1}{2}$ for each AND gate and its input connections	$\frac{1}{2}$ $\frac{1}{2}$ $1\frac{1}{2}$	3
		OR			
			OR gate and correct inputs NOT gate and correct inputs AND gate and correct inputs	1 1 1	3
	(c)		NOT equivalents and correct input connections AND equivalents and correct input connections OR equivalent and correct input connections Cancellation of redundant gates	$\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$	

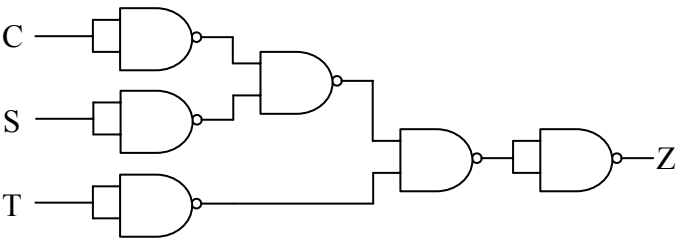Question		Mark Allocation	Marks	
	(d)	OR  OR equivalent and correct input connections 1 NOT equivalent and correct input connections ½ AND equivalent and correct input connections ½ 2		
		(i) CMOS no ½ marks 1 (ii) Voltage range suitable for 9V supply. ½ Low current usage/low power consumption ½ 2 Fan out Noise immunity NOT cost		
				(9)

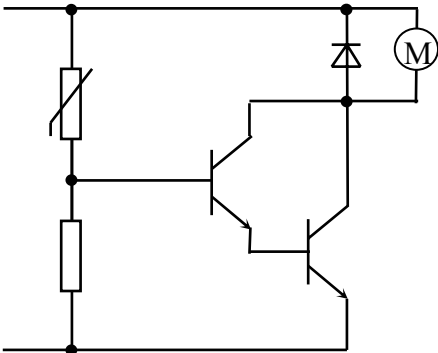Question		Mark Allocation	Marks	
2.	(a)	A diode The diode prevents back emfs from damaging the transistor. (Full answer required)	$\frac{1}{2}$ $\frac{1}{2}$	1
	(b)	<u>Input sub-system:</u> - The input sub-system consists of a thermistor and resistor in a voltage divider. - As the temperature rises, the resistance of the thermistor falls. - As the temperature rises, the voltage across the thermistor falls. any two answers: ($\frac{1}{2}$) As the temperature rises the signal voltage rises (or the voltage at the base of the transistor rises). ($\frac{1}{2}$)	1 $\frac{1}{2}$	3
		<u>Process sub-system:</u> - When the voltage on the base of the transistor reaches 0.7 V a base current flows. - The transistor amplifies the base current into a larger collector current. - When the voltage on the base of the transistor reaches 0.7 V the transistor is switched on. - When the transistor is switched on collector current flows. any two answers @ $\frac{1}{2}$ mark each:	1	
		<u>Output sub-system:</u> - When current flows through the motor (or transistor switches on) the motor turns. $\frac{1}{2}$ mark:	$\frac{1}{2}$	
	(c)	(i)  correct Darlington correct connections of circuit ($\frac{1}{2}$) pair arrangement ($\frac{1}{2}$) shown or indicated to rest	1 1	3
		(ii) Darlington pair/Darlington driver. (iii) $h_{FE(overall)} = h_{FE(1)} \times h_{FE(2)}$ $h_{FE(2)} = h_{FE(overall)} \div h_{FE(1)}$ $h_{FE(2)} = 1500 \div 50 = 30$ formula, stated or implicit ($\frac{1}{2}$) answer with no units ($\frac{1}{2}$)	1	
	(d)	A MOSFET transistor is <i>voltage operated</i> , whereas a bipolar transistor is <i>current operated</i> .		1 (8)

Question		Mark Allocation	Marks	
3.	(a)	(i) $12 \times 4 \times 7.5 = 360^0$ (ii) $12 \times 4 \times 20 = 960 \text{ ms (0.96 s)}$	no half marks (unit not required) no half marks (units required)	1 1 2
	(b)	main: let dirs = %11110000 (optional) for b0 = 1 to 24 let pins = %01100000 pause 5 let pins = %01010000 pause 5 let pins = %10010000 pause 5 let pins = %10100000 pause 5 next b0 end	correct time delays correct number of loops steps in correct order	$\frac{1}{2}$ $\frac{1}{2}$ 1 2
	(c)	Only two output pins of the microcontroller are required. The programming is simpler/easier to change.		1 1 2
				(6)



Question		Mark Allocation	Marks	
4.	(a)	Ductile.		1
	(b)	$\sigma = F/A$ $= 30/80$ correct substitution of values using a load value within elastic region $= 0.375 \text{ kN/mm}^2$ correct calculation (units not necessary)	$\frac{1}{2}$ $\frac{1}{2}$	3
		$\varepsilon = \Delta l/l$ $= 0.1/50$ correct substitution of values using the corresponding extension value $= 0.002$ correct calculation	$\frac{1}{2}$ $\frac{1}{2}$	
		$E = \sigma/\varepsilon$ $= 0.375/0.002$ correct substitution into correct formula $= 188 \text{ kN/mm}^2$ correct answer including correct units	$\frac{1}{2}$ $\frac{1}{2}$	
		(c) $\sigma_{\text{ultimate}} = F/A$ $= 80/80$ correct substitution into correct formula $= 1 \text{ kN/mm}^2$ correct answer including correct units	$\frac{1}{2}$ $\frac{1}{2}$	1
	(d)	(i) Factor of Safety = $\sigma_{\text{ultimate}} / \sigma_{\text{safe working}}$ $\sigma_{\text{safe working}} = \sigma_{\text{ultimate}} / \text{Factor of Safety}$ $= 1000 \text{ N/mm}^2 / 6$ correct substitution into correct formula $= 167 \text{ N/mm}^2$ correct answer including correct units	$\frac{1}{2}$ $\frac{1}{2}$	1
		(ii) $\sigma = F/A$ $F = \sigma \times A$ correct substitution into correct formula $= 167 \times 30 \times 10$ correct answer including correct units $= 50.1 \text{ kN}$	$\frac{1}{2}$ $\frac{1}{2}$	1 (7)

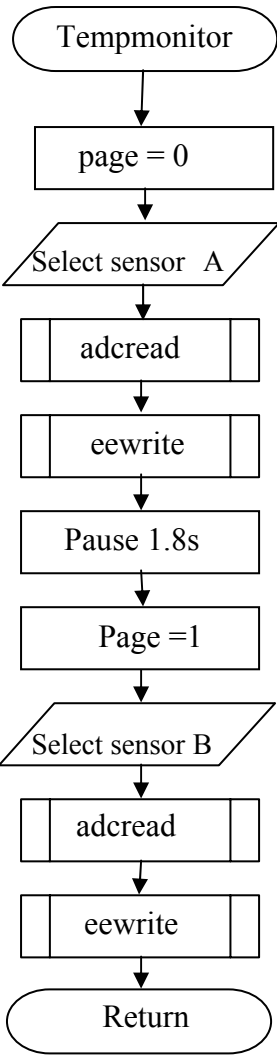Question		Mark Allocation	Marks	
5	(a)	A multiplexer allows either of the analogue signals to be selected; or A multiplexer enables more than one analogue sensor to be connected to one A to D converter.		1
	(b)	<pre>graph TD; Start([Tempmonitor]) --> Init[page = 0]; Init --> SelectA[/Select sensor A/]; SelectA --> ReadA[adcread]; ReadA --> WriteA[eewrite]; WriteA --> Pause[Pause 1.8s]; Pause --> Page1[Page =1]; Page1 --> SelectB[/Select sensor B/]; SelectB --> ReadB[adcread]; ReadB --> WriteB[eewrite]; WriteB --> End([Return]);</pre> tempmonitor & return boxes ½ all other box content ½ mark each 4 ½ correct box types (subtract ½ for first instance of incorrect box type up to 1 mark maximum) 1		6 (7)




Question		Mark Allocation		Marks	
6.	(a)	LDR resistance = 200Ω $R_V = 200/1000 \times 8$ $= 1.6 \text{ k}\Omega$	from data book substitution answer $\frac{1}{2}$; units $\frac{1}{2}$	$\frac{1}{2}$ $\frac{1}{2}$ 1	2
	(b)	Maximum output voltage before saturation = 85% of 9V = 7.65V $I = V/R$ $= (7.65 - 0.7)/760$ $= 9.14 \text{ mA}$	calculation formula stated or implied substitution answer including units	$\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$	
	(c)	(i) $I = 9/15$ $= 600 \text{ mA}$	calculation answer	$\frac{1}{2}$ $\frac{1}{2}$	
		(ii) $h_{FE} = 600/9.14$ $= 65.6$	calculation answer	$\frac{1}{2}$ $\frac{1}{2}$	
		(iii) 2N3704			1 (7)
7.	(a)	$\Sigma M_H = 0$ $(F \cos 30 \times 800) + (142 \cos 70 \times 1100) = (300 \times 400)$ $F \cos 30 = 83.22$ $F = 96.1 \text{ N}$	formula stated or implicit three terms @ $\frac{1}{2}$ each calculation answer, including units	$\frac{1}{2}$ $1\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$	3
	(b)	$\Sigma F_V = 0$ $R_V + 142 \cos 70 + 96.1 \cos 30 = 300$ $R_V = 168.2 \text{ N}$	formula stated or implicit three components @ $\frac{1}{2}$ each answer (units not necessary)	$\frac{1}{2}$ $1\frac{1}{2}$ $\frac{1}{2}$	
		$\Sigma F_H = 0$ $R_H + 96.1 \cos 60 = 142 \cos 20$ $R_H = 85.4 \text{ N}$	formula stated or implicit ($\frac{1}{2}$ if no mark awarded above) two components @ $\frac{1}{2}$ each answer (units not necessary)	$\frac{1}{2}$ 1 $\frac{1}{2}$	
		$R = \sqrt{(168^2 + 85.4^2)}$ $= 188 \text{ N}$	formula and calculation answer including units	$\frac{1}{2}$ $\frac{1}{2}$	
		$\tan \theta = 168/85.4$ $\theta = 63.1^\circ$ (from horizontal)	substitution answer	$\frac{1}{2}$ $\frac{1}{2}$	6 (9)


Question		Mark Allocation	Marks	
8.	(a)	Digital to analogue converter (summing amplifier and inverting amplifier - ½ mark)		1
	(b)	$V_{out} = -R_f (V_1/R_1 + V_2/R_2 + V_3/R_3 + V_4/R_4) \times -R_f/R_i$ (½ for whole formula, stated or implicit)	½	
		$V_{out} = -100 (0/800 + 5/400 + 0/200 + 5/100) \times -100/100$ correct substitution (½ for 1 mistake, 0 for more than 1 mistake)	1	
		$V_{out} = 6.25 \text{ V}$ answer, including units	½	2
	(c)	Pulse width modulation (pwm - ½ mark)		1
	(d)	3:1		1
	(e)	(i) The motor would gradually (or gently) accelerate to full speed. (accelerate - ½ mark; gradually or gently - ½)	1	
		(ii) The purpose is to avoid damage to the motor (or mechanisms connected to the motor). To reduce wear in components.	1	2
				(7)

Section B

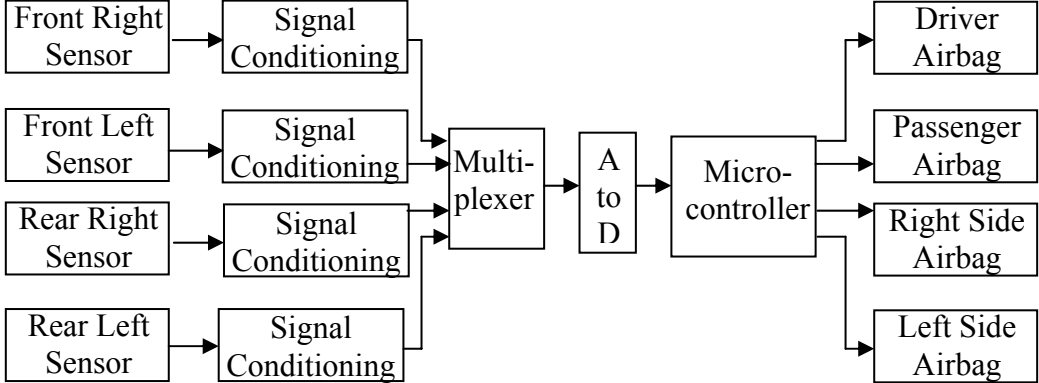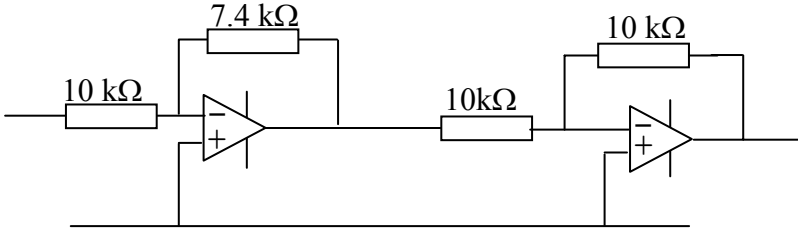Question	Mark Allocation	Marks
9.	(a)  All four sensors $\frac{1}{2}$ Four signal conditioning sub-systems $\frac{1}{2}$ Multiplexer $\frac{1}{2}$ A to D $\frac{1}{2}$ Microcontroller $\frac{1}{2}$ All four airbag outputs $\frac{1}{2}$ 3 (b) $A_v = 5/6.8 = 0.74$ Two inverting amplifiers. First amplifier, $R_f = 7.4 \text{ k}\Omega$, $R_i = 10 \text{ k}\Omega$ (or any other pair in $\text{k}\Omega$ range) $\frac{1}{2}$ Correct connections and resistors correct way round $\frac{1}{2}$ Second amplifier, $R_f = 10 \text{ k}\Omega$, $R_i = 10 \text{ k}\Omega$ (or any other pair in $\text{k}\Omega$ range) $\frac{1}{2}$ Correct connections and resistors correct way round $\frac{1}{2}$ Not in $\text{k}\Omega$ range – deduct $\frac{1}{2}$ mark once only Voltage gain calculation $\frac{1}{2}$ 3 	

Question		Mark Allocation			Marks	
	(c)	10110111 = 183	calculation	½	2	
		V _{in} to ADC = 5 x 183/255 = 3.59V	calculation	½		
		V from sensor = 3.59/0.74	calculation	½		
		= 4.88 V	answer (including units)	½		
		<u>Alternative answer</u>				
	V from sensor = 6.8 x 183/255	calculation	1	2		
	= 4.88 V	answer ½, units ½	1			
	(d)	frontbags:	low 0		(½)	9
			gosub adcread		(½)	
			if data > 147 then testpassenger		(1)	
testdriver:		high 0	(½)			
		gosub adcread	(½)			
		if data > 103 then deploydrivers	(1)			
		return	(½)			
testpassenger:		if data > 182 then deployboth	(1)			
		high 6	(½)			
		goto testdriver	(½)			
deployboth:		high6 } high7 }	(½)			
		return	(½ both returns)			
deploydrivers:		if data > 182 then deployboth	(1)			
		high7	(½)			
		return	no marks for labels			
(e)	V _{out} = - R _f (V ₁ /R ₁ + V ₂ /R ₂ + V ₃ /R ₃ + V ₄ /R ₄)	formula, stated or implicit	½	2		
	- 4.5 = -R _f (1.2/10 + 1.2/10 + 0.6/5 + 0.6/5)	correct substitution	½			
	- 4.5 = -R _f (4.8x10 ⁻⁴)	calculation	½			
	R _f = 9.38 kΩ	answer including units	½			
(f)	I _c = 3.6/6 = 0.6 A			1		
	h _{FE} = 600/15.5	calculation	½		20	
	= 38.7	answer	½			

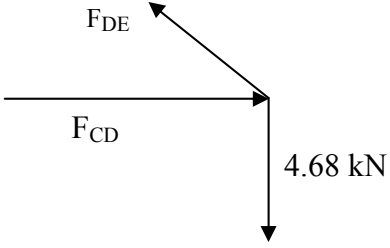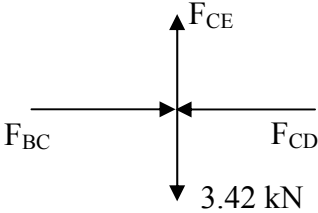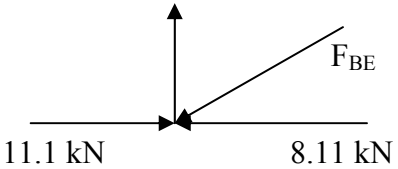Question		Mark Allocation	Marks	
10.	(a)	<u>Analysing Node D</u>		
			$\Sigma F_{up} = \Sigma F_{down}$ $F_{DE} \cos 60 = 4.68$ equation 1/2 $F_{DE} = 4.68 / \cos 60$ $F_{DE} = 9.36 \text{ kN (tension)}$ magnitude & units & nature 1	
		$\Sigma F_{right} = \Sigma F_{left}$ $F_{CD} = 9.36 \cos 30$ equation 1/2 $F_{CD} = 8.11 \text{ kN (compression)}$ magnitude & units & nature 1		
		<u>Analysing Node C</u>		
			$\Sigma F_{left} = \Sigma F_{right}$ $F_{BC} = F_{CD}$ $F_{BC} = 8.11 \text{ kN (compression)}$ magnitude & units & nature 1	
		<u>Analysing Node B</u>		
			$\Sigma F_{left} = \Sigma F_{right}$ $F_{BE} \cos 30 + 8.11 = 11.1$ equation 1 $F_{BE} = 2.99 / \cos 30$ $F_{BE} = 3.45 \text{ kN (compression)}$ magnitude & units & nature 1	6
	(b)	UTS = 430 N/mm ² from data book 1/2		
		Force in each bolt = (3.42/4) + 80 = 935 N calculation 1/2		
		answer (units not necessary) 1/2		
		σ in each bolt = 430/8 = 53.8 N/mm ² calculation 1/2		
		answer (units not necessary) 1/2		
		$A = F / \sigma$ $= 935 / 53.75$ $= 17.4 \text{ mm}^2$ $d = \sqrt{(A \times 4) / \pi}$ $= \sqrt{(17.4 \times 4) / 3.14}$ $= 4.71 \text{ mm}$	calculation 1/2 answer (units not necessary) 1/2 formula, stated or implicit 1/2 calculation 1/2 answer, including units 1/2	5

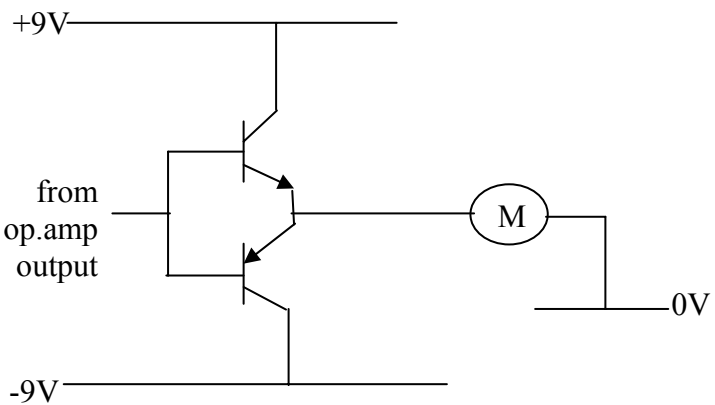Question	Mark Allocation	Marks
(c)		
	NPN/PNP transistors (½ mark each) 1 transistor connections ½ motor ½	2
	(d) (i) $V_2 - V_1 = V_{out}/(R_f/R_i)$ formula, stated or implicit ½ $V_2 - V_1 = 9.68/(260/9)$ $V_2 - V_1 = 0.34$ answer (units not necessary) ½ $V_1 = V_2 - 0.34$ calculation ½ $V_1 = 4.08 - 0.34$ answer including units ½ $V_1 = 3.74 \text{ V}$	2
	(ii) $V_{out}(\text{max}) = 0.85 \times 16 = 13.6 \text{ V}$ calculation and answer ½ $V_2 - V_1 = 13.6/(260/9) = 0.47 \text{ V}$ calculation and answer ½	1
	(e) If lower resistance in potentiometer B is increased/alterd, V_2 will increase/change Non-inverting input voltage becomes greater than inverting input voltage Difference amplifier amplifies voltage difference, output goes positive & motor turns As motor turns lower resistance of potentiometer A increases and V_1 increases Voltage difference decreases and motor slows and then stops. If lower resistance of potentiometer B is decreased then motor will turn other way V_1 will decrease and the motor will slow down and stop any four answers (½ mark each)	2
	(f) Increase gain of difference amplifier	1
	(g) Motor will overshoot desired position. Motor will not settle at desired position (it will hunt). Motor will run either full speed forward or full speed reverse ON/OFF NOT acceptable any answer	1 (20)

Question		Mark Allocation		Marks																	
11	(a)	(i)	<table><tr><td>X</td><td>Y</td><td>Z</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> (no half marks)	X	Y	Z	0	0	0	0	1	0	1	0	1	1	1	0			1
		X	Y	Z																	
	0	0	0																		
	0	1	0																		
	1	0	1																		
	1	1	0																		
	(ii) $Z = X \cdot \bar{Y}$	(no half marks)			1																
	(b)	Keys 4, 6 and 7 must be pressed	(no half marks)			1															
	(c)	The correct keys must be held down to open the door.	(no half marks)	1																	
		If any of the correct keys are released, the door will shut.	(no half marks)	1		2															
	(d)	(i) 4, 5, 6 and 7	(no half marks)			1															
		(ii) Input pin 2				1															
	(e)	main: gosub scan	½ for all three 'gosub scan' commands																		
if b0 = 10 then scan2		1																			
goto main		½																			
scan2: gosub scan		(awarded above)																			
if b0 = 12 then scan3		1																			
goto scan2	½																				
scan3: gosub scan	(awarded above)																				
if b0 = 12 then scan 3	1																				
if b0 = 3 then scan 4	1																				
goto main	½				6																
(f)	The # key must be pressed, then released; the '3' key must be pressed, then released; the '8' key must be pressed, then released; the '5' key must be pressed, then released.																				
		# key	½																		
		correct number keys in correct order	1																		
		pressing then releasing of each key	½		2																
(g)	$R = V/I = (5 - 0.7) V/0.8 \times 10^{-3}$	(correct substitution in correct formula)	½																		
	= 5.38 kΩ	(correct answer including units)	½		1																
(h)	The microcontroller signal is low		½																		
	The NPN transistor is switched off		½																		
	the voltage at the collector of the transistor is +12 V		½																		
	this voltage is applied to the gate of the MOSFET, turning red LED on		½		2																
(i)	Current through solenoid = $V/R = (12 - 0.2)/50 = 0.236 \text{ A}$	(units not necessary)	1																		
	Total collector current = $0.236 + 0.020 = 0.256$ (only 1 LED is on)	(units not necessary)	½																		
	$h_{FE} = I_c/I_b = 256/0.8 = 320$	(NO units)	½		2																
					(20)																

[END OF MARKING INSTRUCTIONS]