



2012 Technological Studies

Higher

Finalised Marking Instructions

© Scottish Qualifications Authority 2012

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from SQA's NQ Delivery: Exam Operations.


Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's NQ Delivery: Exam Operations may be able to direct you to the secondary sources.



These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

Section A

Question		Mark Allocation				Marks																																						
1.	(a)	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>Z</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>				A	B	C	Z	0	0	0	0	0	0	1	0	0	1	0	1	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	0	3 marks for all z output 2 marks 7 or 6 z correct 1 mark 5 or 4 z correct 0 marks 3 or less correct	1	3
		A	B	C	Z																																							
		0	0	0	0																																							
0	0	1	0																																									
0	1	0	1																																									
0	1	1	0																																									
1	0	0	1																																									
1	0	1	0																																									
1	1	0	1																																									
1	1	1	0																																									
(b)	$Z = \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.\bar{C}$				1 mark for each correct combination 1 mark for logic operators	3	4																																					
Alternatively $Z = (A + B).\bar{C}$ (if operators swapped, deduct 1 mark) (C not \bar{C} , deduct 1 mark) (missing brackets, deduct 1 mark)				1																																								
(c)					AND gate equivalents and connections NOT gate equivalents and connections OR gate equivalent and connections Cancellation of redundant gates	3 3 2 1		9																																				
See Supplementary Sheet for part (c) from simplified Boolean (page 3)							(16)																																					

Supplementary Sheet

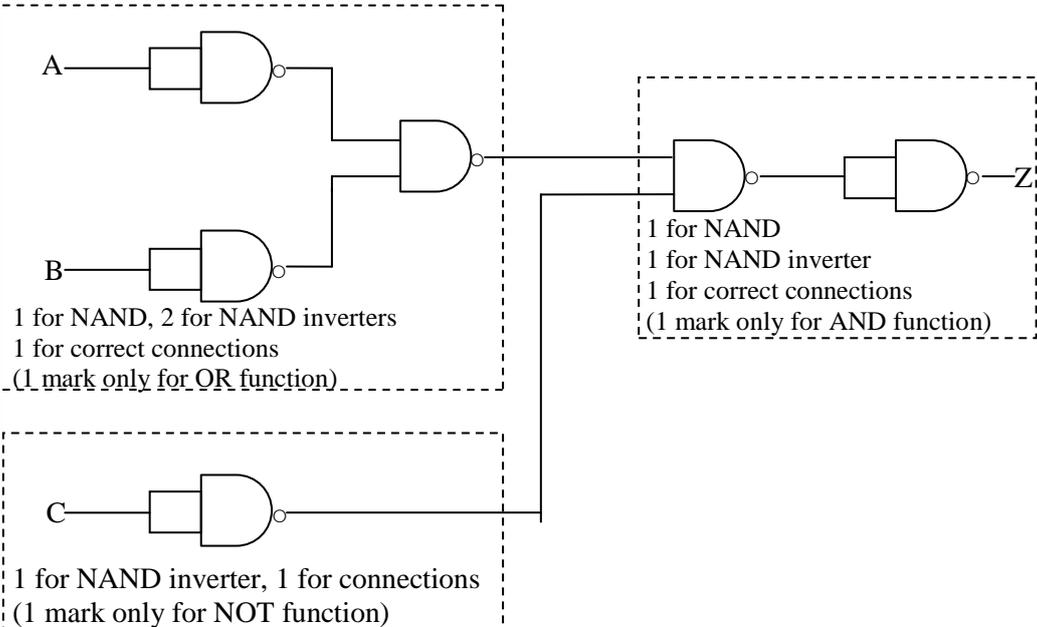
Question	Mark Allocation	Marks
<p>1.</p>	<p>(b) $Z = (A+B) \cdot \overline{C}$ (simplified form)</p> <p>(c)</p>  <p>1 for NAND, 2 for NAND inverters 1 for correct connections (1 mark only for OR function)</p> <p>1 for NAND inverter, 1 for connections (1 mark only for NOT function)</p> <p>1 for NAND 1 for NAND inverter 1 for correct connections (1 mark only for AND function)</p>	

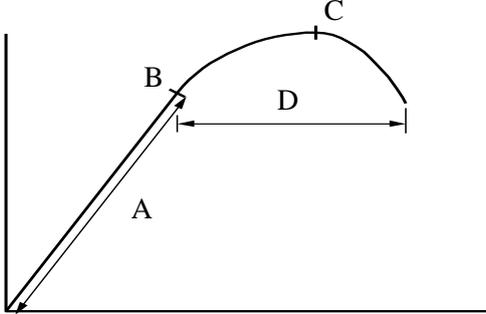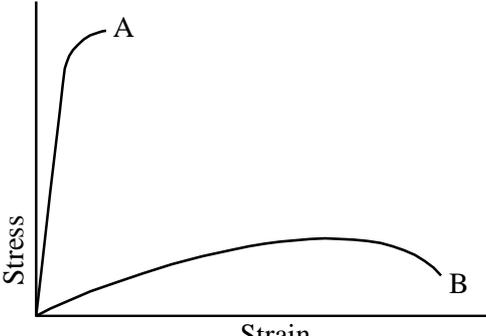Question	Mark Allocation					Marks
2.	(a)	$A = 100 \text{ mm}^2$	answer			1
		$\sigma = \frac{F}{A}$				
		$= \frac{1000}{100} \quad \frac{2000}{100} \quad \frac{3000}{100} \quad \frac{4000}{100} \quad \frac{5000}{100}$				
		$= 10 \text{ N/mm}^2 \quad 20 \text{ N/mm}^2 \quad 30 \text{ N/mm}^2 \quad 40 \text{ N/mm}^2 \quad 50 \text{ N/mm}^2$		any of the above (units not necessary)		1
		$\epsilon = \frac{\Delta l}{l}$				
		$= \frac{0.02}{200} \quad \frac{0.04}{200} \quad \frac{0.06}{200} \quad \frac{0.08}{200} \quad \frac{0.10}{200}$				
		$= 1 \times 10^{-4} \quad 2 \times 10^{-4} \quad 3 \times 10^{-4} \quad 4 \times 10^{-4} \quad 5 \times 10^{-4}$		any of the above		1
		$E = \frac{\sigma}{\epsilon} = \frac{20}{2 \times 10^{-4}}$		(must be two matching substitutions)		1
		$E = 100 \text{ kN/mm}^2$		answer and unit		1
	(b)	Soft Brass				1
	(c)		A – elastic range B – yield point C – ultimate load D – plastic range			1 1 1 1
	(d)		Brittle trace Ductile trace Correct labels Correct axis			1 1 1 1
						(14)





Question		Mark Allocation	Marks	
3.	(a)	Close: TIME = 10	1	
		for b0 = 1 to 20 (or COUNTER)	1	
		for b1=1 to 10	1	
		high 4	} both for 1 mark	
		pause 10		
		low 4		
		pause TIME		
		next b1	1	
		TIME = TIME + 2	1	
		if pin2 = 1 then finish	2	
next b0				
finish: return	including label 'close' above	1		
(b)	(i) Pulse Width Modulation (PWM)	1	1	
	(ii) Valve closes at a reducing speed either until closed or a fixed time has elapsed.	1	2	
		1		
	(c)	Mark = 10 ms	2	2
	Max Space = 10 + (2 × 20) = 50 ms			
Mark: Space ratio = 1:5				
4.	(a)	(i) Darlington Pair/Driver	1	1
		(ii) Protection diode to prevent current generated at switch-off damaging transistor.	2	2
	(b)	$V_{be2} = 0.7 \text{ V}$ by inspection	1	
		$V_{3600} = 2.3 - 1.4 = 0.9 \text{ V}$	calculation	1
		$I_{b1} = \frac{V}{R} = \frac{0.9}{3600}$	all substitutions	1
		$I_{b1} = 0.25 \text{ mA}$	answer	1
		$I_{b2} = 2.5 \times 10^{-6} \times 80$	substitutions	1
		$= 0.02 \text{ A}$	answer	1
		Pump resistance $R_p = \frac{P}{I^2}$		
		$= \frac{500}{2.13^2}$	substitutions	1
		$= 110 \Omega$	answer	1
		$h_{FE2} = \frac{I_c}{I_b} = \frac{2.13}{0.02}$	substitutions	1
		$= 106.5$	answer	1
		Overall current gain = $h_{FE1} \times h_{FE2}$		
		$= 80 \times 106.5$	substitutions	1
$= 8520$	answer	1		
See Supplementary Sheet, page 6			(15)	


Supplementary Sheet



Question	Mark Allocation		Marks	
4.	Quantity	Working		
	V _{in}	2.3 V		
	V _{be2}	0.7 V by inspection	1	
	I _{b1}	$V_{3600} = 2.3 - 1.4 = 0.9 \text{ V}$ Calculation $I_{b1} = \frac{V}{R} = \frac{0.9}{3600}$ All substitutions I_{b1} = 0.25 mA Answer	1 1 1	
	I _{b2}	$I_{b2} = 0.25 \times 10^{-3} \times 80$ Substitutions = 20 mA (0.02 A) Answer	1 1	
	I _p	2.13 A		
	Pump Resistance	$R_p = \frac{P}{I^2}$ $\frac{500}{2.13^2}$ Substitutions = 110 Ω Answer	1 1	
	h _{FE1}	80		
	h _{FE2}	$h_{FE2} = \frac{I_c}{I_b} = \frac{2.13}{0.02}$ Substitutions = 106.5 (no unit) Answer	1 1	
	Overall Current Gain	Overall gain: h _{FE1} × h _{FE2} = 80 × 106.5 Substitutions = 8520 (no unit) Answer	1 1	
				(12)

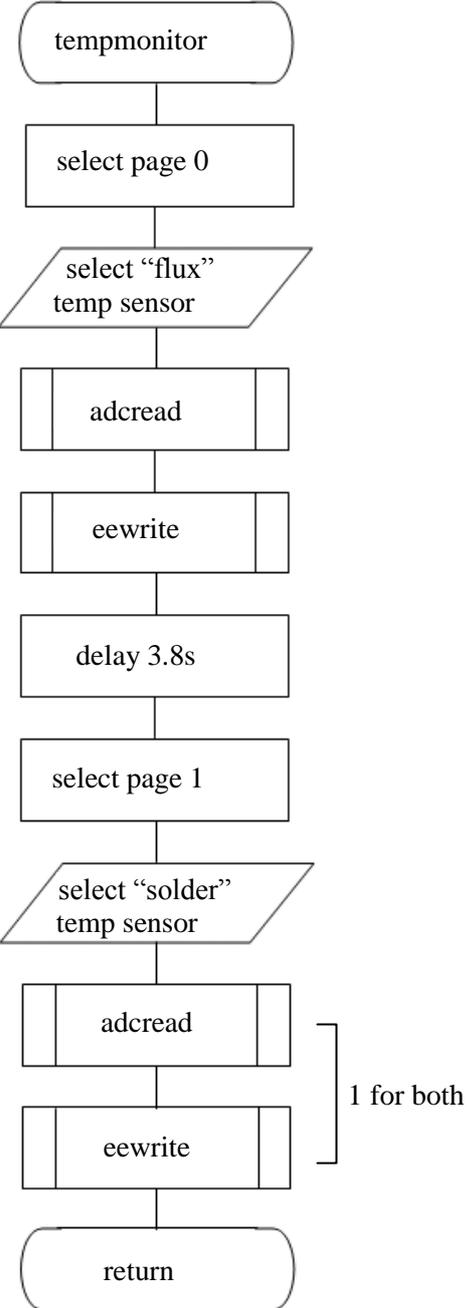Question	Mark Allocation	Marks		
5.	(a) To provide an appropriate signal within the correct voltage range.	1	1	
	(b) Data is held whether powered or not (ie non volatile) Data may be erased (electronically).	1 1	2	
	(c) How rapidly data is changing; memory available; consequence of missing an event (any 2 acceptable)	2	2	
	(d)	 <pre> graph TD A([tempmonitor]) --> B[select page 0] B --> C[/select "flux" temp sensor/] C --> D[adcread] D --> E[eewrite] E --> F[delay 3.8s] F --> G[select page 1] G --> H[/select "solder" temp sensor/] H --> I[adcread] I --> J[eewrite] I & J --- K[1 for both] J --> L([return]) </pre>	1 1 1 1 1 1 1 1 1 1	10
	If flowchart box is incorrect, do not award a mark (to a maximum of 4)			(15)

Question		Mark Allocation			Marks	
6.	(a)		Summing		1	1
	(b)	(i)	$\frac{R}{120} = \frac{11.98}{0.02}$	substitutions	1	
			$R = 71880 \Omega = 71.9 \text{ k}\Omega$	answer	1	2
	(b)	(ii)	$\frac{71880}{R_{g1}} = \frac{11.97}{0.03}$	substitutions	1	
			$R_{g1} = \frac{71880 \times 0.03}{11.97}$			
			$R_{g1} = 180.2 \Omega$	answer	1	2
	(b)	(iii)	$R_2 = 5 \times 2 = 10 \text{ k}\Omega$	answer	1	
			$R_1 = \frac{100}{40} \times 5 = 12.5 \text{ k}\Omega$	answer	1	2
	(c)		$V_2 = \frac{12500}{71880 + 12500} \times 12$	substitutions	1	
			$= 0.021 \text{ V}$	answer	1	
		$V_{\text{out}} = (0.03 \times (-40)) + (0.021 \times (-50)) + (0.02 \times (-100))$	substitutions	3		
		OR				
		$V_{\text{out}} = -500 \left(\frac{0.03}{12.5} + \frac{0.021}{10} + \frac{0.02}{5} \right)$				
		$V_{\text{out}} = -1.2 - 1.05 - 2$	simplification	1		
		$= -4.25 \text{ V}$	answer	1	7	
						(14)

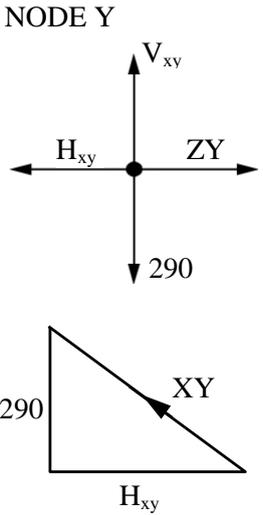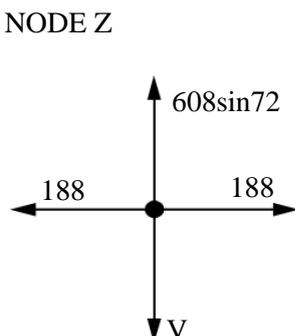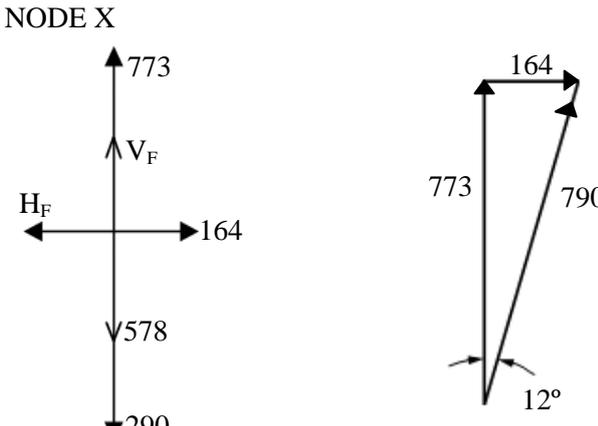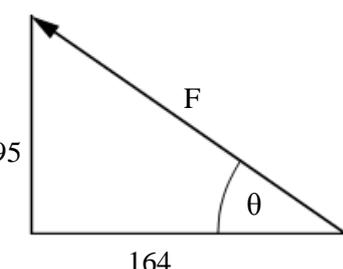
Question	Mark Allocation		Marks
7.	(a)	<p>(i) NODE Y</p>  <p>$V_{xy} = 290$ $H_{xy} = ZY$</p> <p>$XY = \frac{290}{\sin 57}$ (substitution) 1 $= 345.7 \text{ N}$ (answer) 1 $YZ = H_{XY} = 345.7 \cos 57$ (substitution) 1 $= 188 \text{ N}$ (answer) 1</p> <p>$H_{XZ} = 188$ $XZ = \frac{188}{\cos 72}$ (substitution) 1 $= 608 \text{ N}$ (answer) 1</p> <p>(ii) NODE Z</p>  <p>$V = 608 \sin 72$ $V = 578 \text{ N}$ (answer) 1</p> <p>NODE X</p>  <p>Applied force 790 N Components $F_n = 164 \text{ N}; F_v = 773 \text{ N}$</p> <p>$H_F = 164$ $V_F = (578 + 290) - 773$ (substitution) 1 $= 95$ (answer) 1</p> <p>$F = \sqrt{95^2 + 164^2}$ (substitution) 1 $= 190 \text{ N}$ (answer) 1</p> <p>(iii)</p>  <p>$\tan \theta = \frac{95}{164}$ (substitution) 1 $\theta = 90 - 30.1$ (substitution) 1 $\theta = 59.9^\circ$ (answer) 1</p>	<p>6</p> <p>6</p> <p>2</p> <p>(14)</p>


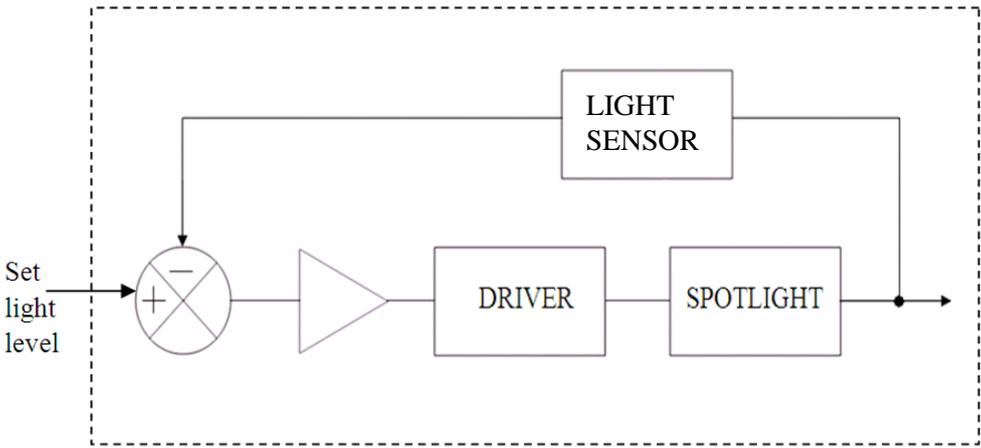
Question	Mark Allocation		Marks		
8.	(a)	 <p data-bbox="606 716 973 952"> 1 for set light level 1 for error detector 1 for error amplifier 1 Driver 1 Spotlight 1 Light Sensor 1 for Light Sensor connections </p>		1 1 1 1 1 1 1	7
	(b)	$V_{\text{ref}} = \frac{2}{2 + 4.8} \times 12$ $= 3.53 \text{ V}$	substitution answer	1 1	2
	(c)	At 400 Lux $R_{\text{LDR}} = 310 \Omega$ (accept 300–320) Difference amplifier gain $= \frac{120}{10} = 12$ $V_o = A_v (V_{\text{ref}} - V_{\text{in}})$ So $V_{\text{ref}} - V_{\text{in}} = \frac{8}{12} = 0.667 \text{ V}$ $V_{\text{LDR}} = 3.53 - 0.667$ $= 2.86 \text{ V}$ $R = \frac{310 \times 2.86}{9.14}$ $= 97.0 \Omega$	from Data Book gain calculation error calculation substitution answer substitution answer	1 1 1 1 1 1 1	7
(16)					

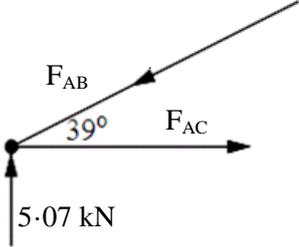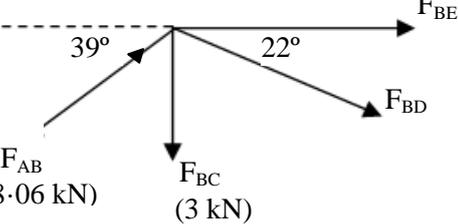Question	Mark Allocation		Marks	
9.	(a)	About R_2 : $\Sigma M = 0$ $37.1R_1 = (19.6 \times 4.8) + (31.3 \times 3)$ $R_1 = 5.07 \text{ kN}$	substitutions 1 answer 1	2
	(b)	NODE A  $5.07 = AB \sin 39^\circ$ $F_{AB} = 8.06 \text{ kN STRUT}$ $AC = 8.06 \cos 39^\circ$ $F_{AC} = 6.26 \text{ kN TIE}$ NODE B  $F_{BC} = 3 \text{ kN}$ $\Sigma F_V = 0$ (stated or implicit) $F_{AB} \sin 39 - F_{BC} - F_{BD} \sin 22 = 0$ $F_{BD} = \frac{8.06 \sin 39 - 3}{\sin 22}$ $F_{BD} = 5.53 \text{ kN TIE}$	substitutions 1 force including unit 1 nature 1 substitutions 1 force, unit 1 nature 1 1 1 3 1 force, unit 1 nature 1	
	(c)	$\epsilon = \frac{\Delta l}{l}$ $= \frac{2.5}{13700}$ $= 182 \times 10^{-6}$ $E = 70 \times 10^3 \text{ N/mm}^2$ $\sigma = E \epsilon$ $= 70 \times 10^3 \times 182 \times 10^{-6}$ $= 12.77 \text{ N/mm}^2$ $A = \frac{F}{\sigma}$ $= \frac{8000}{12.77}$ $= 626.5 \text{ mm}^2$ $\text{Area} = \frac{\pi D^2}{4} - \frac{\pi d^2}{4}$ $d = \sqrt{D^2 - \frac{4A}{\pi}}$ $d = \sqrt{75^2 - \frac{4 \times 626.5}{\pi}}$ $d = 69.5$ Min wall thickness = $\frac{75 - 69.5}{2} = 2.75 \text{ mm}$	substitutions 1 answer 1 value from Data Book 1 substitutions 1 answer 1 substitution 1 answer 1 substitutions 1 answer 1 substitutions 1 answer 1	11

Question		Mark Allocation	Marks	
10.	(a)	(holding) torque accurate (angular) positioning; easily controlled by microcontroller (any 2 acceptable answers)	1 1 2	
	(b)	(i)	locate: if pin 1 = 0 then locate inc label 1	
			loop: if pin 0 = 0 then loop inc label 1	
			gosub pulsedata 1	
b5 = DATA 1				
pause 500 1				
gosub pulsedata 1				
if DATA = b5 then onward (OR b5 = DATA) 1				
goto error 1				
onward: gosub pulsedata b6 = DATA pause 500 gosub pulsedata if DATA = b6 then onagain (OR b6 = DATA) 1			Repeated block of code	1
goto error 1				
onagain: high 4 inc label 1				
gosub x-move 1				
high 6 1				
gosub y-move 1				
ending: return inc label 1				
error: high 2 inc label 1				
goto ending 1				
(ii)	xmove: for count = 1 to b5 (OR DATA) correct variable 1	high 5		
		pause 10		
		low 5 high & low 1		
		pause 10 both pauses 1		
		next count counting loop 1		
return 1				
(c)	<ul style="list-style-type: none"> The variable-resistor-voltage-divider sets light level required to switch comparator output. LDR produces increasing voltage signal as light level decreases. When picker not breaking light beam comparator output is 0 V. When light beam broken comparator output goes high. Voltage to microcontroller conditioned (by resistors) 	1		
		1		
		1		
		1		
			4	
			18	
			5	

Question		Mark Allocation	Marks	
(d)		85% of 12 V = 10.2 V	saturation value	1
		$\frac{R}{2} = \frac{5}{5.2}$	expression and substitution	1
		R = 1.92 kΩ	answer	1
(e)	(i)	$\frac{R_2}{6} = \frac{4}{5}$	substitutions	1
		R ₂ = 4.8 kΩ	answer	1
		$\frac{R_1}{6 + 4.8} = \frac{3}{9}$	substitutions	1
		R ₁ = 3.6 kΩ	answer	1
	(ii)	‘Dark’ signal changes state when V _{in} = V _{ref} = 9 V		1
		$\frac{R_{LDR}}{5} = \frac{9}{3}$	substitutions	1
R _{LDR} = $\frac{9}{3} \times 5 = 15$ kΩ		answer	1	
	Light level for 15 kΩ = 5 lux (accept 5–6 lux)	answer	1	
				4
				(40)

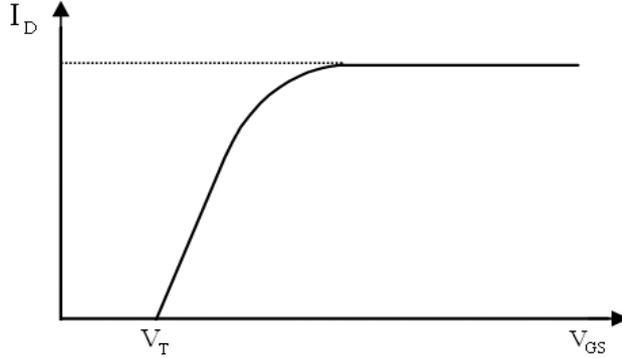Question		Mark Allocation	Marks	
11.	(a)	Thermocouple generates a voltage signal dependent on temperature. Thermistor is resistive so requires power supply and voltage divider.	1 1	2
	(b)	thermocouple 1: 400 °C = 16 mV thermocouple 2: 100 °C = 4 mV	2 values 1	
		$T_1 : -\frac{R_f}{R_i} = -\frac{18}{200} = -0.09 \times 16 = -1.44 \text{ mV}$	1	
		$V_1 \text{ to diff. amp} = -1.44 \times (-1)$ $= 1.44 \text{ mV}$	answer 1	
		$T_2 : 1 + \frac{R_f}{R_i} = 1 + \frac{270}{100} = 3.7$	substitutions 1	
		$V_2 \text{ to diff. amp} = 3.7 \times 4$ $= 14.8 \text{ mV}$	answer 1	
		difference at inputs = 14.8 - 1.44 = 13.36 mV	1	
		$V_{\text{out}} = 3.84 \text{ V}$ $A_v = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{3.84}{13.36 \times 10^{-3}}$	substitutions 1	
		$= 287.5$ $A_v = \frac{R_f}{R_i} \Rightarrow R_i = \frac{R_f}{A_v}$	answer no unit 1	
		$= \frac{820 \times 10^3}{287.5}$ $R_i = 2.85 \text{ k}\Omega$	substitutions 1 answer 1	10
(c)	(i)	Threshold voltage = 3.82 V (3.80 ≤ V _T ≤ 3.82 V) I _{sat} = 40.8 mA	within range value 1 1	2
	(ii)		offset from origin correct curve shape saturation line axis labels 1 1 1 1	4
	(iii)	$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$ $= \frac{10.2}{0.04}$ $= 255$	substitutions 1 answer (no unit) 1	2

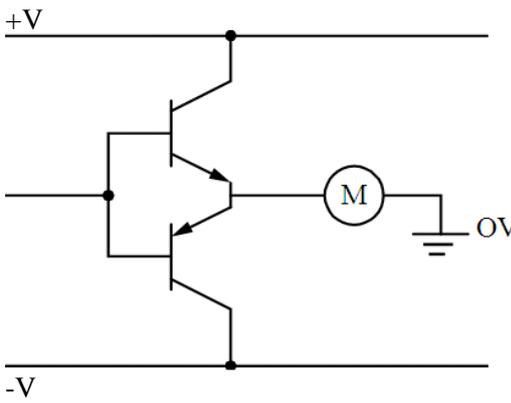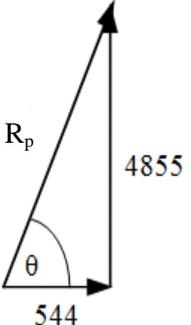Question	Mark Allocation	Marks
(d)		<p data-bbox="1125 324 1300 358">+/-power rails 1</p> <p data-bbox="1157 369 1300 403">npn correct 1</p> <p data-bbox="1157 414 1300 448">pnp correct 1</p> <p data-bbox="1029 459 1300 492">motor with connections 1</p> <p data-bbox="1476 459 1500 492">4</p>
(e)	<p data-bbox="279 705 486 750">$\Sigma M_{\text{pivot}} = 0$ (+ve)</p> <p data-bbox="279 772 981 817">$-(900 \cos 20 \times 1.6) + (720 \sin 8 \times 1.2) + (F \sin 77 \times 0.3) = 0$</p> <p data-bbox="279 840 718 907">$F = \frac{(900 \cos 20 \times 1.6) + (720 \sin 8 \times 1.2)}{0.3 \sin 77}$</p> <p data-bbox="279 929 550 963">$F = 4218 \text{ N} = 4.22 \text{ kN}$</p>	<p data-bbox="1204 772 1300 806">3 terms 3</p> <p data-bbox="1141 862 1300 896">manipulation 1</p> <p data-bbox="1204 929 1300 963">answer 1</p> <p data-bbox="1476 929 1500 963">5</p>
(f)	<p data-bbox="279 996 454 1030">$\Sigma F_v = 0$ (\uparrow+ve)</p> <p data-bbox="279 1052 813 1086">$-900 \cos 20 + 720 \sin 8 - 4218 \sin 77 + R_v = 0$</p> <p data-bbox="279 1108 598 1142">$R_v = 845.7 - 100.2 + 4110$</p> <p data-bbox="279 1164 454 1198">$R_v = 4855 \text{ N} \uparrow$</p> <p data-bbox="279 1220 438 1254">$\Sigma F_h = 0$ (\rightarrow+ve)</p> <p data-bbox="279 1276 805 1310">$-900 \sin 20 + 720 \cos 8 - 4218 \cos 77 + R_h = 0$</p> <p data-bbox="279 1332 534 1366">$R_h = 308 - 713 + 949$</p> <p data-bbox="279 1388 478 1422">$R_h = 544 \text{ N} \rightarrow$</p> <div data-bbox="327 1433 518 1758">  </div> <p data-bbox="550 1467 798 1512">$R_p = \sqrt{4855^2 + 544^2}$</p> <p data-bbox="550 1523 710 1556">$R_p = 4885 \text{ N}$</p> <p data-bbox="550 1601 821 1668">$\theta = \tan^{-1}\left(\frac{4855}{544}\right) = 83.6^\circ$</p> <p data-bbox="766 1668 821 1702">6.4°</p>	<p data-bbox="1117 1052 1300 1086">3 correct terms 3</p> <p data-bbox="1204 1164 1300 1198">answer 1</p> <p data-bbox="1117 1276 1300 1310">3 correct terms 3</p> <p data-bbox="1204 1388 1300 1422">answer 1</p> <p data-bbox="1109 1534 1300 1568">answer and unit 1</p> <p data-bbox="1364 1713 1380 1747">1</p> <p data-bbox="1476 1713 1500 1747">11</p> <p data-bbox="1460 1780 1508 1814">(40)</p>

[END OF MARKING INSTRUCTIONS]