

Distributed  
Spring 2005

## E2.2 SAMPLE Examination

PLEASE ANSWER QUESTION 1 AND ANY **TWO** of QUESTIONS 2,3 and 4.

### QUESTION 1 IS MANDATORY

- 1
- a) A transformer with a 1:10 turns ratio has a voltage gain of 10. What is its maximum possible current gain? Is such a transformer an amplifier? [5 marks]
- b) What is the value of the input impedance of an ideal transimpedance amplifier? What is the value of the output impedance of an ideal current amplifier? [5 marks]
- c) You need to use realistic current amplifier as a voltage amplifier. To do this you decide to use negative feedback to improve its input-output impedance. What feedback connection will you choose, and why? [5 marks]
- d) What is the input impedance of the circuit in figure 1.1? The voltage gain of the amplifier is  $G=19$ , as indicated. The amplifier is an otherwise ideal voltage amplifier. [5 marks]

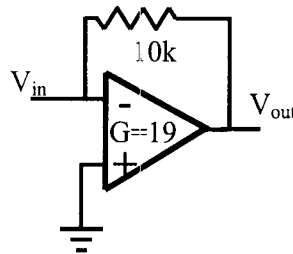


Figure 1.1

- e) Write an expression for the general form of the second order band-pass filter transfer function. Identify any parameters appearing in this equation. [5 marks]
- f) The FET Cascode amplifier is a two-stage amplifier. Name the two stages, and describe the terminal characteristics (input-output impedance) and function of each one. Why does the cascode amplifier have a wider bandwidth than its first stage used alone at the same voltage gain? [5 marks]
- g) Which family of 2-port parameters is the most suitable to represent a realistic operational amplifier? [5 marks]
- h) Prove that a unilateral voltage amplifier is also a unilateral current amplifier, and conversely, a unilateral current amplifier is also a unilateral voltage amplifier. [5 marks]

## ANSWERS Q1:

(a) Max current gain is 0.1 since the transformer is passive and its power gain needs to be less than or equal to unity. This is NOT an amplifier.

(b) 0 and  $\infty$  respectively.

(c) series-shunt, to raise the input impedance and lower the output impedance

(d) 0.5k due to the Miller effect (the feedback element divided by G+1).

(e)  $H(s) = \frac{H_0 2\zeta s \omega_0}{s^2 + 2\zeta s \omega_0 + \omega_0^2}$  ( $H_0$  is max gain at resonance,  $\omega_0$  the resonant frequency,  $\zeta$  the damping factor.

(f) Common Source (transconductance amplifier) – Common gate (transimpedance amplifier). The Voltage gain of the common source is -1, hence the miller effect is minimized.


(g) G parameters, also known as voltage gain or inverse hybrid parameters.

(h) Need to show  $\left. \frac{\partial V_1}{\partial V_2} \right|_{I_1=0} = 0$  But we know the voltage amplifier is unilateral. Therefore, in G

representation:  $I_1 = G_{11}V_1 \Rightarrow V_1 = \frac{1}{G_{11}}I_1$  This implies we can write:  $\left. \frac{\partial V_1}{\partial V_2} \right|_{I_1=0} = \left. \frac{\partial V_1}{\partial V_2} \right|_{V_1=0} = 0$  QED.

2.

- (a) Calculate the voltage gain of the amplifier in figure 2.1 if the op-amp is ideal. What is this transfer function? [10 marks]
- (b) Now consider a finite gain op-amp, with  $G = 1000$  otherwise ideal. If  $1/2\pi\sqrt{LC} = 1\text{kHz}$ ,  $\sqrt{L/C} = 50\Omega$  calculate at which frequency the gain will deviate from its ideal value by more than 10% [10 marks]
- (c) Now assume the op-amp is a real dominant pole amplifier, with a low frequency open loop gain of  $G=1000$  and a gain bandwidth product of  $\text{GBW}=10^4$  Hz. Write an expression, and make a magnitude and phase bode plot for the closed loop amplifier. [10 marks]

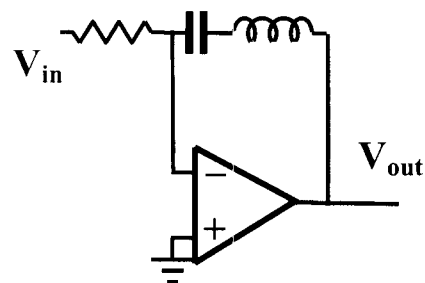

**Figure 2.1:** An amplifier.

### Answer Question 2:

a) This is an inverting amplifier, therefore


$$A_v = -\frac{sL + 1/sC}{R} = -\frac{s^2LC + 1}{R}$$

This is a band reject function

[10 marks]

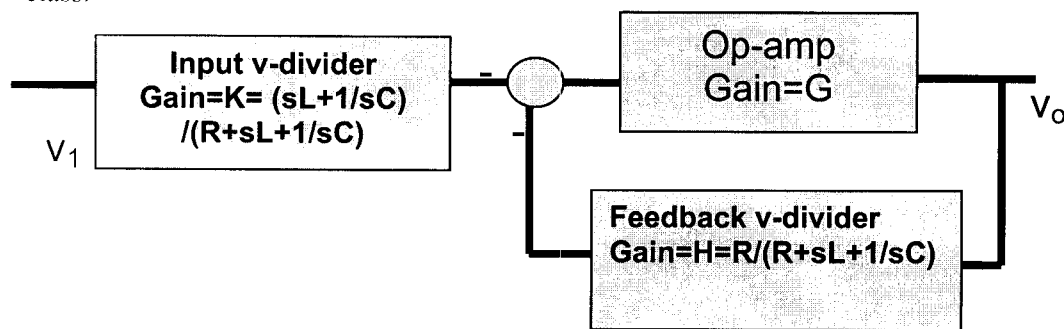b) The correction comes from the formula

$A_v = G_0 \frac{G}{1+GH}$  the question is to make  $GH > 100$ . We can view the amplifier as shown in class:



The loop gain is then

$$G_{LOOP} = \frac{A_v R}{R + sL + 1/sC} = \frac{A_v R sC}{s^2LC + sRC + 1}$$

This is a bandpass function, with a peak gain of

$H_0 = A_v RC / RC = A_v$ . Since  $A_v = 1000$ , it follows that the loop gain will be less than 10 at 0.01 and 100 times the centre frequency, i.e. 10Hz and 100kHz.

[10 marks]

c) the dominant pole amplifier has a response:

$G(s) = G_0 / (1 + s\tau)$  and the gain bandwidth product is :

$GBW = G_0 / \tau$ . Then  $G_0 = 10^3$  and  $\tau = 1/2\pi \cdot 10\text{Hz} = 15.9\text{ms}$  or, simply, the breakpoint is at 10Hz.

We can now write for the transfer function:


$$A_v = \frac{sL + 1/sC}{R + sL + 1/sC} \cdot \frac{\frac{G_0}{1 + s\tau}}{1 + \frac{R}{R + sL + 1/sC} \frac{G_0}{1 + s\tau}} = \frac{(s^2LC + 1)G_0}{(s^2LC + sRC + 1)(1 + s\tau) + sRCG_0}$$

This has a breakpoint at  $f = 1\text{kHz}$ ,

[10 marks]

3 Filters can be synthesized by transforming the function of circuit elements using feedback circuits. In this problem we synthesise a 2<sup>nd</sup> order LC filter by using a Generalised impedance converter.

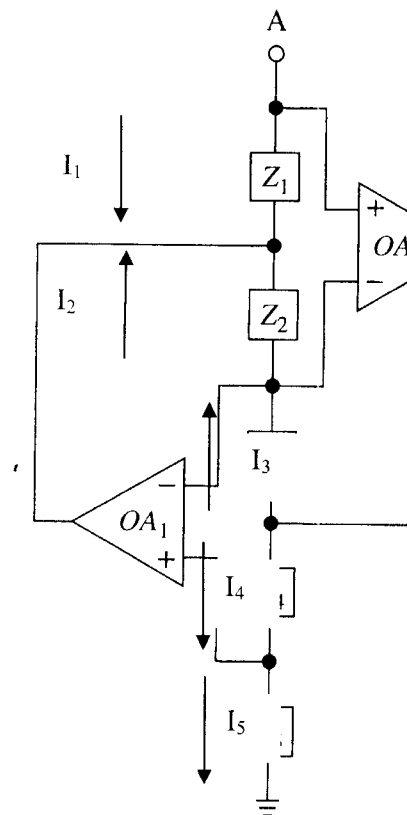- (a) Analyse the generalized impedance converter in figure 3.1, and derive an equation expressing the terminal impedance at A in terms of the components used. [10 marks]
- (b) Choose components to implement a grounded inductor using only resistors and capacitors. What is the inductance value? [5 marks]
- (c) Choose components that allow you to create a floating capacitance of greater value than the available components. [5 marks]
- (d) Using only resistors (any value), op-amps and 100nF capacitors design a 2<sup>nd</sup> order LC voltage low pass filter with a break frequency at 15.9Hz. Since this is an audio filter choose your components so that  $\sqrt{\frac{L}{C}} = 600 \Omega$  in your filter. (this choice of components impedance-matches the filter to a 600 Ohm source, 600 ohms being quite standard in audio work) [10 marks]



$$\frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

Figure 3.1

**Answer Q3:**

**ANSWER:**

a) The golden rules  $V_+ = V_-$  and  $i_+ = i_- = 0$  for each op-amp lead to:

$$V_1 = V_{2+} = V_2 = V_{1-} = V_{1+} \text{ and } i_3 Z_3 = i_4 Z_4 \Rightarrow i_3 = i_4 \frac{Z_4}{Z_3} = i_2, \quad i_1 Z_1 = i_2 Z_2 \Rightarrow i_1 = i_2 \frac{Z_2}{Z_1}.$$

$$\Rightarrow i_5 = V_4 / Z_5 = i_4$$

putting all together,

$$Z = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

[10 marks]


b) make  $Z_2$  or  $Z_4$  a capacitor, keep everything else a resistor of suitable magnitude.

[5 marks]

c) make  $Z_1$ ,  $Z_3$  or  $Z_5$  a capacitor, keep everything else a resistor of suitable magnitude. The gain will be the ratio. If a floating element is required simply use the ground connection as a second terminal.

[5 marks]

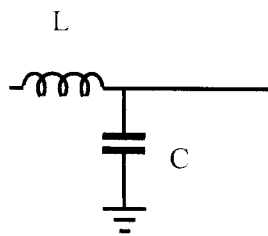d) For the filter required we need to implement:



$$\left. \begin{aligned} \text{with } \frac{1}{\sqrt{LC}} &= 15.9\text{Hz} = 100\text{rad/s} \\ \sqrt{\frac{L}{C}} &= 600 \, \Omega \end{aligned} \right\} \Rightarrow C = 16.67 \, \mu\text{F}, L = 6\text{H}$$

Starting with 100nF capacitor we need to magnify the capacitance by a factor of 166.7, and invert the 100nF capacitance to 6H:

$$Z_3 = \frac{1}{j\omega C} \Rightarrow Z_1 = \frac{1}{j\omega C \frac{R_2 R_4}{R_1 R_5}} \Rightarrow$$

For the capacitor, say

$$\frac{R_2 R_4}{R_1 R_5} = 16.67 \mu F / 100 nF = 166.7$$

For the inductor:

$$Z_2 = \frac{1}{j\omega C} \Rightarrow Z_L = j\omega C \frac{R_1 R_3 R_5}{R_4} \Rightarrow$$

$$\frac{R_1 R_3 R_5}{R_4} = 6 / 100 n = 6 \times 10^7$$

[10 marks]

4. Analyse the filter in figure 4.1. What function does it perform? What is its  $Q$  and centre frequency? What is its maximum gain?

[30 marks]

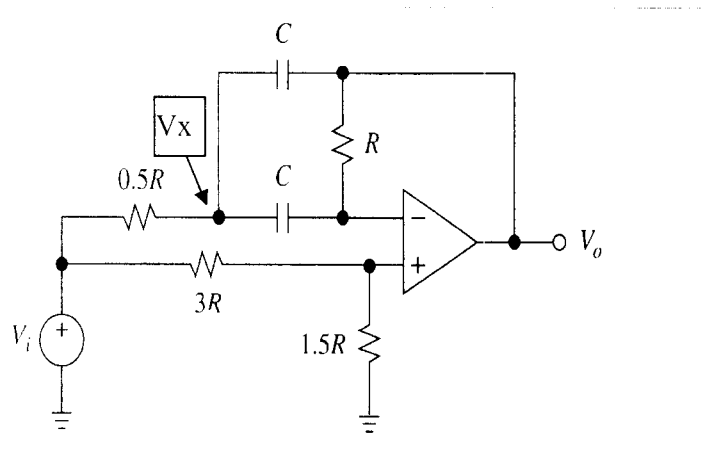


Figure 4.1



#### Answer, Question 4

(as some may remember this is a Deliyannis-Friend MFB filter)

This problem is included here because the solution is not (by error) in the distributed sets.

Let  $V_x$  the unknown node,  $G=1/R$ ,  $\tau = RC$

$$V_i = \frac{1}{3}V_o = V$$

$$\text{KCL on } V : \begin{cases} \left(V_o - \frac{V_i}{3}\right)G = sC\left(\frac{V_i}{3} - V_x\right) \Rightarrow \\ \left(V_o - \frac{V_i}{3}\right)\frac{1}{s\tau} = \frac{V_i}{3} - V_x \Rightarrow V_x = \frac{V_i}{3} - \left(V_o - \frac{V_i}{3}\right)\frac{1}{s\tau} \\ V_x = \frac{V_i}{3s\tau}(s\tau + 1) - \frac{V_o}{s\tau} \end{cases}$$

$$\text{KCL on } V_x : \begin{cases} sC\left(\frac{V_i}{3} - V_x\right) + 2G(V_i - V_x) + sC(V_o - V_x) = 0 \Rightarrow \\ s\tau\left(\frac{V_i}{3} - V_x\right) + 2(V_i - V_x) + s\tau(V_o - V_x) = 0 \Rightarrow \\ V_i\left(\frac{s\tau}{3} + 2\right) + s\tau V_o = 2V_x(1 + s\tau) \end{cases}$$

Combine the two,

$$\begin{aligned} V_i\left(\frac{s\tau}{3} + 2\right) + s\tau V_o &= 2\left(\frac{V_i}{3s\tau}(s\tau + 1) - \frac{V_o}{s\tau}\right)(1 + s\tau) \Rightarrow \\ V_i s\tau(s\tau + 6) + 3s^2\tau^2 V_o &= 2V_i(1 + s\tau)^2 - 6V_o(1 + s\tau) \Rightarrow \\ V_i(s^2\tau^2 + 6s\tau + 2 - 2s^2\tau^2 - 4s\tau) &= -V_o(6 + 6s\tau + 3s^2\tau^2) \Rightarrow \\ \frac{V_i}{V_o} &= \frac{-s^2\tau^2 + 2s\tau + 2}{6(0.5s^2\tau^2 + s\tau + 1)} = -\frac{1}{3} \frac{0.5s^2\tau^2 - s\tau + 1}{0.5s^2\tau^2 + s\tau + 1} \end{aligned}$$

This is an (inverting) all pass filter of gain=1/3, centre frequency:

$$\frac{1}{\omega_c} = 0.5\tau^2 \Rightarrow \omega_0 = \frac{\sqrt{2}}{\tau} \text{ and quality factor:}$$

$$2Q = \omega_c = \tau \Rightarrow 2Q = \sqrt{2} \Rightarrow Q = \frac{1}{\sqrt{2}}$$